
*In The Name of God The Most
Compassionate The Most Merciful*



General Theory of Electric Machines



Table of Contents



1. Introduction

2. Transformers

3. Reference-Frame Theory

4. Induction Machines

5. Synchronous Machines



Chapter 2

Transformers

2.1. Introduction

2.2. Ideal Transformers

2.3. Model of Two-Winding Transformers

2.4. Simulation of Two-Winding Transformers

2.5. Load Modelling

2.6. Core Saturation Effects

2.7. Three-Phase Connections



Introduction

Transformers have the following characteristics

1. Transformers are **electromagnetic energy conversion** systems; as they receive electrical energy from the network; convert it to the magnetic energy; and then the magnetic energy is converted to the electrical energy with different voltage and current level.
2. A transformer has at least two windings: a primary and a secondary winding. **Primary winding** is the winding connected to the **power source** and the **secondary winding** is that connected to the **load**.
3. There is **no electrical connection** between the primary and secondary windings (except in auto-transformers); the connection is through a magnetic field.



Introduction

4. If the secondary voltage is lower than that of primary, the transformer is **step-down**; otherwise it is **step-up**.
5. **Swapping the primary and secondary windings** will change a step-down transformer to a step-up transformer and vice-versa.
6. In a **step-up** transformer, the **number of turns of the secondary winding** is **higher** than that of the **primary** winding.
7. In a **step-down** transformer, the **number of turns of the secondary winding** is **lower** than that of the **primary** winding.
8. Since transformers have **no mechanical part**, their **efficiency** is normally **very high**.

Applications of Transformers



1. Electric Power **Transmission Systems**.

2. **Impedance Matching** (e.g. in speakers).



3. **Blocking** the dc component of an ac + dc signal or power.

4. Voltage and current **measurement**: Voltage or potential transformers (VT) or (PT); Current transformers (CT).



Ideal Transformers

An ideal transformer has the following characteristics:

1. The **ohmic losses** due to the primary and secondary winding resistances are **neglected**.
2. The **core losses** are **neglected**.
3. The **magnetizing curve** of the transformer core is assumed to be **linear**.

$$r_1 = r_2 = 0$$

$$R_c \rightarrow \infty$$

4. The **leakage flux** of the windings is **neglected**.



$$L_{l1} = L_{l2} = 0$$

5. The **core permeability** goes to **infinity**.

$$\mu_c \rightarrow \infty$$



$$L_{m1} \rightarrow \infty$$

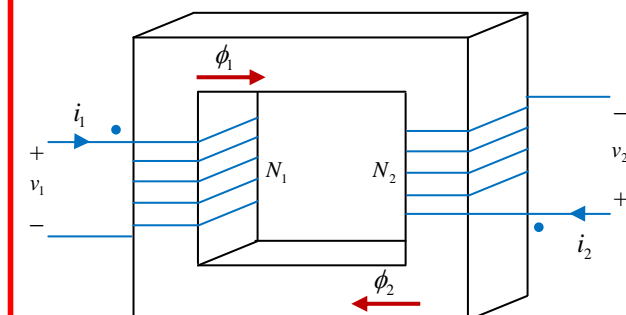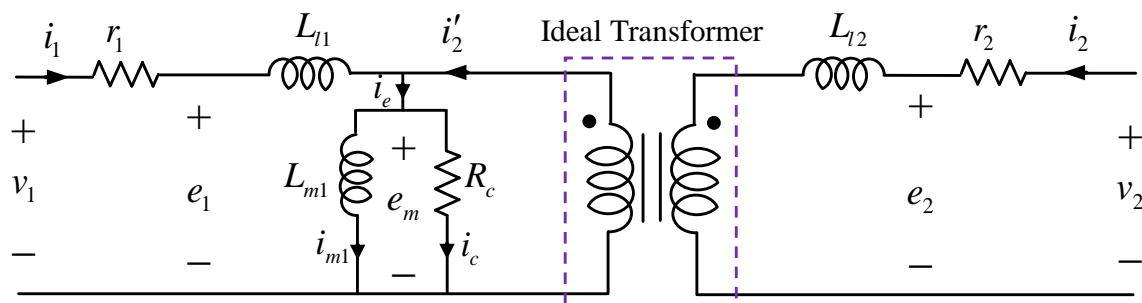


Ideal Transformers

- The **induced voltage** in the primary and secondary windings will be



$$e_1 = N_1 \frac{d\phi_1}{dt}$$

$$e_2 = N_2 \frac{d\phi_2}{dt}$$

$$\phi_1 = \phi_2 = \phi_m$$

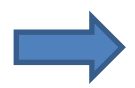


$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$

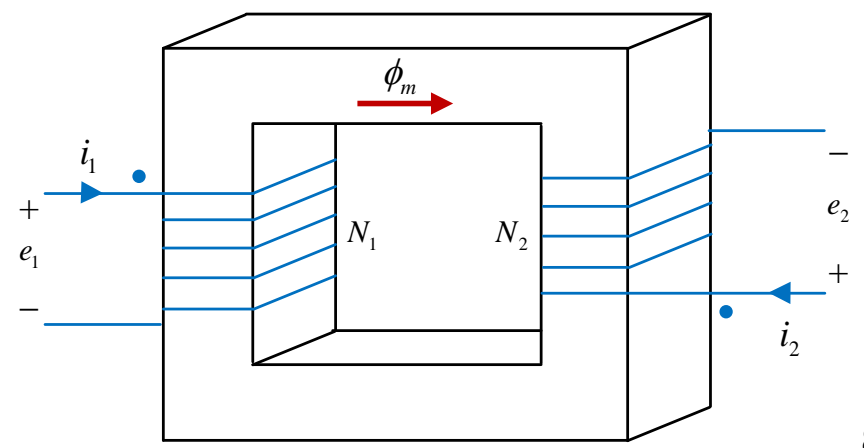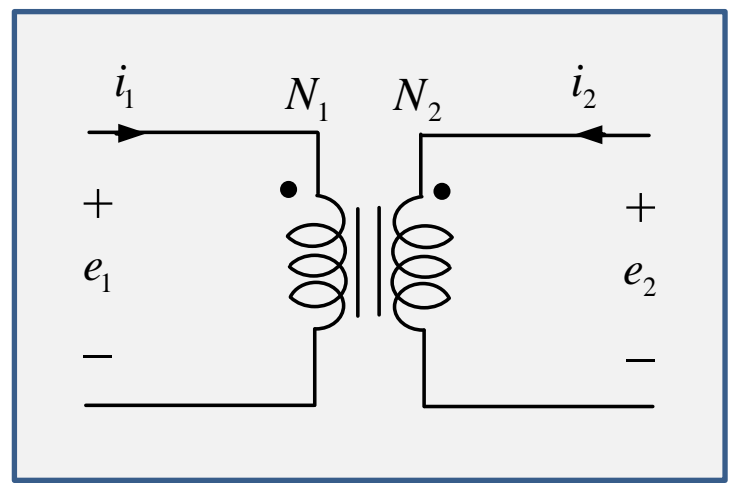

Ideal Transformers

- Since the algebraic sum of the magneto-motive forces (MMFs) is zero, in two-winding transformers it follows that:



$$\sum_k N_k i_k = 0$$

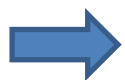

$$N_1 i_1 + N_2 i_2 = 0$$




$$\frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

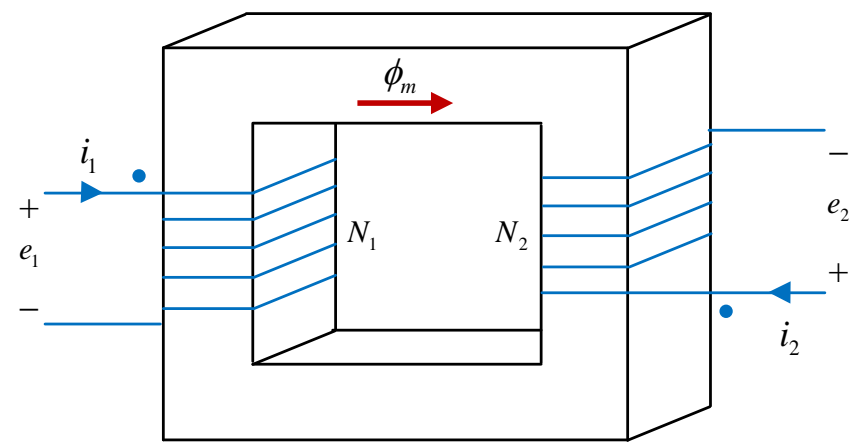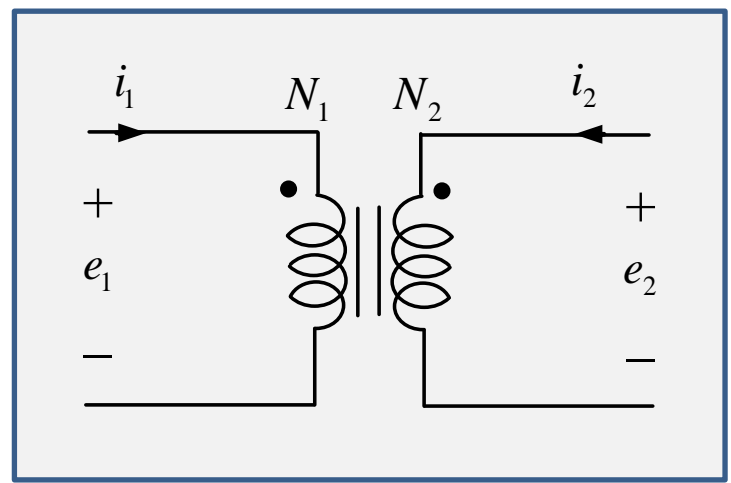

More Realistic Transformers

The transformer has the following characteristics:

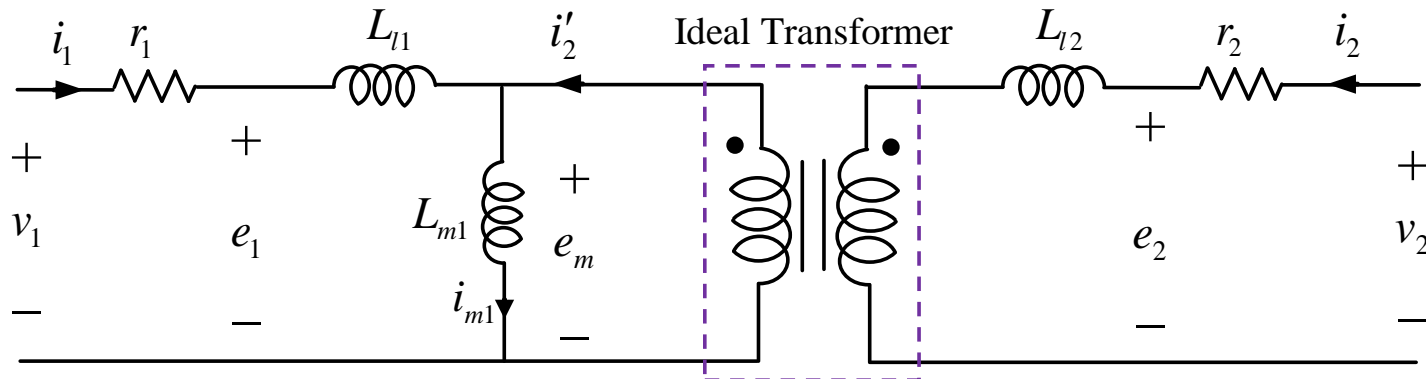1. The **ohmic losses** due to the primary and secondary winding resistances are **considered**.
2. The **core losses** are still **neglected**.
3. The **magnetizing curve** of the transformer core is still assumed to be **linear**.
4. The **leakage flux** of the windings is **considered**.
5. The **core permeability** is a **finite** value.



Model of Two-Winding Transformers

1. Flux linkage equations

- The fluxes of the windings are:



$$\phi_1 = \phi_{l1} + \phi_m$$

$$\phi_2 = \phi_{l2} + \phi_m$$

- The flux linkages of the windings are:

$$\lambda_1 = N_1 \phi_1 = N_1 (\phi_{l1} + \phi_m)$$
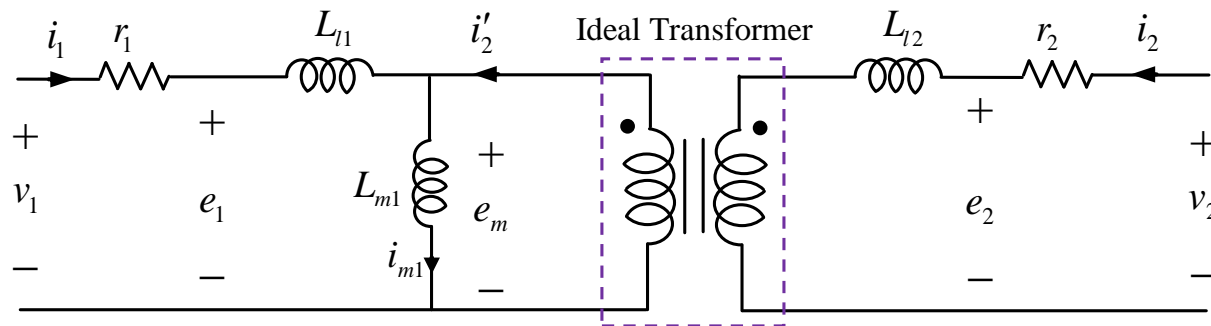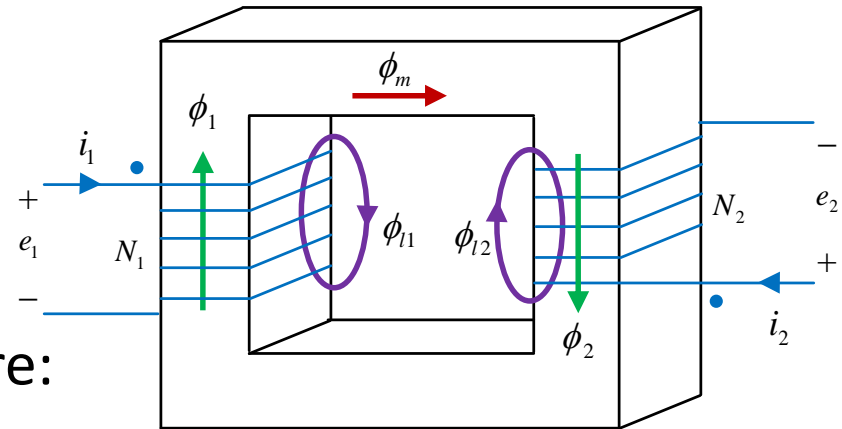
$$\lambda_2 = N_2 \phi_2 = N_2 (\phi_{l2} + \phi_m)$$



Model of Two-Winding Transformers

1. Flux linkage equations

- The relation between the **MMF**, magnetic **flux** and **permeance** is as follows:


$$MMF = \sum Ni = \mathfrak{R}\phi = \frac{1}{P}\phi$$

$$\mathfrak{R} = \frac{1}{P}$$

where \mathfrak{R} is the reluctance and P is the permeance.

- It can be rewritten as

$$\phi = P \sum Ni$$

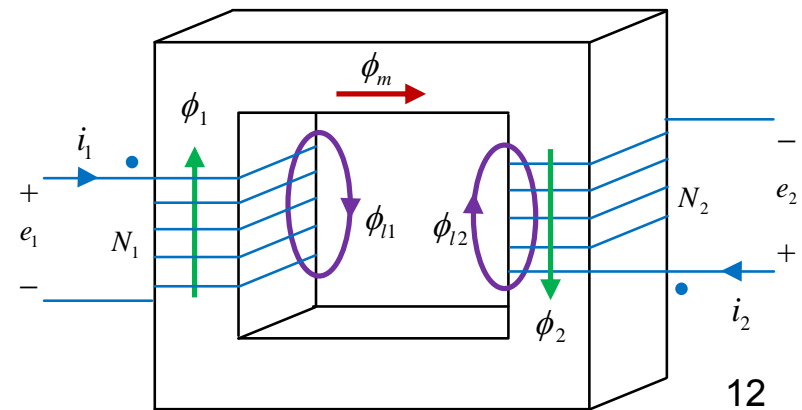

Model of Two-Winding Transformers

1. Flux linkage equations

- Substitution the permeance relation into the flux linkage expression for the primary winding yields

$$\lambda_1 = N_1(\phi_{l1} + \phi_m)$$


$$\phi = P \sum Ni$$

$$\lambda_1 = N_1 \left[(N_1 i_1 P_{l1}) + (N_1 i_1 + N_2 i_2) P_m \right]$$

$$\lambda_1 = (N_1^2 P_{l1} + N_1^2 P_m) i_1 + N_1 N_2 P_m i_2$$

 L_{11}
 L_{12}

$$\lambda_1 = L_{11} i_1 + L_{12} i_2$$

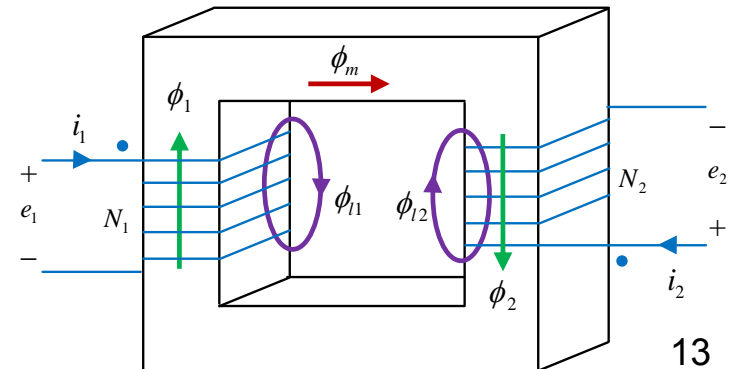

Model of Two-Winding Transformers

1. Flux linkage equations

- Similarly for the secondary winding:

$$\lambda_2 = N_2(\phi_{l2} + \phi_m)$$


$$\phi = P \sum Ni$$

$$\lambda_2 = N_2 \left[(N_2 i_2 P_{l2}) + (N_1 i_1 + N_2 i_2) P_m \right]$$

$$\lambda_2 = (N_2^2 P_{l2} + N_2^2 P_m) i_2 + N_1 N_2 P_m i_1$$

$$L_{22} \qquad L_{21}$$

$$\lambda_2 = L_{21} i_1 + L_{22} i_2$$

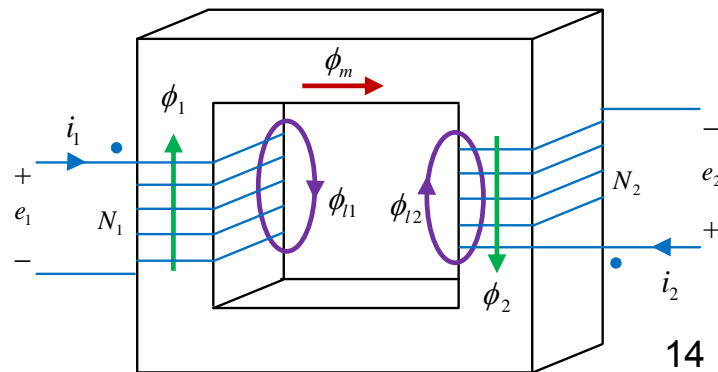

Model of Two-Winding Transformers

1. Flux linkage equations


- The resulting flux linkage equations for the two-winding transformers in terms of the winding inductances are:

$$\lambda_1 = L_{11}i_1 + L_{12}i_2$$

$$\lambda_2 = L_{21}i_1 + L_{22}i_2$$

- Or in the matrix form
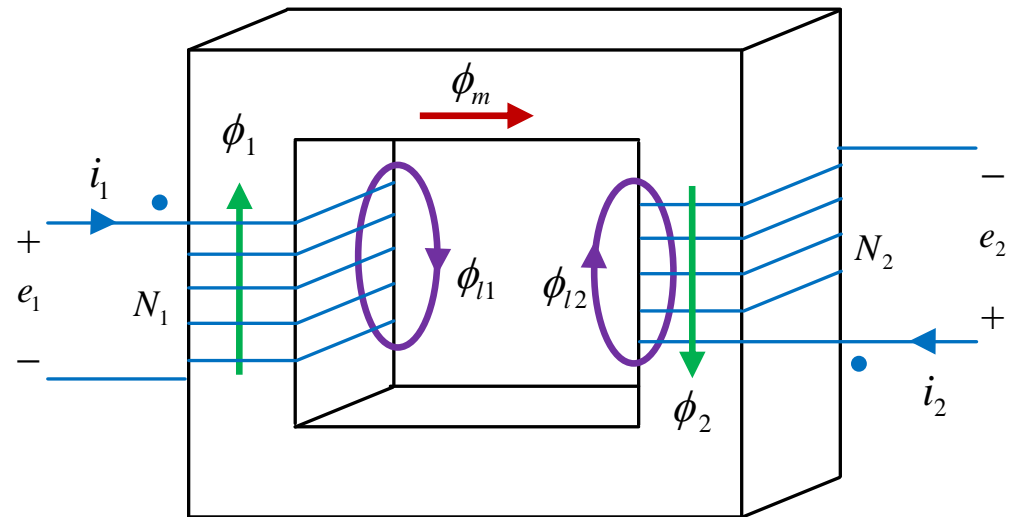
$$\begin{bmatrix} \lambda_1 \\ \lambda_2 \end{bmatrix} = \begin{bmatrix} L_{11} & L_{12} \\ L_{21} & L_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



where L_{11} and L_{22} are the self-inductances of the windings, and L_{12} and L_{21} are the mutual inductances between them.

Model of Two-Winding Transformers


1. Flux linkage equations

- The self-inductance of winding 1 is obtained as

$$L_{11} = \frac{\lambda_1 |_{i_2=0}}{i_1} = \underbrace{N_1^2 P_{l1}}_{L_{l1}} + \underbrace{N_1^2 P_m}_{L_{m1}}$$

- Likewise for winding 2

$$L_{22} = \frac{\lambda_2 |_{i_1=0}}{i_2} = \underbrace{N_2^2 P_{l2}}_{L_{l2}} + \underbrace{N_2^2 P_m}_{L_{m2}}$$

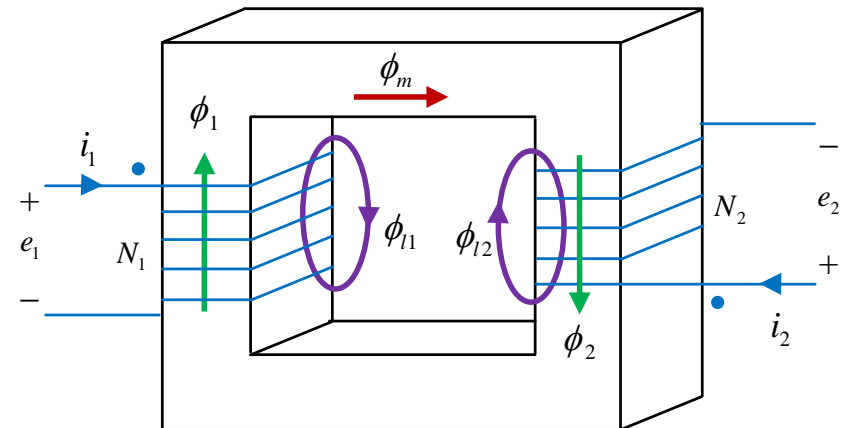

$$\frac{L_{m1}}{L_{m2}} = \left(\frac{N_1}{N_2} \right)^2$$

where L_{l1} and L_{l2} are the leakage inductances of the windings and L_{m1} and L_{m2} are the magnetizing inductances

Model of Two-Winding Transformers



1. Flux linkage equations

- The total mutual flux linked by winding 1 is expressed as

$$N_1 \phi_m = N_1 (\phi_{m1} + \phi_{m2}) = L_{m1} \left(i_1 + \frac{N_2}{N_1} i_2 \right) = L_{m1} (i_1 + i'_2) = L_{m1} i_{m1}$$

where i'_2 is the 2nd winding current referred to the 1st side,

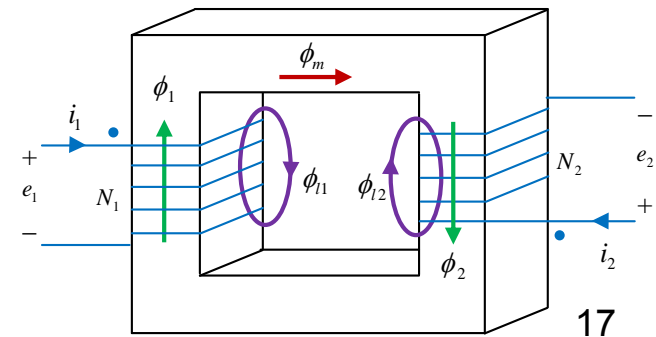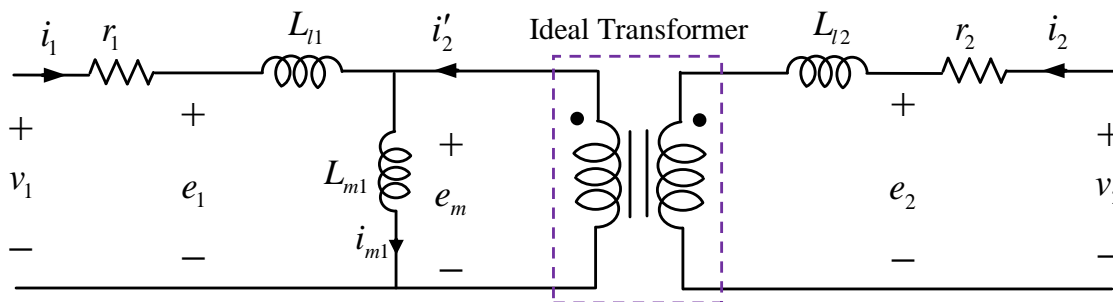$\phi_{m1} = N_1 i_1 P_m$ and $\phi_{m2} = N_2 i_2 P_m$ are the portions of the mutual flux magnetized by i_1 and i_2 respectively, and i_{m1} is the magnetizing current in the 1st side.




Model of Two-Winding Transformers

Review on the Inductances

Leakage inductance of the 1st winding

Leakage inductance of the 2nd winding

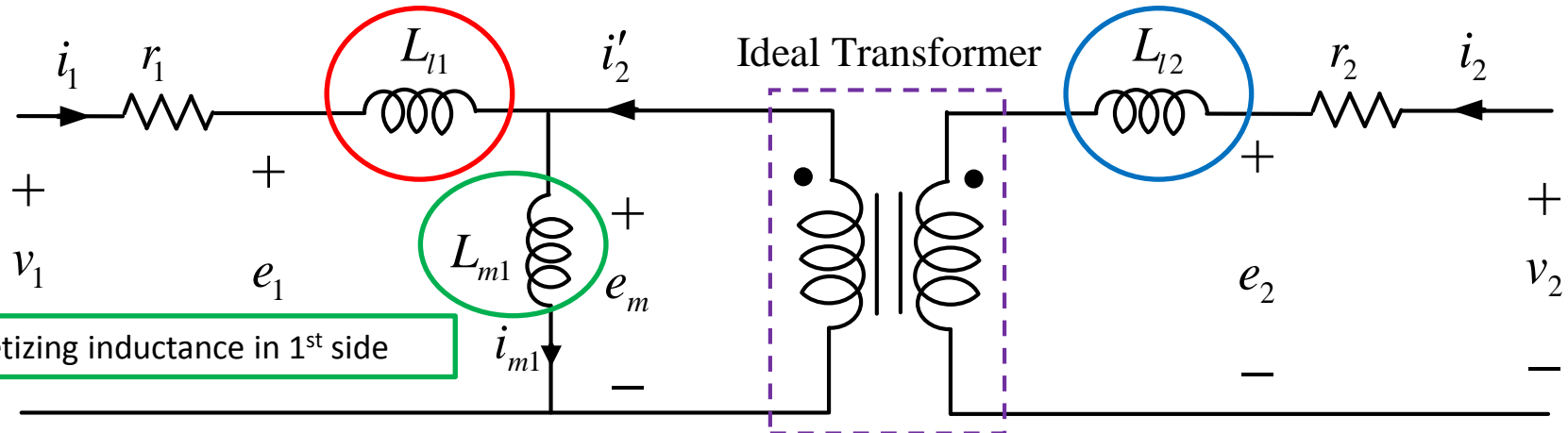

Magnetizing inductance in 1st side

Self-inductance of the 1st winding

Magnetizing inductance in 2nd side

$$L_{11} = L_{l1} + L_{m1}$$

$$L_{12} = \frac{N_2}{N_1} L_{m1}$$

$$L_{22} = L_{l2} + L_{m2}$$

$$L_{21} = \frac{N_1}{N_2} L_{m2}$$

$$L_{m2} = L_{m1} \left(\frac{N_2}{N_1} \right)^2$$

Self-inductance of the 2nd winding

Mutual-inductances

Model of Two-Winding Transformers


A Question

What would be the relation between L_{11} , L_{22} , L_{12} and L_{21} if the leakage inductances could be neglected?

With this assumption, write the following expression in terms of the magnetizing inductance in the first side.

$$\lambda_1 = L_{11} i_1 + L_{12} i_2$$

$$\lambda_2 = L_{21} i_1 + L_{22} i_2$$

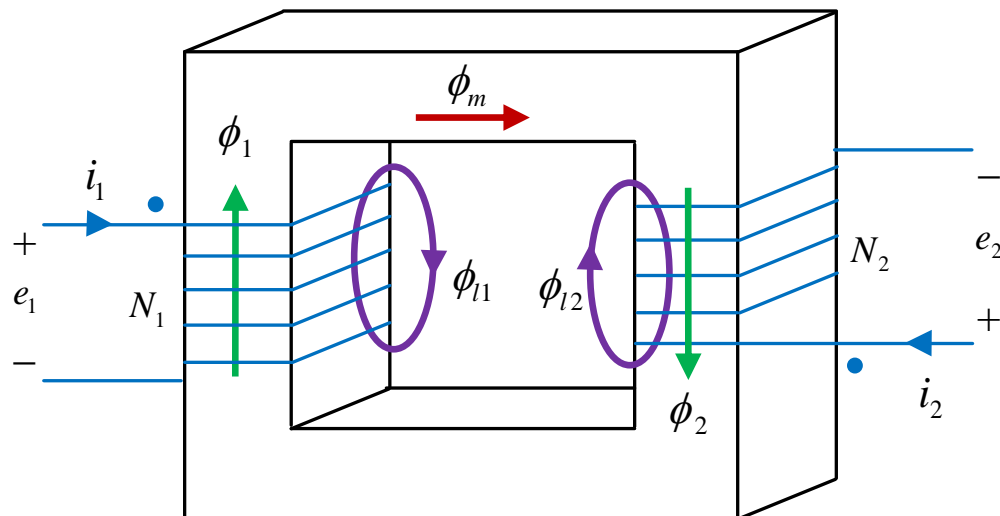



Model of Two-Winding Transformers

2. Voltage equations

- The terminal voltage can be expressed as the ohmic drop and the induced voltage for each winding

$$v_1 = r_1 i_1 + e_1$$

$$v_2 = r_2 i_2 + e_2$$

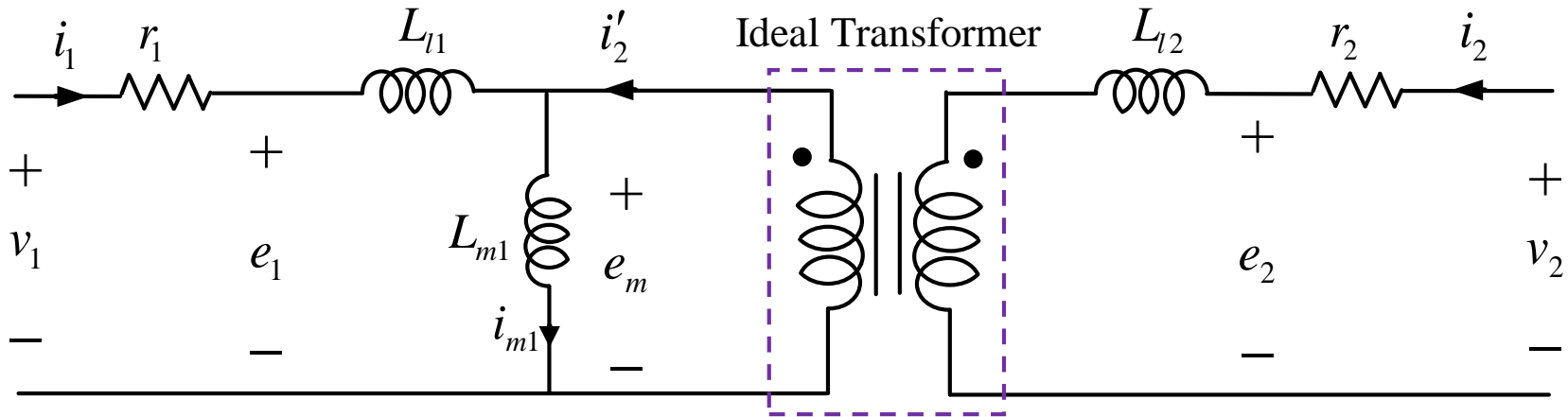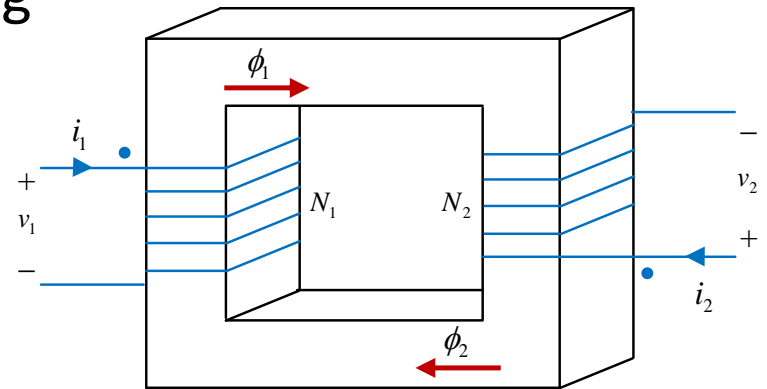



Model of Two-Winding Transformers

2. Voltage equations

- The induced voltage in winding 1 is equal to the time rate of change of the winding flux linkage:

$$e_1 = \frac{d\lambda_1}{dt} = L_{11} \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$

- Since $L_{11} = L_{l1} + L_{m1}$ and $L_{12} = \frac{N_2}{N_1} L_{m1}$ it can be written as

$$e_1 = L_{l1} \frac{di_1}{dt} + L_{m1} \frac{d}{dt} \left(i_1 + \frac{N_2}{N_1} i_2 \right) \quad \rightarrow \quad e_1 = L_{l1} \frac{di_1}{dt} + L_{m1} \frac{d}{dt} (i_1 + i'_2)$$

$$e_1 = L_{l1} \frac{di_1}{dt} + L_{m1} \frac{di_{m1}}{dt}$$



Model of Two-Winding Transformers

2. Voltage equations

- Similarly the induced voltage in winding 2 is obtained as:

$$e_2 = \frac{d\lambda_2}{dt} = L_{21} \frac{di_1}{dt} + L_{22} \frac{di_2}{dt}$$

- Since $L_{22} = L_{l2} + L_{m2}$ and $L_{21} = \frac{N_1}{N_2} L_{m2}$ it can be written as

$$e_2 = L_{l2} \frac{di_2}{dt} + L_{m2} \frac{d}{dt} \left(\frac{N_1}{N_2} i_1 + i_2 \right) \rightarrow e_2 = L_{l2} \frac{di_2}{dt} + L_{m2} \frac{d}{dt} (i'_1 + i_2)$$

$$\rightarrow e_2 = L_{l2} \frac{di_2}{dt} + L_{m2} \frac{di_{m2}}{dt}$$

Model of Two-Winding Transformers

2. Voltage equations

$$e_2 = L_{l2} \frac{di_2}{dt} + L_{m2} \frac{d}{dt} (i_1' + i_2)$$




$$e_2 = L_{l2} \frac{di_2}{dt} + L_{m2} \frac{di_{m2}}{dt}$$

- The voltage e_2 can be referred to winding 1

$$e_2' = L_{l2}' \frac{di_2'}{dt} + L_{m1} \frac{d}{dt} (i_1 + i_2')$$


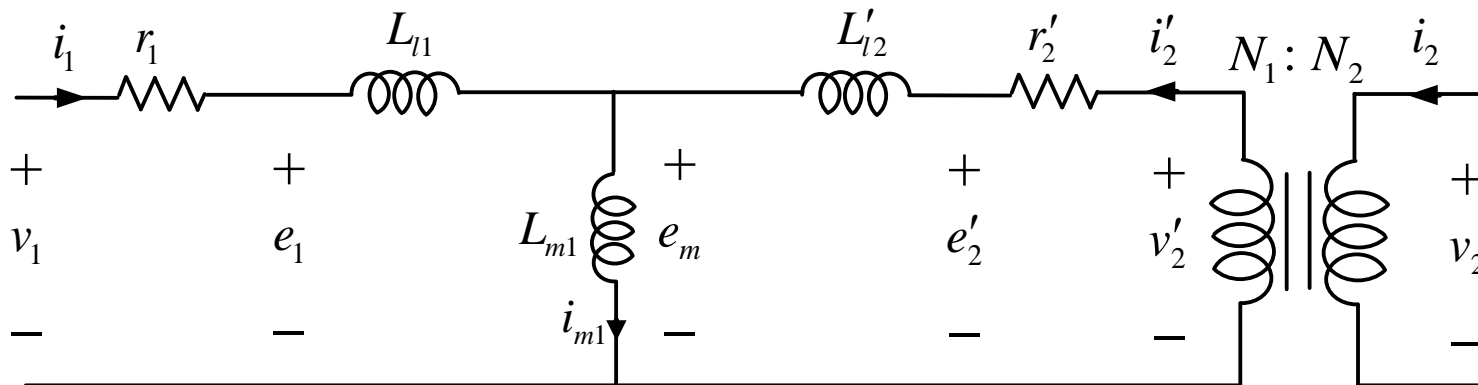
$$e_2' = L_{l2}' \frac{di_2'}{dt} + L_{m1} \frac{di_{m1}}{dt}$$



Model of Two-Winding Transformers

2. Voltage equations

- Therefore the voltage equations are

$$v_1 = r_1 i_1 + e_1$$




$$v_1 = r_1 i_1 + L_{l1} \frac{di_1}{dt} + L_{m1} \frac{di_{m1}}{dt}$$

$$i_{m1} = i_1 + i'_2$$

$$v'_2 = r'_2 i'_2 + e'_2$$


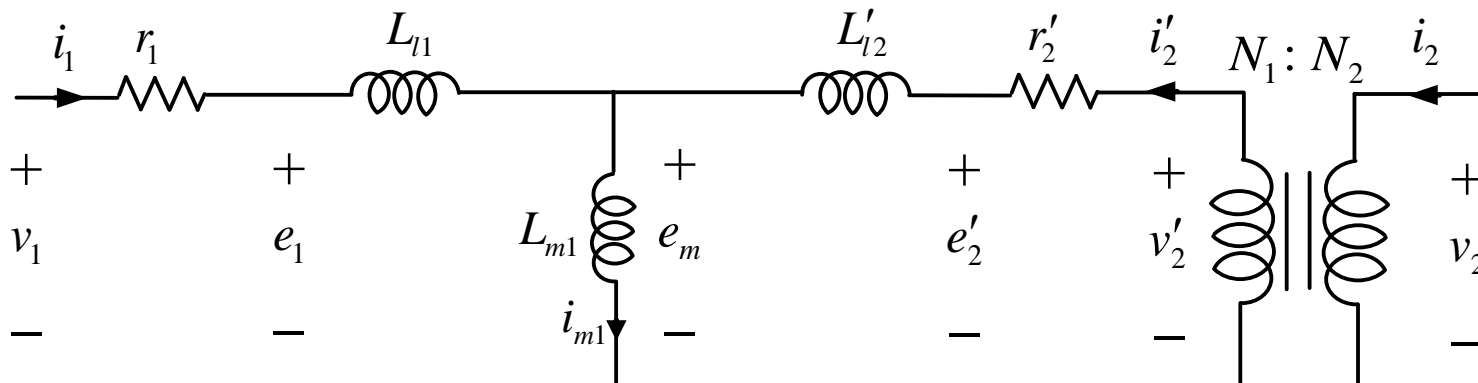
$$v'_2 = r'_2 i'_2 + L'_{l2} \frac{di'_2}{dt} + L_{m1} \frac{di_{m1}}{dt}$$



Model of Two-Winding Transformers

3. Equivalent circuit

$$v_1 = r_1 i_1 + L_{l1} \frac{di_1}{dt} + L_{m1} \frac{di_{m1}}{dt}$$

$$v'_2 = r'_2 i'_2 + L'_{l2} \frac{di'_2}{dt} + L_{m1} \frac{di_{m1}}{dt}$$


$$r'_2 = r_2 \left(\frac{N_1}{N_2} \right)^2$$

$$L'_{l2} = L_{l2} \left(\frac{N_1}{N_2} \right)^2$$

$$v'_2 = v_2 \frac{N_1}{N_2}$$

$$i'_2 = i_2 \frac{N_2}{N_1}$$

$$i_{m1} = i_1 + i'_2$$

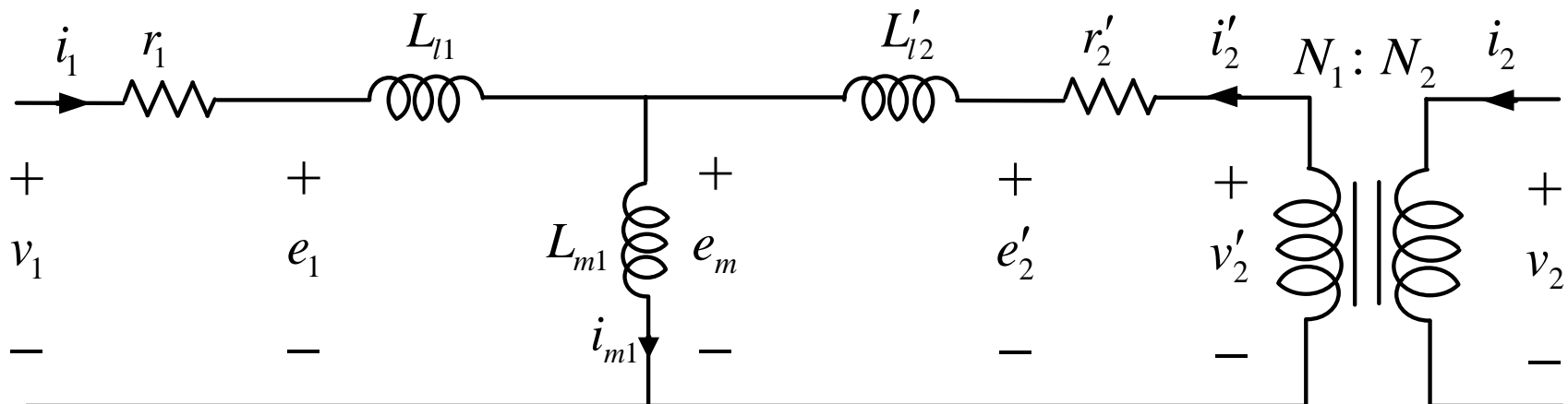



Simulation of Two-Winding Transformers

- There are several ways to simulate a two-winding transformer, e.g.:
- The inputs are the primary and secondary voltages, both in the primary side.


Inputs → v_1 v'_2

- The outputs are the primary and secondary current, both in the primary side.

Outputs → i_1 i'_2


- The states are the flux linkages of the primary and secondary windings.

States → λ_1 λ'_2

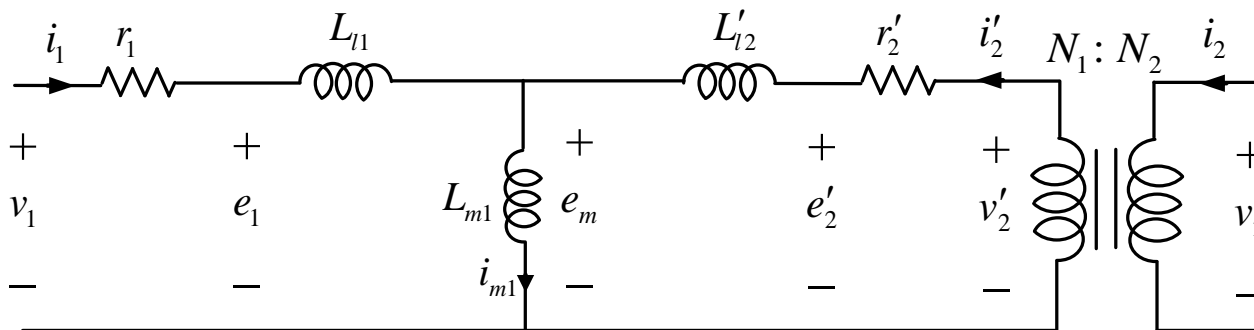

Simulation of Two-Winding Transformers

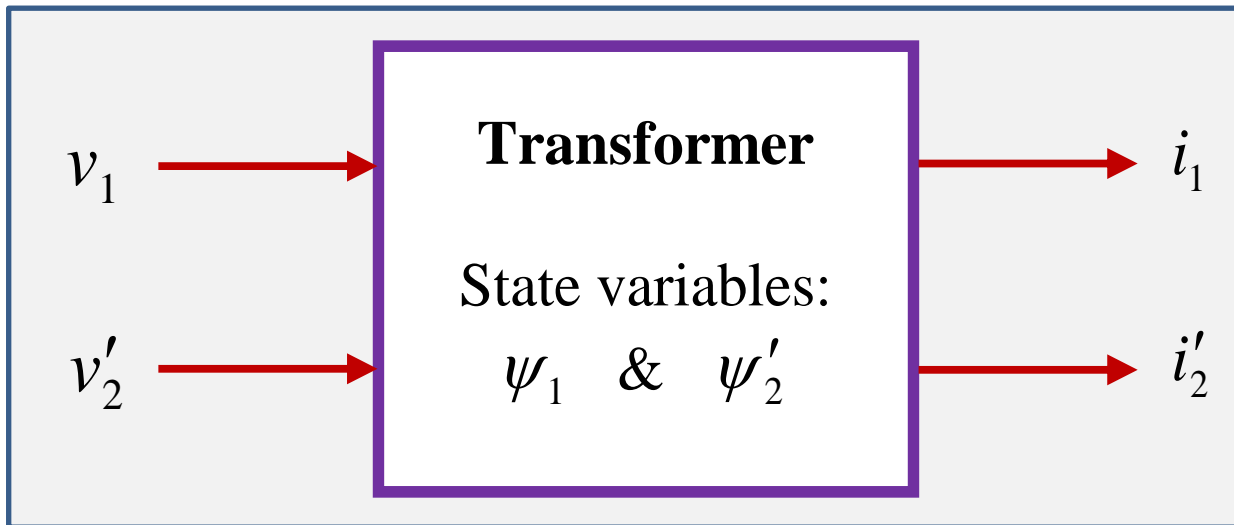
- It's possible to consider the **flux linkage per second** of the windings as state variables **States** \rightarrow ψ_1 ψ'_2



$$\psi_1 = \omega_b \lambda_1$$

$$\psi'_2 = \omega_b \lambda'_2$$

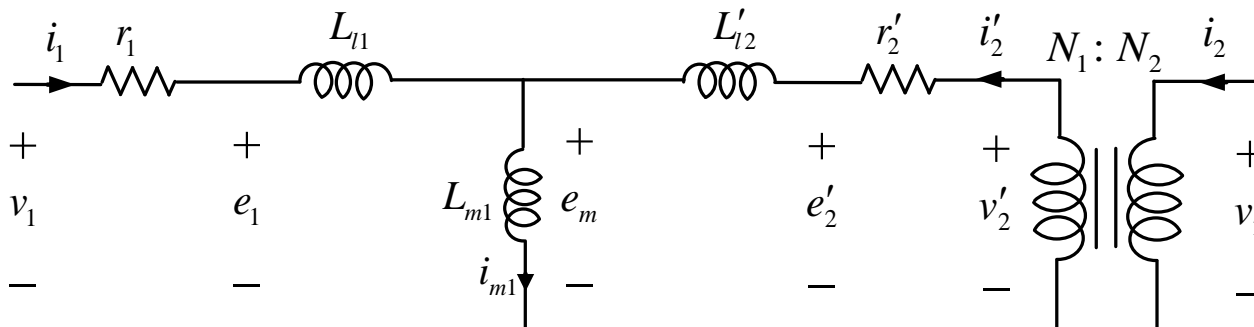where ω_b is the base frequency at which the reactances are computed.



Simulation of Two-Winding Transformers

- The **voltage equations** will be

$$v_1 = r_1 i_1 + \frac{1}{\omega_b} \frac{d\psi_1}{dt}$$

$$v'_2 = r'_2 i'_2 + \frac{1}{\omega_b} \frac{d\psi'_2}{dt}$$

- The **flux linkage per second** of the windings are

$$\psi_1 = \omega_b \lambda_1 = x_{l1} i_1 + \psi_m$$

$$\psi'_2 = \omega_b \lambda'_2 = x'_{l2} i'_2 + \psi_m$$

where ψ_m is the **magnetizing flux** referred to winding 1

$$\psi_m = \omega_b L_{m1} (i_1 + i'_2) = x_{m1} (i_1 + i'_2) = x_{m1} i_{m1}$$

and the **reactances** are defined as

$$x_{l1} = \omega_b L_{l1}$$

$$x'_{l2} = \omega_b L'_{l2}$$

$$x_{m1} = \omega_b L_{m1}$$

Simulation of Two-Winding Transformers

- The currents can be written in terms of the flux linkages

$$\psi_1 = x_{l1} i_1 + \psi_m \quad \Rightarrow \quad i_1 = \frac{\psi_1 - \psi_m}{x_{l1}} \quad \mathbf{1}$$

$$\psi'_2 = x'_{l2} i'_2 + \psi_m \quad \Rightarrow \quad i'_2 = \frac{\psi'_2 - \psi_m}{x'_{l2}} \quad \mathbf{2}$$

- Using the above two expressions and $\psi_m = x_{m1} (i_1 + i'_2)$ we have:

$$\frac{\psi_m}{x_{m1}} = \frac{\psi_1 - \psi_m}{x_{l1}} + \frac{\psi'_2 - \psi_m}{x'_{l2}} \quad \Rightarrow \quad \psi_m \left(\frac{1}{x_{m1}} + \frac{1}{x_{l1}} + \frac{1}{x'_{l2}} \right) = \frac{\psi_1}{x_{l1}} + \frac{\psi'_2}{x'_{l2}}$$



Simulation of Two-Winding Transformers

- It can be rewritten as

$$\psi_m \left(\frac{1}{x_{m1}} + \frac{1}{x_{l1}} + \frac{1}{x'_{l2}} \right) = \frac{\psi_1}{x_{l1}} + \frac{\psi'_2}{x'_{l2}} \quad \Rightarrow \quad \psi_m = x_M \left(\frac{\psi_1}{x_{l1}} + \frac{\psi'_2}{x'_{l2}} \right) \quad 3$$

where

$$\frac{1}{x_M} = \frac{1}{x_{m1}} + \frac{1}{x_{l1}} + \frac{1}{x'_{l2}}$$

- The above expression states the **magnetizing flux linkage per second** as a function of the **primary and secondary flux linkages per second**.




Simulation of Two-Winding Transformers

- The voltage equation of the primary side can be expressed as follows:

$$v_1 = r_1 i_1 + \frac{1}{\omega_b} \frac{d\psi_1}{dt}$$

$$i_1 = \frac{\psi_1 - \psi_m}{x_{l1}}$$

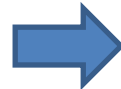

$$\psi_1 = \omega_b \int \left\{ v_1 - r_1 \left(\frac{\psi_1 - \psi_m}{x_{l1}} \right) \right\} dt$$

4


- Similarly for the secondary side we have:

$$\psi'_2 = \omega_b \int \left\{ v'_2 - r'_2 \left(\frac{\psi'_2 - \psi_m}{x'_{l2}} \right) \right\} dt$$

5


Simulation of Two-Winding Transformers

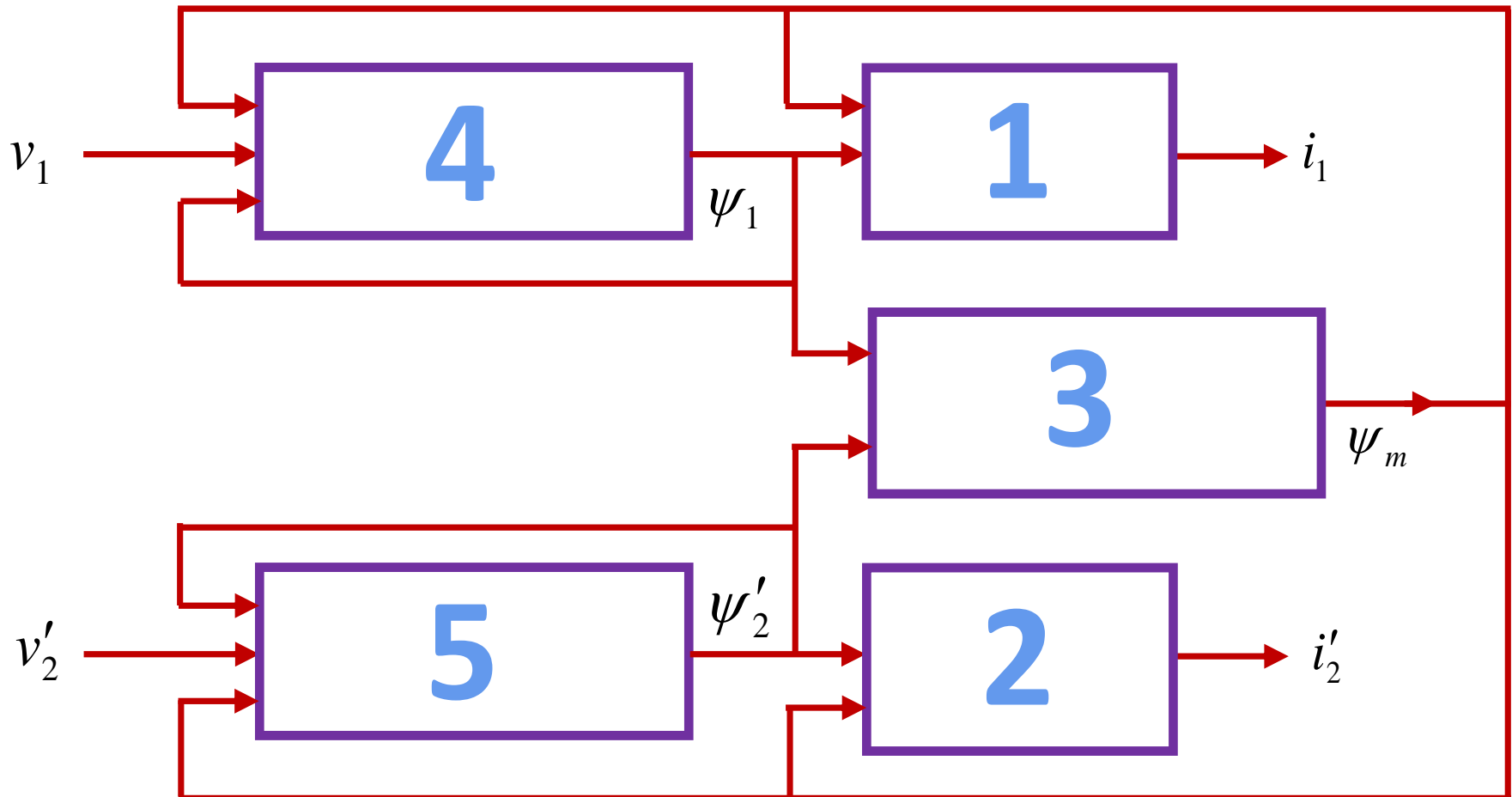- The block diagram of the simulation can be shown as



Simulation of Two-Winding Transformers

- The block diagram with equations

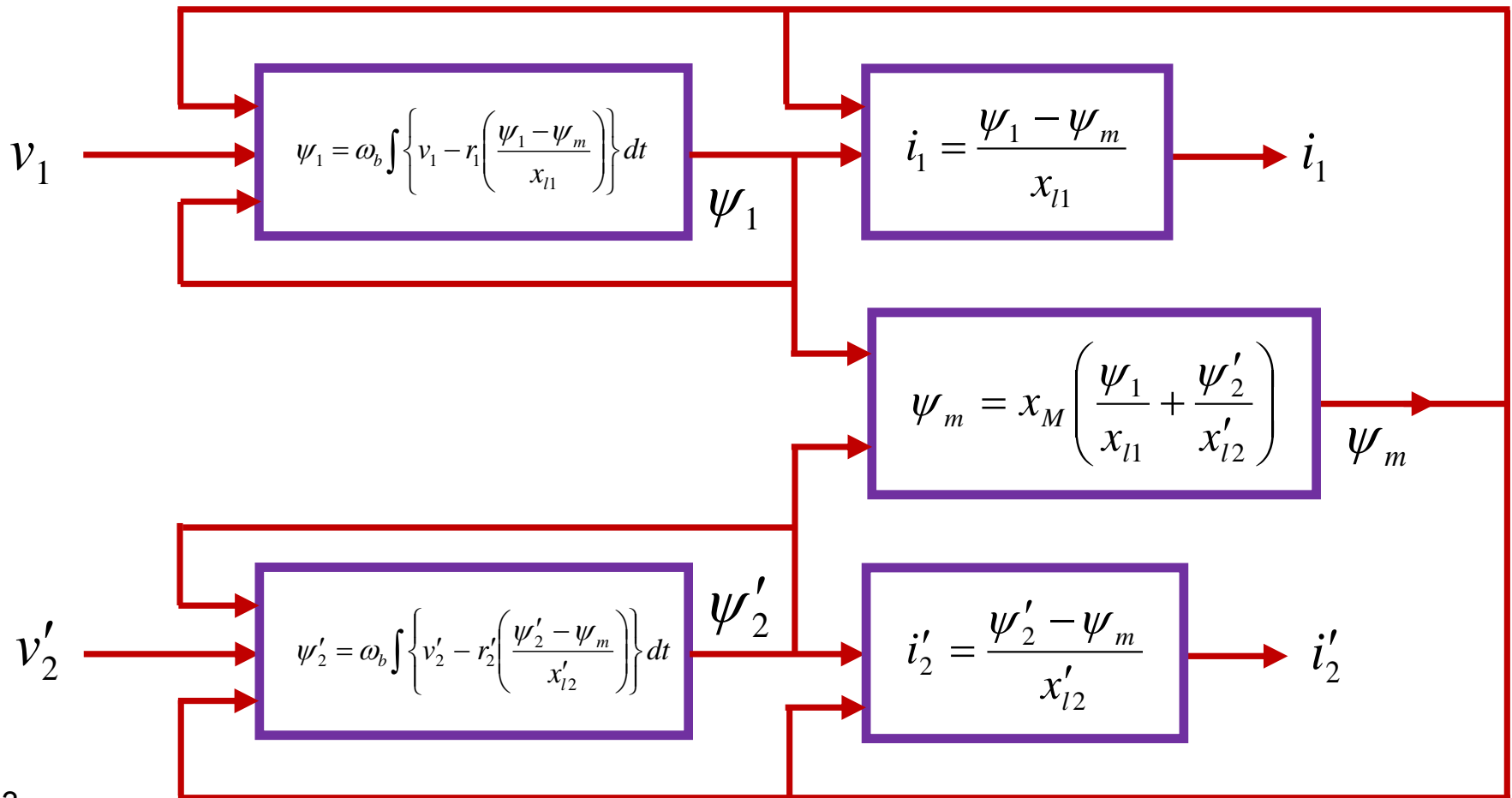



Simulation of Two-Winding Transformers

- In order to simulated the transformer, the following **parameters** are required:

r_1 : the primary winding resistance in Ω

r_2' : the secondary winding resistance referred to the primary

ω_b : the base frequency in rad/s


x_{l1} : the primary leakage reactance in Ω

x_{l2}' : the secondary leakage reactance referred to the primary

x_{m1} : the magnetizing reactance in the primary side in Ω


Simulation of Two-Winding Transformers

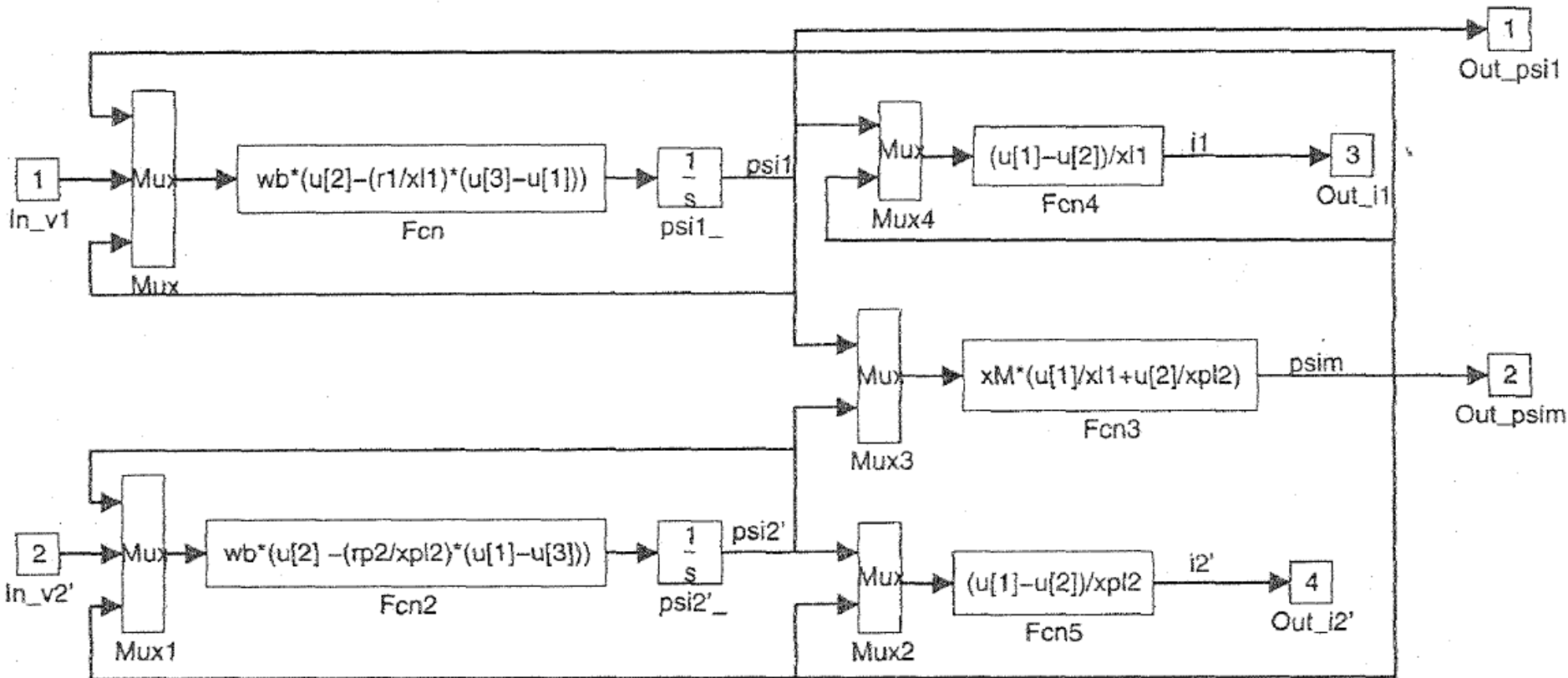- The simulation of the two-winding transformer in MATLAB/SIMULINK



Load Modelling

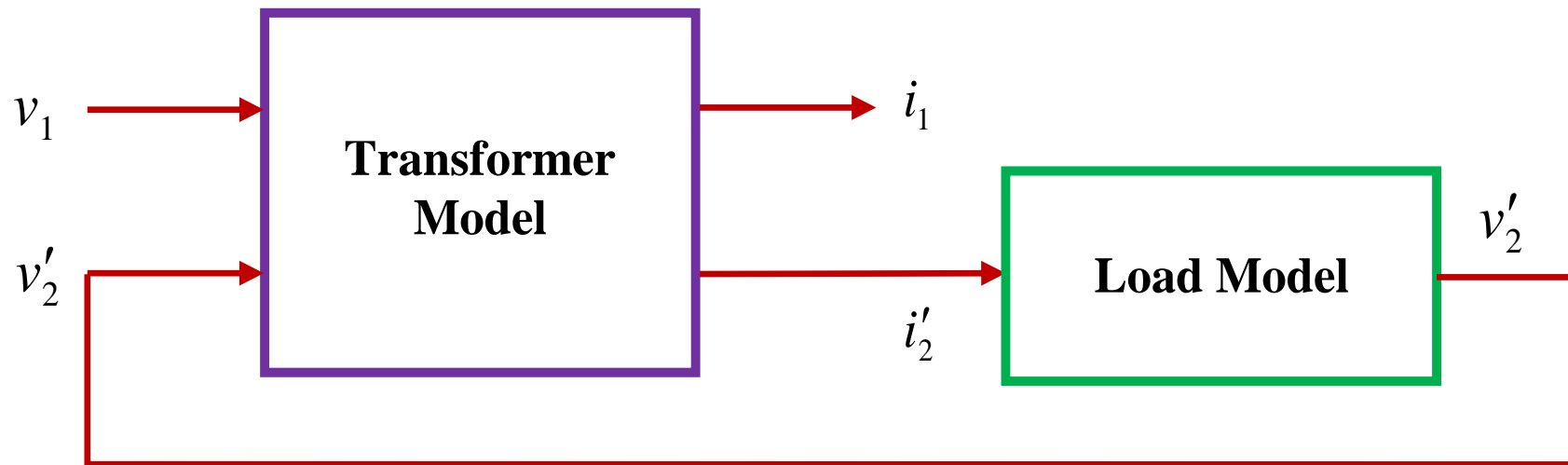- It is noted that the secondary terminal voltage is **not an explicit input** and depends on the load connected to this terminal.
- Therefore the **load** should be modelled in modular form.
- Then the load model is combined with the transformer model to obtain the overall response of the system:





Load Modelling

Two Special Cases

1. Short Circuit

$$v'_2 = 0$$

It's straightforward to implement the short-circuit condition by setting the secondary voltage to zero.

2. Open Circuit

$$i'_2 = 0$$

- It's not as easy as the short-circuit condition and the open-circuit secondary voltage is expressed as follows:

$$v'_{2oc} = \frac{1}{\omega_b} \frac{d\psi_m}{dt} = \frac{1}{\omega_b} \frac{x_{m1}}{x_{l1} + x_{m1}} \frac{d\psi_1}{dt} = \frac{x_{m1}}{x_{l1} + x_{m1}} (v_1 - r_1 i_1)$$

Why?

Load Modelling

Two Special Cases

2. Open Circuit

$$\psi'_2 = x'_{l2} i'_2 + \psi_m$$

$$i'_2 = 0 \rightarrow$$

$$\psi'_2 = \psi_m$$

$$v'_2 = r'_2 i'_2 + \frac{1}{\omega_b} \frac{d\psi'_2}{dt}$$

$$i'_2 = 0 \rightarrow$$

$$v'_2 = \frac{1}{\omega_b} \frac{d\psi'_2}{dt}$$

$$v'_2 = \frac{1}{\omega_b} \frac{d\psi_m}{dt}$$

$$\psi_m = x_{m1} (i_1 + i'_2)$$

$$i'_2 = 0 \rightarrow$$




$$\psi_m = x_{m1} i_1$$

$$\psi_1 = x_{l1} i_1 + \psi_m$$

$$\psi_m = \frac{x_{m1}}{x_{l1} + x_{m1}} \psi_1$$

Load Modelling

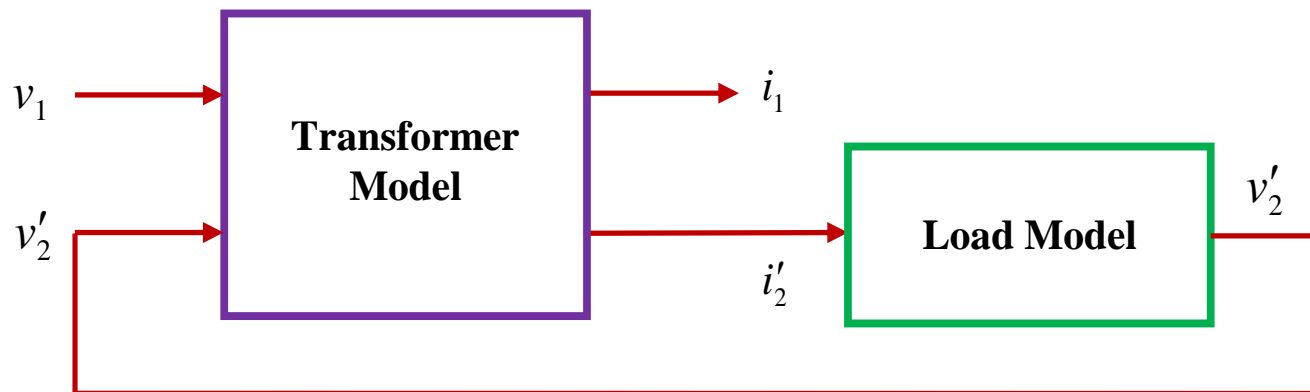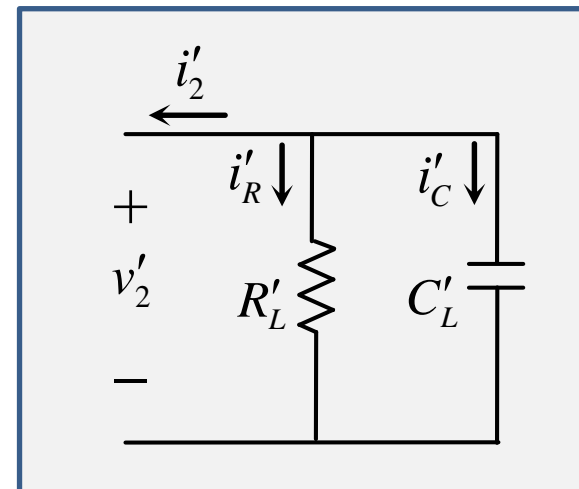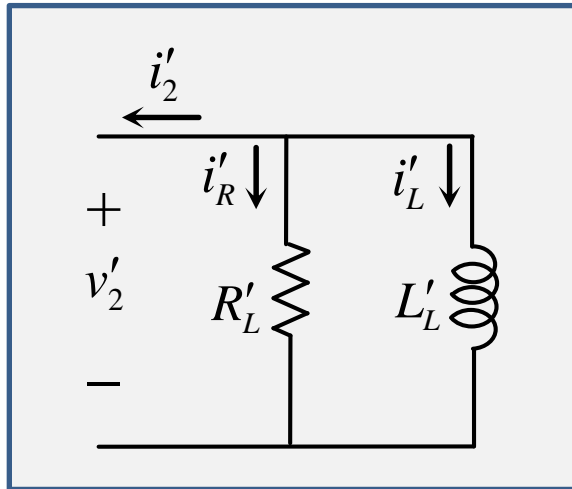- The load can be represented by an equivalent impedance or admittance in the form of either RL or RC circuit.



Load Modelling

- Consider a specified loading of S_L at the rated voltage of v_{2rated} .
- It can be translated into an equivalent circuit load admittance referred to the primary side:


$$(G'_L \pm jB'_L)^{-1} = \left(\frac{N_1}{N_2}\right)^2 \frac{v_{2rated}^2}{S_L^*}$$

Conductance

Susceptance

- For **lagging power factor** loads, the parallel **RL** circuit is used.

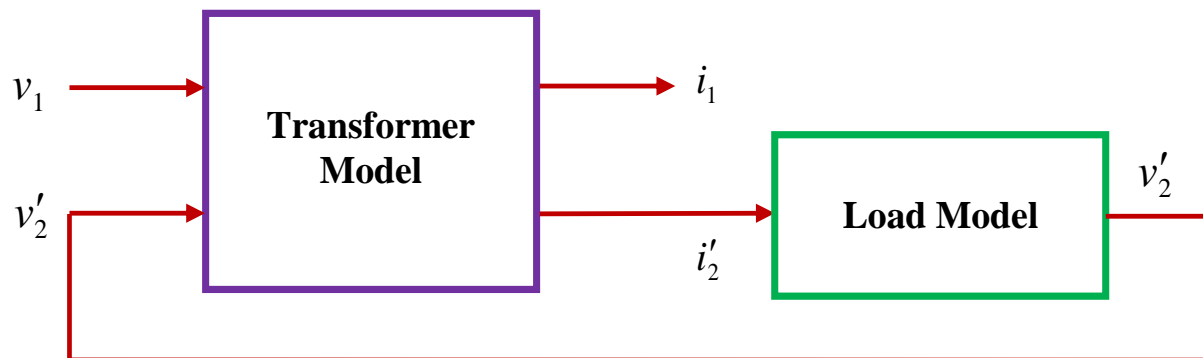
- For **leading power factor** loads, the parallel **RC** circuit is used.



Load Modelling

Lagging power factor loads (parallel RL circuit)
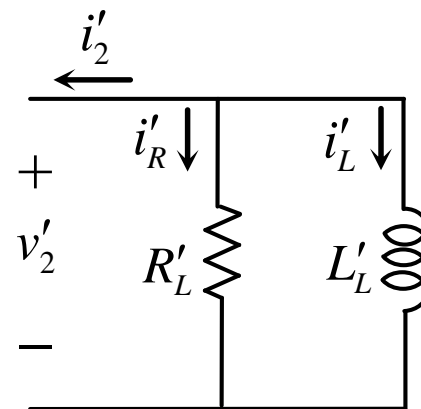
$$(G'_L - jB'_L)^{-1} = \left(\frac{N_1}{N_2} \right)^2 \frac{v_{2rated}^2}{S_L^*}$$



- Assume that the conductance and susceptance are calculated based on the complex power and rated voltage

$$v'_2 = R'_L i'_R = R'_L (-i'_2 - i'_L)$$


$$i'_L = \frac{1}{L'_L} \int v'_2 dt = \omega_b B'_L \int v'_2 dt$$

$$v'_2 = R'_L \left(-i'_2 - \omega_b B'_L \int v'_2 dt \right)$$

Load Modelling

Leading power factor loads (parallel RC circuit)
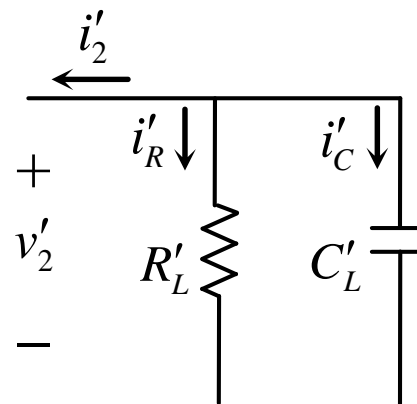
$$(G'_L + jB'_L)^{-1} = \left(\frac{N_1}{N_2} \right)^2 \frac{v_{2rated}^2}{S_L^*}$$



- Assume that the conductance and susceptance are calculated based on the complex power and rated voltage

$$i'_R = v'_2 / R'_L$$

$$v'_2 = \frac{1}{C'_L} \int i'_C dt = \frac{\omega_b}{B'_L} \int (-i'_2 - i'_R) dt$$

$$v'_2 = \frac{\omega_b}{B'_L} \int \left(-i'_2 - \frac{v'_2}{R'_L} \right) dt$$




Core Saturation Effects


- Core saturation mainly affects the value of the **magnetizing inductance** and, to a much lesser extent, the **leakage inductances**.
- Considering the core saturation effects on the **leakage inductances** is complex and **neglected** here.
- Therefore the core saturation effects on the **magnetizing inductance** are only **considered**.
- Core saturation behaviour can be determined from just the **open-circuit magnetization curve** of the transformer.

Core Saturation Effects

Saturation characteristics

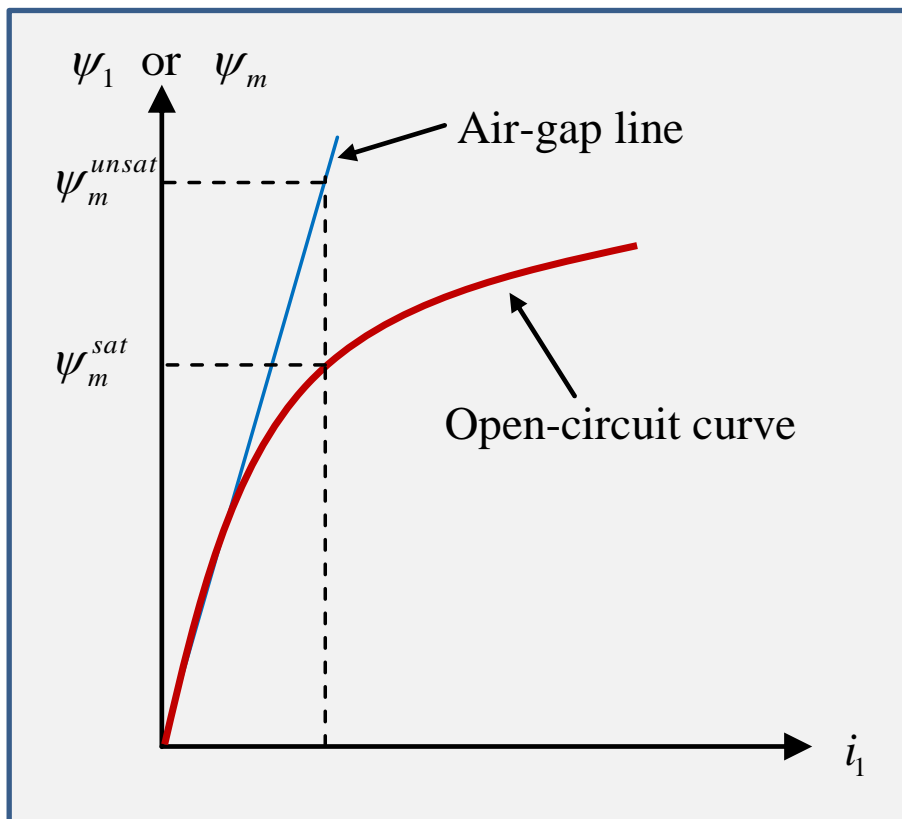

(a) Open-circuit curve

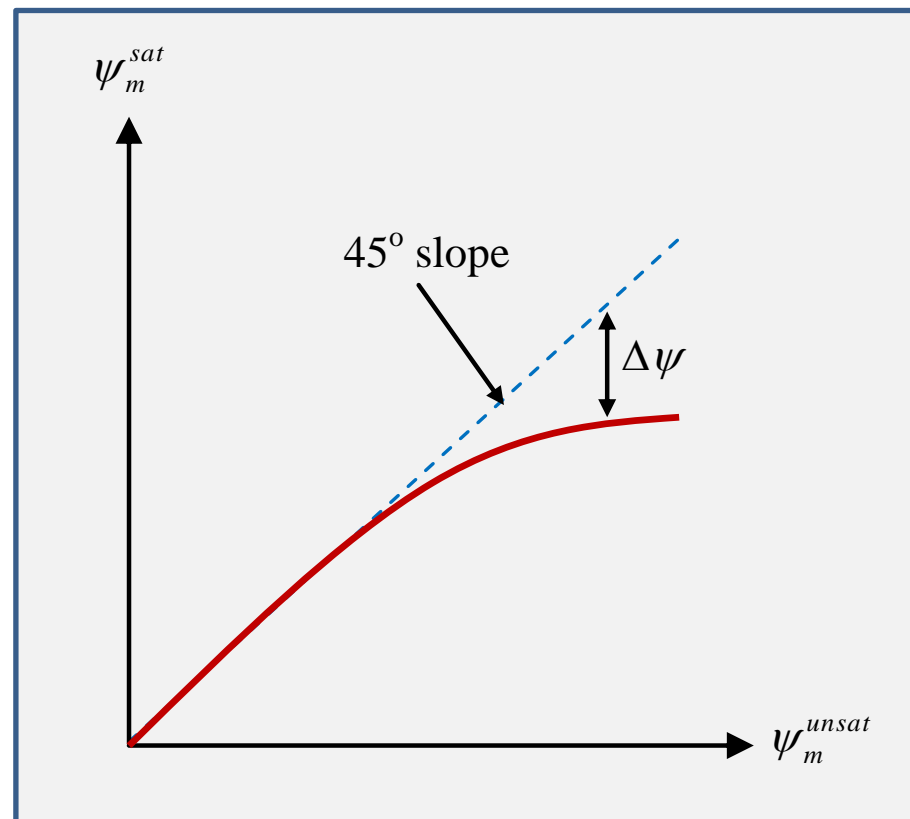

(b) Saturated vs. unsaturated flux linkage



Core Saturation Effects

Some of the methods to incorporate the core saturation effects in the dynamic simulation are:

1. Using the appropriate **saturated value of the magnetizing reactance** at each time step of the simulation.
2. Approximating the magnetizing current by some **analytic function** of the saturated flux linkage.
3. Using the **relation between saturated and unsaturated values** of the magnetizing flux linkage.

Core Saturation Effects

Method 1: Using the appropriate **saturated value of the magnetizing reactance** at each time step of the simulation.


- The saturated value of the magnetizing reactance x_{m1}^{sat} can be updated using the product of the unsaturated value of the magnetizing reactance x_{m1}^{unsat} times a saturation factor k_s .

$$x_{m1}^{sat} = k_s x_{m1}^{unsat}$$

- k_s is determined from the open-circuit curve:

$$k_s = \frac{\psi_m^{sat}}{\psi_m^{unsat}} \leq 1$$

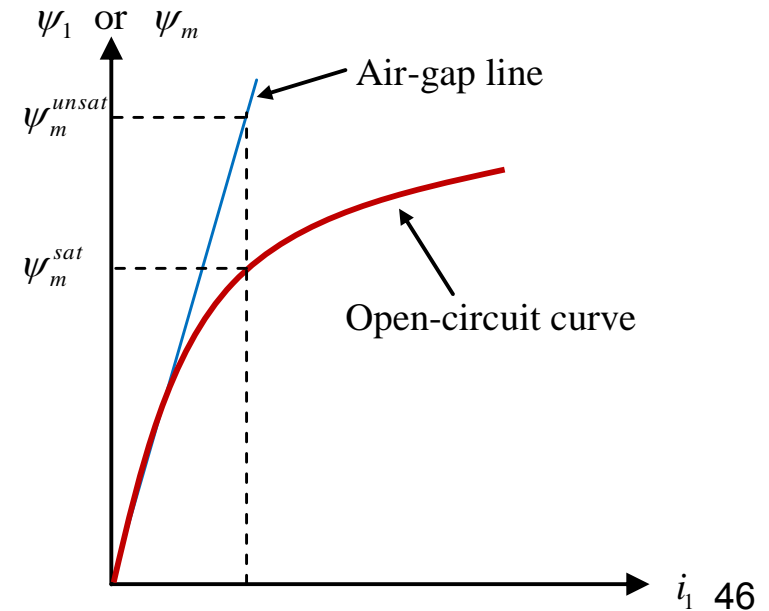- x_{m1}^{unsat} is a **constant** value.




Core Saturation Effects

Method 2: Approximating the magnetizing current by some **analytic function** of the saturated flux linkage.

$$i_m = f(\psi_m)$$

For more details see
pages 101-105 of Reference [1]

(Chee-Mun Ong)

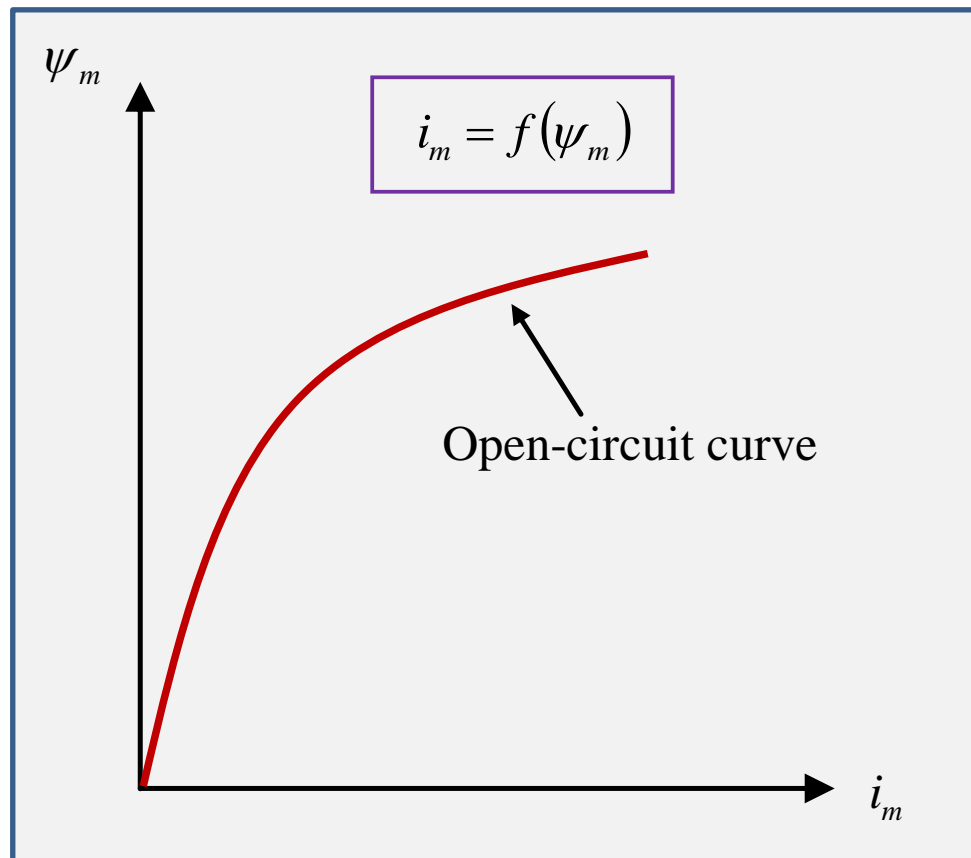

Core Saturation Effects

Method 3: Using the **relation between saturated and unsaturated values** of the magnetizing flux linkage.

$$\psi_m^{unsat} = x_{m1}^{unsat} (i_1 + i'_2)$$

$$i_1 = \frac{\psi_1 - \psi_m^{sat}}{x_{l1}}$$

$$i'_2 = \frac{\psi'_2 - \psi_m^{sat}}{x'_{l2}}$$

$$\psi_m^{unsat} = \psi_m^{sat} + \Delta\psi$$

$$\frac{\psi_m^{unsat}}{x_{m1}^{unsat}} = \frac{\psi_1 - \psi_m^{sat}}{x_{l1}} + \frac{\psi'_2 - \psi_m^{sat}}{x'_{l2}}$$

$$\psi_m^{sat} = x_M \left(\frac{\psi_1}{x_{l1}} + \frac{\psi'_2}{x'_{l2}} - \frac{\Delta\psi}{x_{m1}^{unsat}} \right)$$

where

$$\frac{1}{x_M} = \frac{1}{x_{m1}^{unsat}} + \frac{1}{x_{l1}} + \frac{1}{x'_{l2}}$$



Core Saturation Effects

Method 3: Using the **relation between saturated and unsaturated values** of the magnetizing flux linkage.

$$\psi_m^{sat} = x_M \left(\frac{\psi_1}{x_{l1}} + \frac{\psi_2'}{x_{l2}'} - \frac{\Delta\psi}{x_{m1}^{unsat}} \right)$$

where

$$\frac{1}{x_M} = \frac{1}{x_{m1}^{unsat}} + \frac{1}{x_{l1}} + \frac{1}{x_{l2}'}$$


- Comparing to the case with no saturation effects, the only additional term appeared in the above expression is:

$$\frac{\Delta\psi}{x_{m1}^{unsat}}$$

- Therefore similar model with minor modification is used.
- Only $\Delta\psi$ has to be obtained.

Core Saturation Effects

Block diagram of Method 3

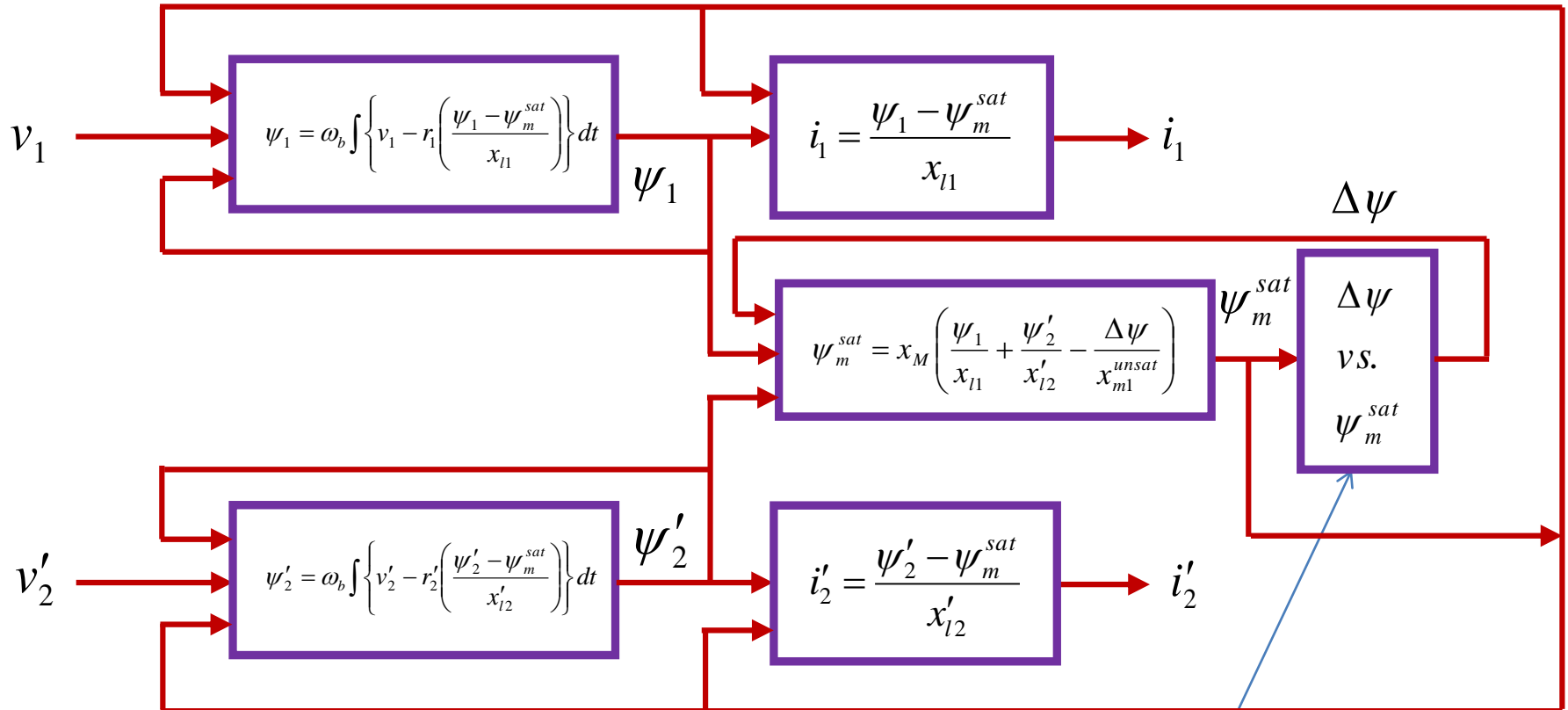

Now we need to find the way to represent the **saturation block**

Core Saturation Effects

Method 3: It is required to compute $\Delta\psi$ from ψ_m^{sat} .

The approaches to represent the **saturation block** are as follows:

- Using a **look-up table** and interpolation technique

<i>input</i>	ψ_m^{sat}	_____	_____	_____	_____
<i>output</i>	$\Delta\psi$	_____	_____	_____	_____

- Approximate **analytic functions**

- 2.1. Three-segment linear-exponential approximation

- 2.2. Three-segment linear approximation

Core Saturation Effects

2. Approximate **analytic functions**

2.1. Three-segment linear-exponential approximation

Linear region ($\psi_m^{sat} < B_1$):

$$\Delta\psi = 0$$


Knee region ($B_1 < \psi_m^{sat} < B_2$):

$$\Delta\psi = ae^{b(\psi_m^{sat} - B_1)}$$

Fully saturated region ($\psi_m^{sat} > B_2$):

$$\Delta\psi = A_2(\psi_m^{sat} - B_2) + \Delta\psi(B_2)$$

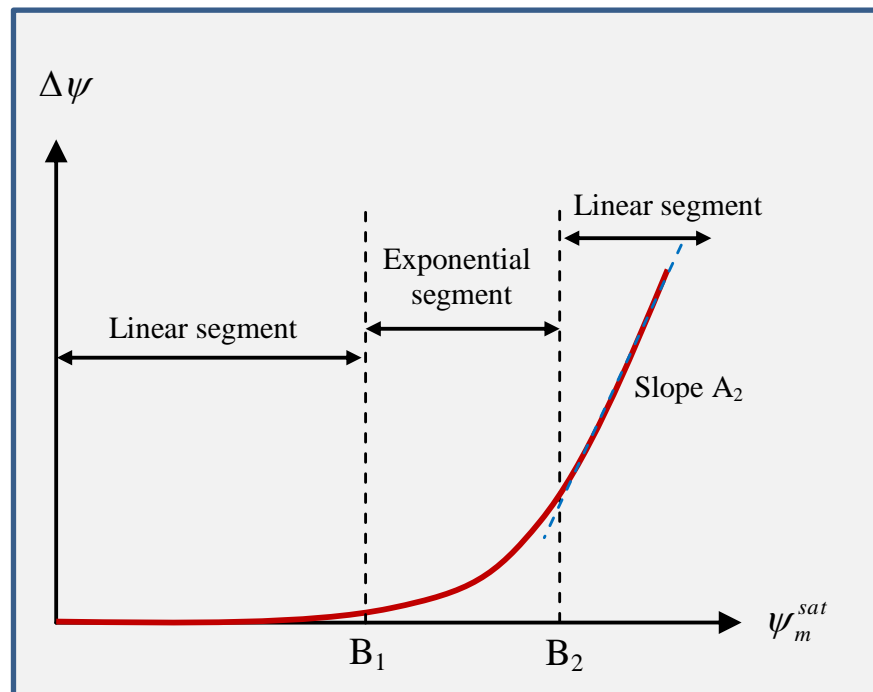where $\Delta\psi(B_2) = ae^{b(B_2 - B_1)}$



Core Saturation Effects

2. Approximate **analytic functions**


2.2. Three-segment linear approximation

$$\Delta \psi = A_1 (\psi_m^{sat} - B_1) + A_2 (\psi_m^{sat} - B_2)$$

where

$$A_1 = \begin{cases} \text{slope 1} & \text{if } \psi_m^{sat} > B_1 \\ 0 & \text{otherwise} \end{cases}$$

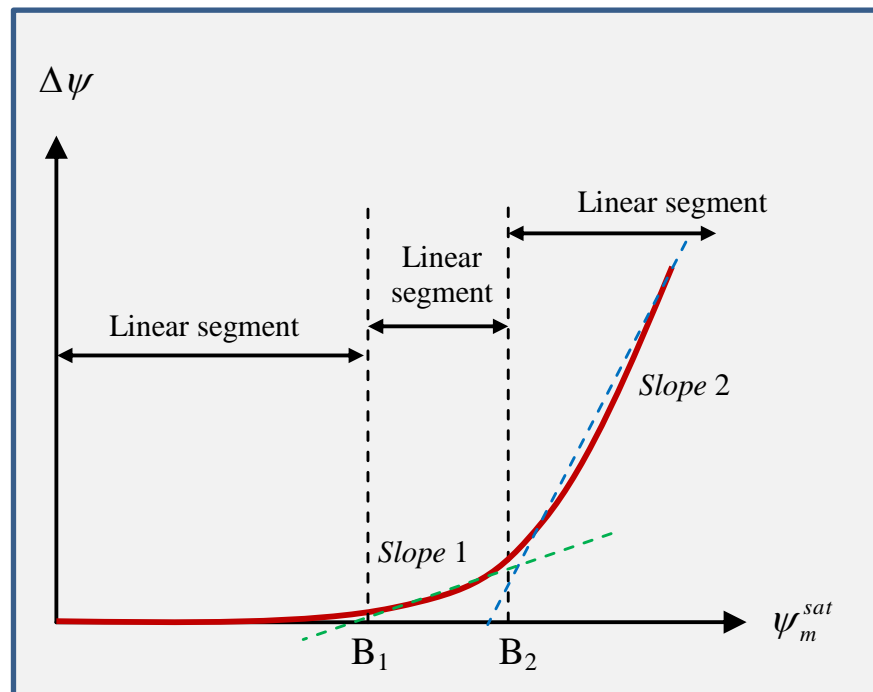
$$A_2 = \begin{cases} \text{slope 2} - \text{slope 1} & \text{if } \psi_m^{sat} > B_2 \\ 0 & \text{otherwise} \end{cases}$$



Core Saturation Effects

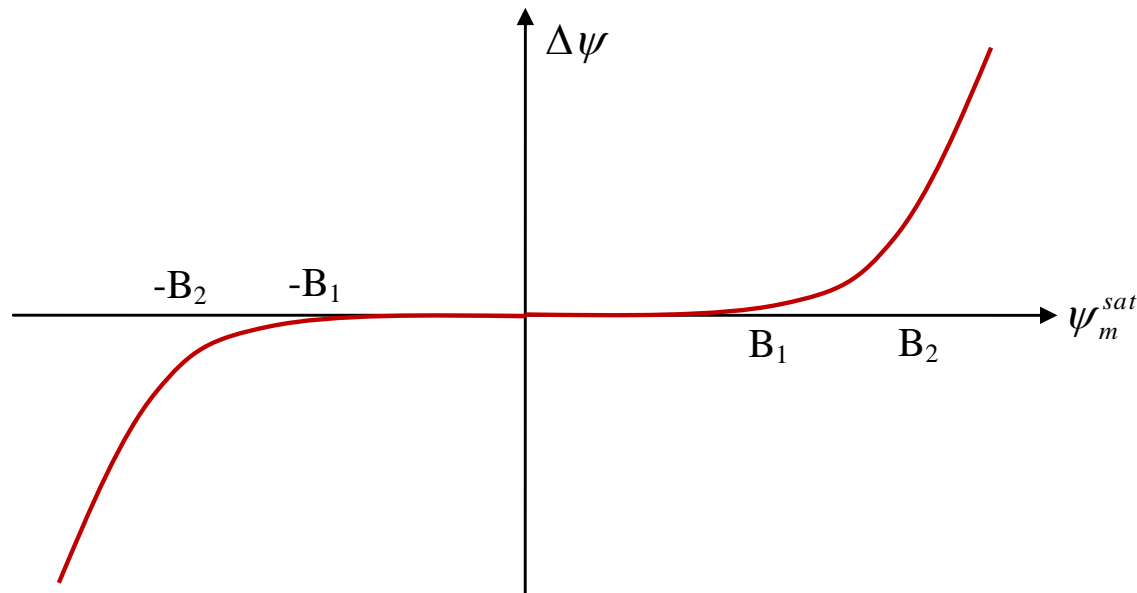
2. Approximate **analytic functions**

- Since ψ_m is alternating, saturation for negative ψ_m must be taken care of by a similar approximation in the third quadrant.
- In the third quadrant the slope of the linear approximation remains the same but the sign of B_1 and B_2 changes.



Core Saturation Effects

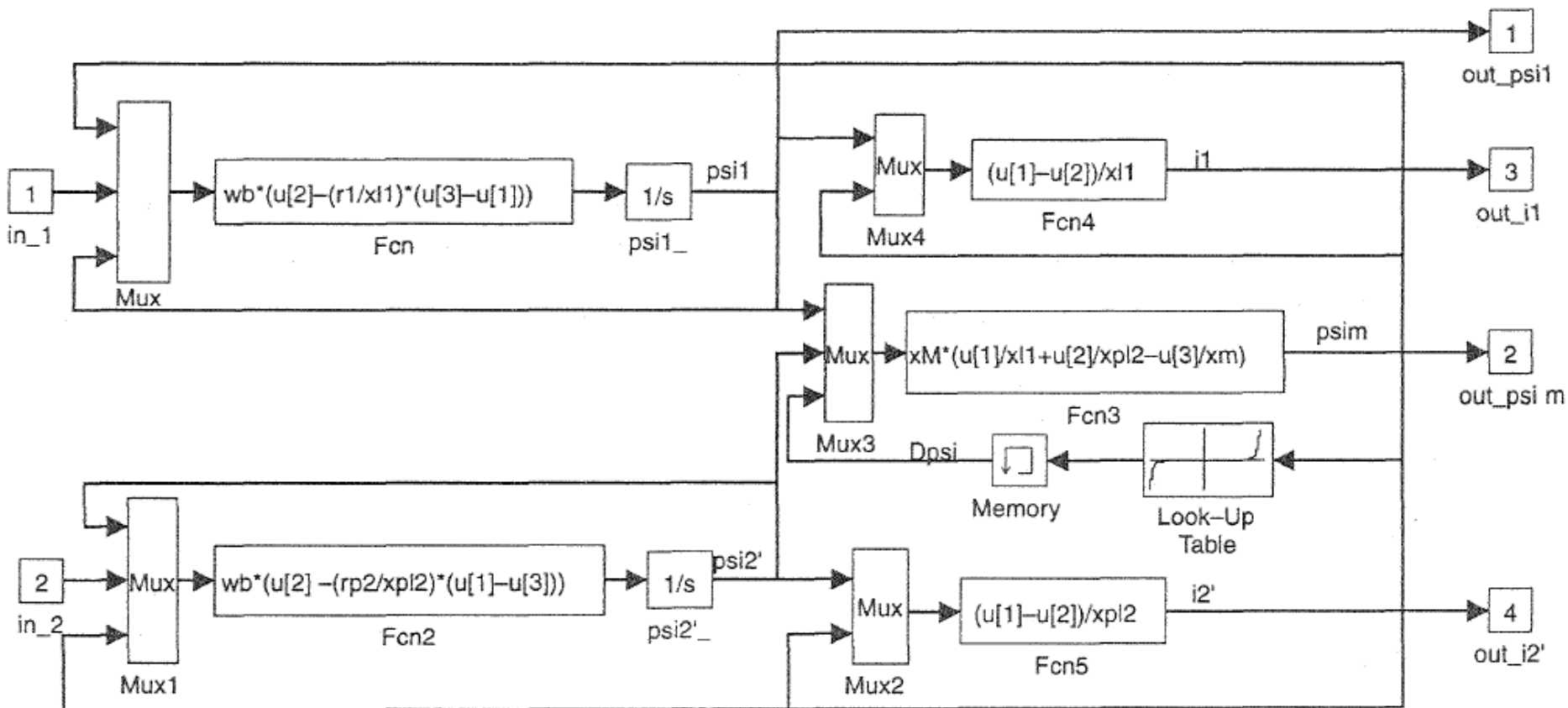Implementation in MATLAB/SIMULINK using Look-up Table







Three-Phase Connections

- The **generation, transmission** and **distribution** of AC electric power systems are mostly in **three-phase**.
- When the three-phase system is operating under **balanced conditions**, it can be represented by a **single phase equivalent circuit**.
- For **unbalanced** operating conditions, the three-phase system must be represented as it is.
- The operating characteristic of a 3-phase transformer depends on both **winding connections** and the **magnetic circuit of its core**.
- Here only the **winding connection** effects are considered and the effects of the magnetic circuit of the core (e.g. mutual effects of the primary windings when share a common core) are not considered.

Three-Phase Connections

Y-Y Connection

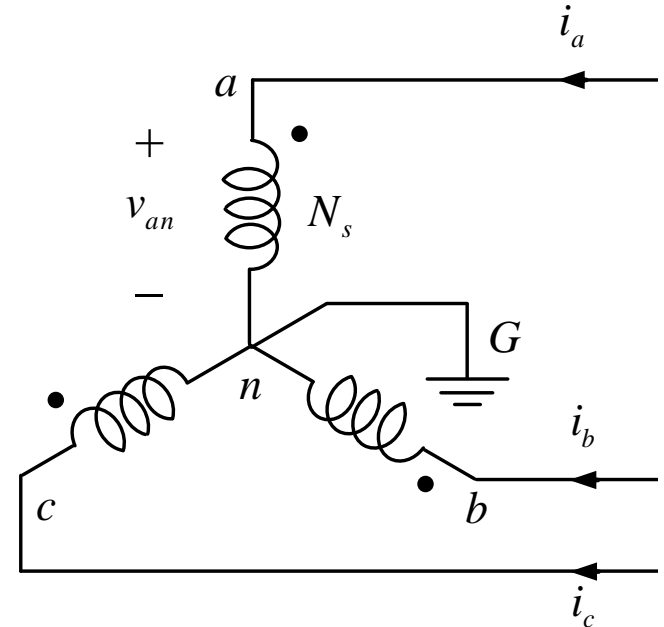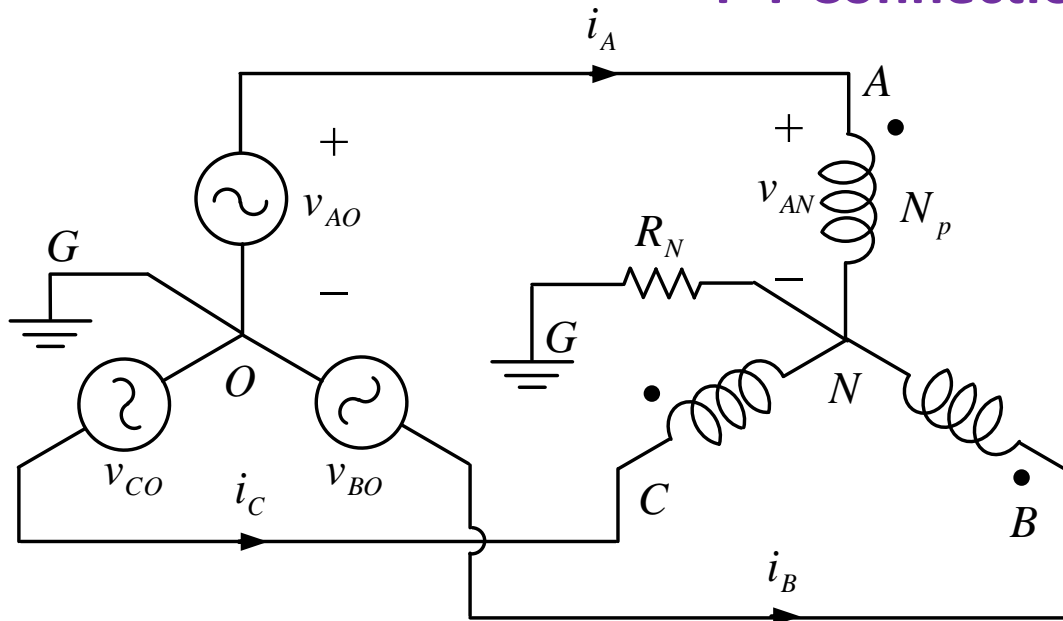

Terminal &
ground
point
Voltage
expressions

$$V_{AG} = V_{AO}$$

$$V_{BG} = V_{BO}$$

$$V_{CG} = V_{CO}$$

$$V_{AN} = V_{AG} - V_{NG}$$

$$V_{BN} = V_{BG} - V_{NG}$$


$$V_{CN} = V_{CG} - V_{NG}$$

$$V_{NG} = R_N (i_A + i_B + i_C)$$

Three-Phase Connections


Y-Y Connection

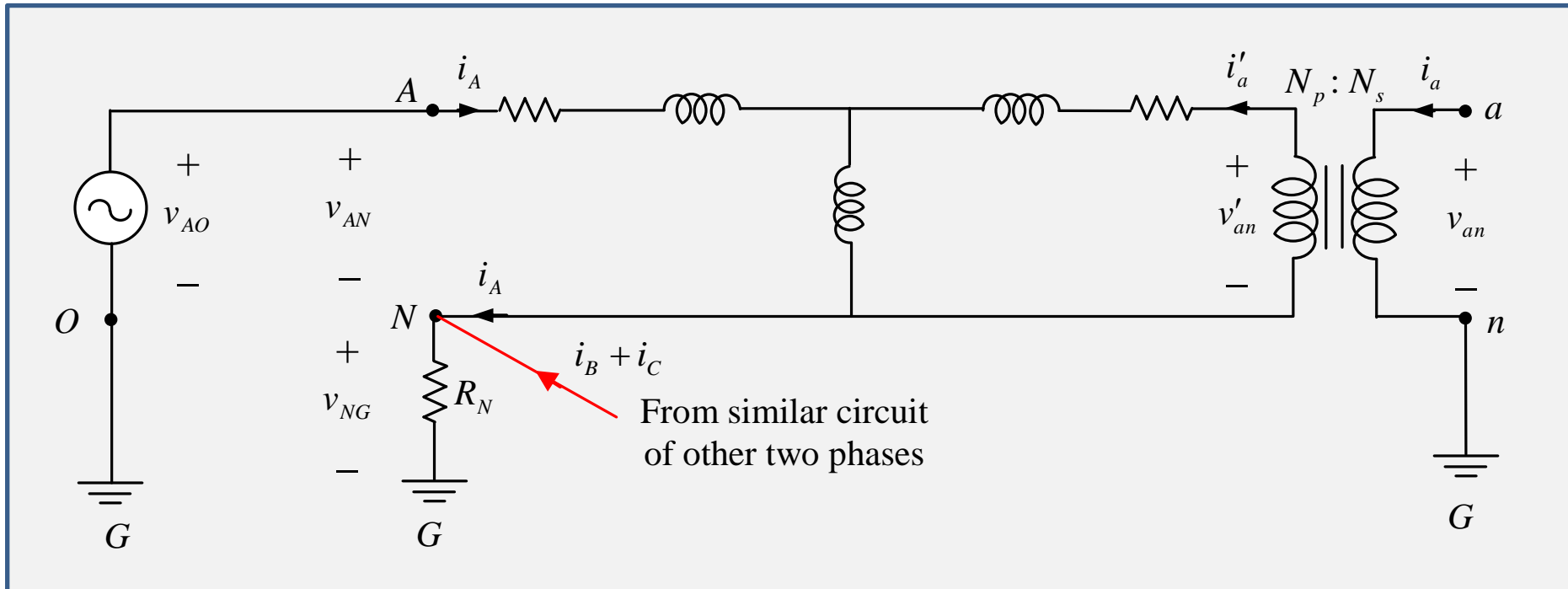Equivalent circuit representation of one transformer in detail



Three-Phase Connections

Y-Y Connection

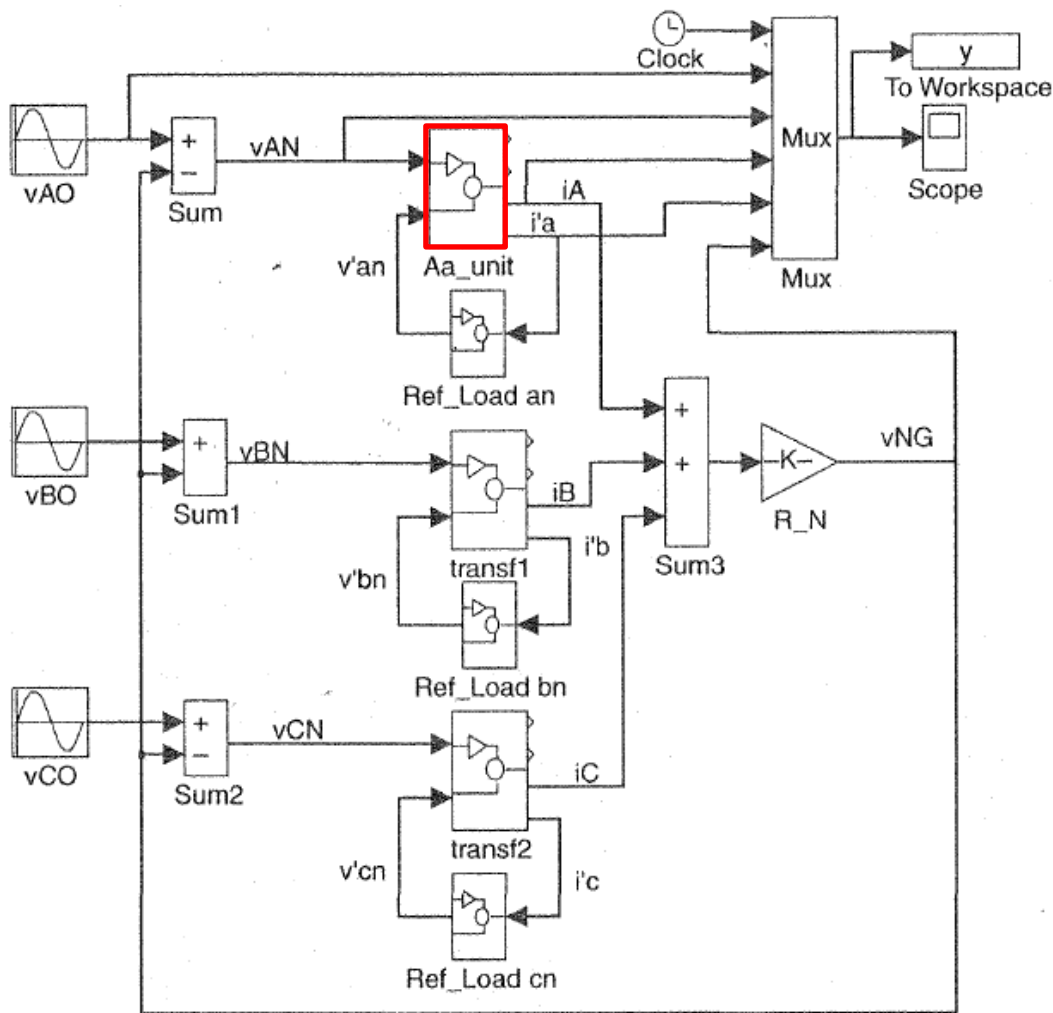

Simulation in MATLAB/SIMULINK

$$v_{AN} = v_{AG} - v_{NG}$$


$$v_{BN} = v_{BG} - v_{NG}$$

$$v_{CN} = v_{CG} - v_{NG}$$

$$v_{NG} = R_N (i_A + i_B + i_C)$$

Three-Phase Connections




Y-Y Connection Inside the Aa_unit

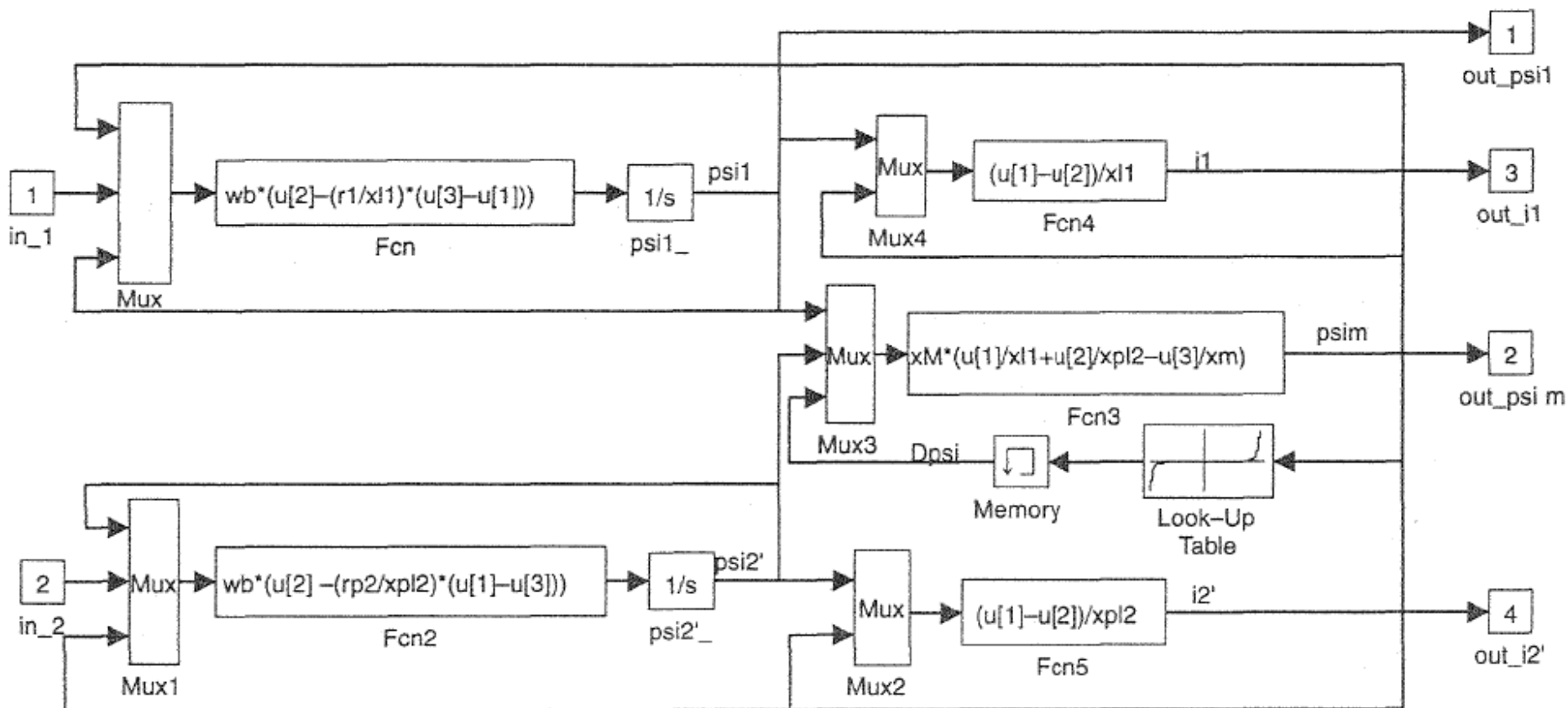

Three-Phase Connections



Y-Y Connection

Inside the Ref_Load an

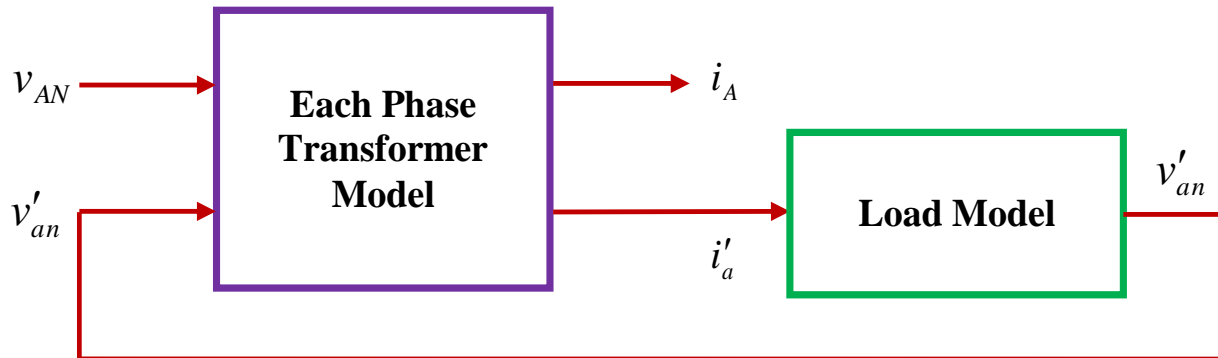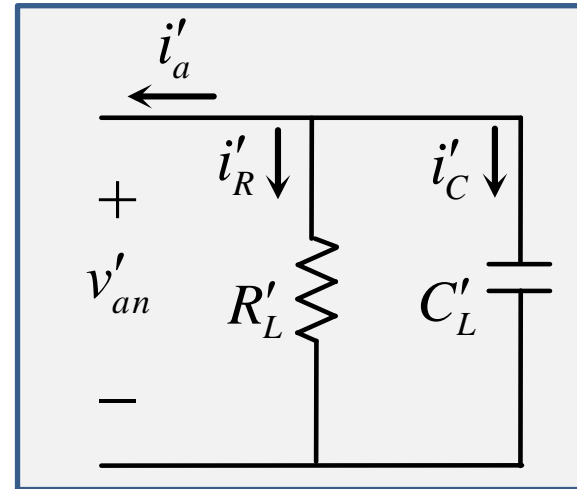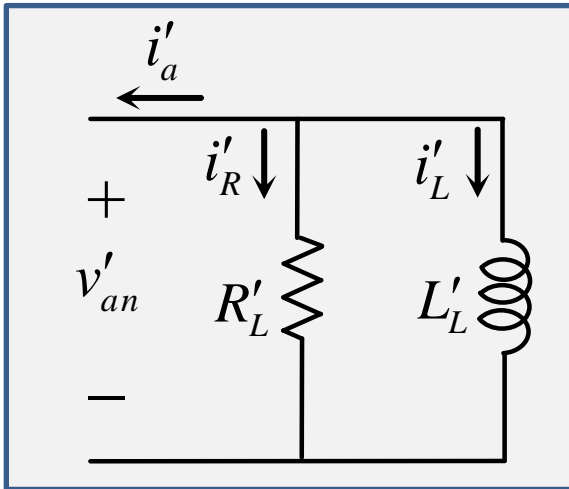

Three-Phase Connections

Δ-Y Connection

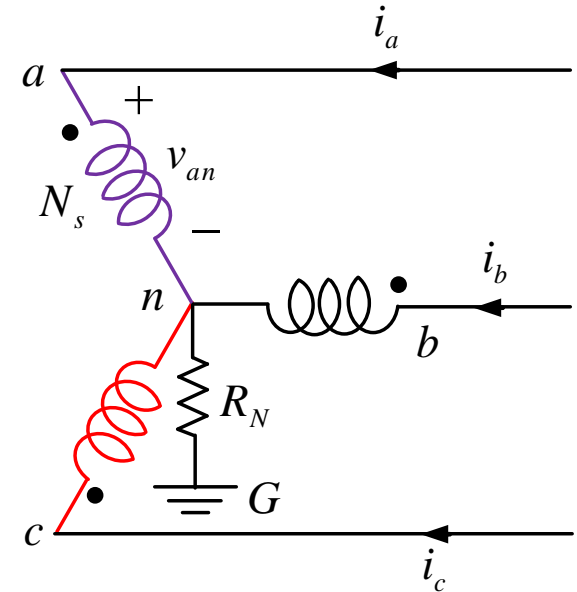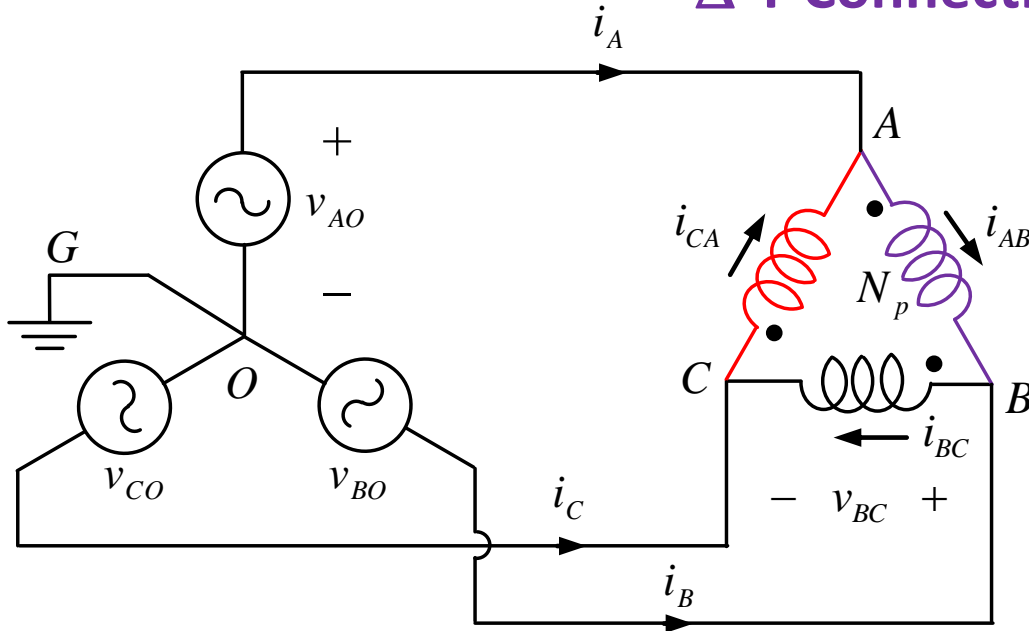

Voltage & current expressions

$$V_{AB} = V_{AO} - V_{BO}$$

$$V_{BC} = V_{BO} - V_{CO}$$

$$V_{CA} = V_{CO} - V_{AO}$$

$$i_A = i_{AB} - i_{CA}$$


$$i_B = i_{BC} - i_{AB}$$

$$i_C = i_{CA} - i_{BC}$$

Three-Phase Connections


Δ -Y Connection

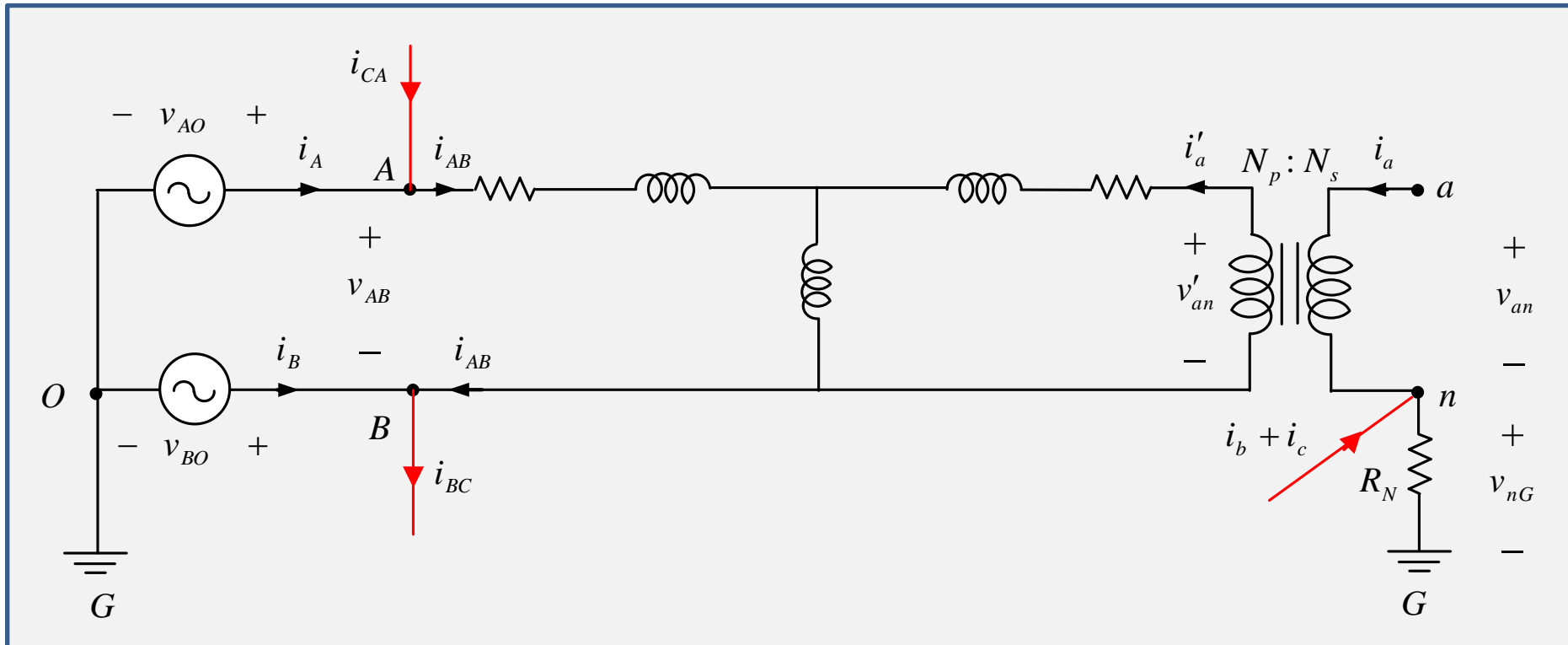Equivalent circuit representation of one transformer in detail



Three-Phase Connections

Δ -Y Connection

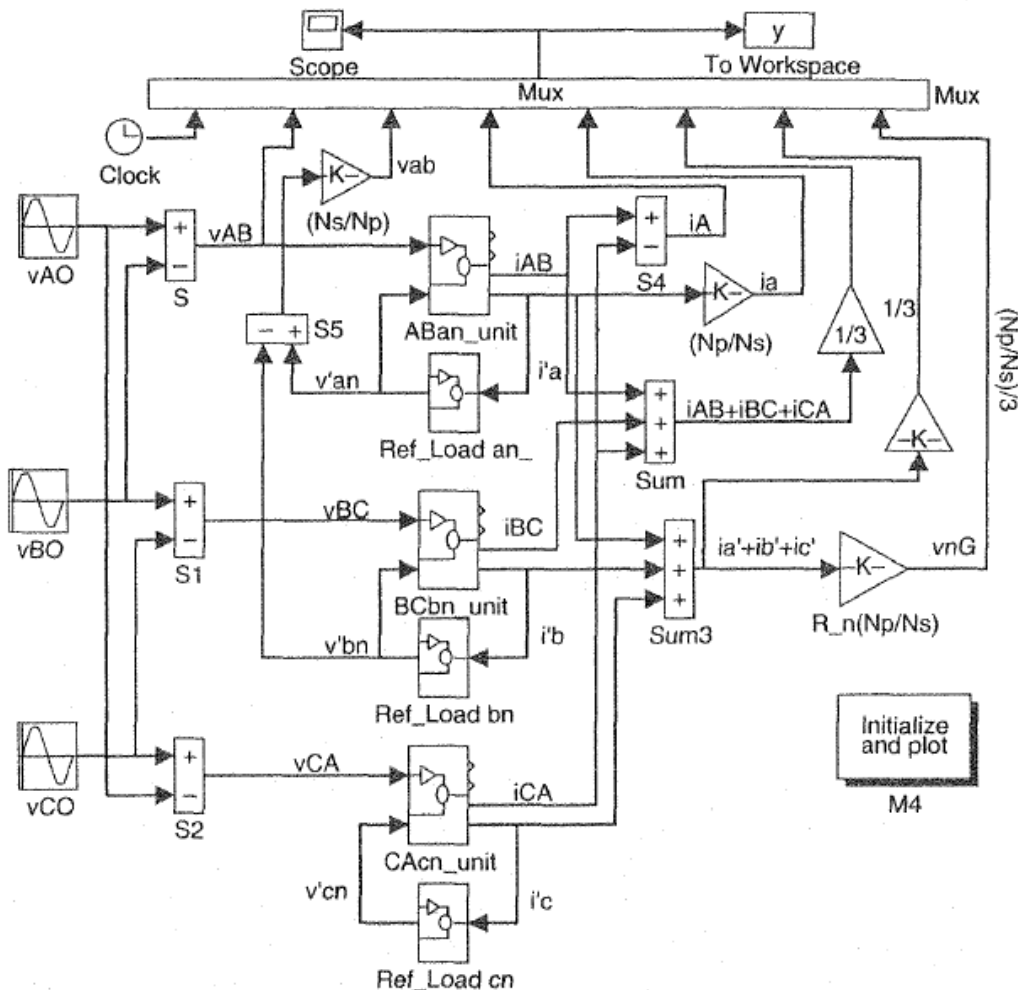

Simulation in MATLAB/SIMULINK

$$V_{AB} = V_{AO} - V_{BO}$$

$$V_{BC} = V_{BO} - V_{CO}$$

$$V_{CA} = V_{CO} - V_{AO}$$

$$i_A = i_{AB} - i_{CA}$$

$$i_B = i_{BC} - i_{AB}$$

$$i_C = i_{CA} - i_{BC}$$