
*In The Name of God The Most
Compassionate, The Most Merciful*



Electric Machines II





Table of Contents

1. Single-Phase Transformers

2. Principle of Alternating Current (AC) Machines

3. Three-Phase Induction (Asynchronous) Machines

Chapter 3

Three-Phase Induction (Asynchronous) Machines

3.1. Structure of Induction Machines

3.2. Basic Notions of Induction Machines

3.3. Different Modes of Induction Machines



3.4. Equivalent Circuits of Induction Motors

3.5. No-Load and Locked Rotor Tests

Not Included

3.6. Power and Torque in 3-Phase Induction Motors



Structure of Induction Machines

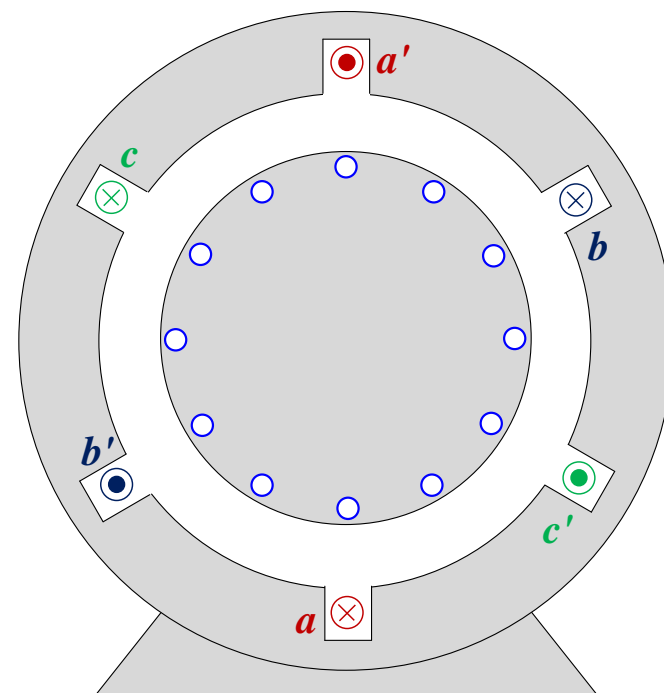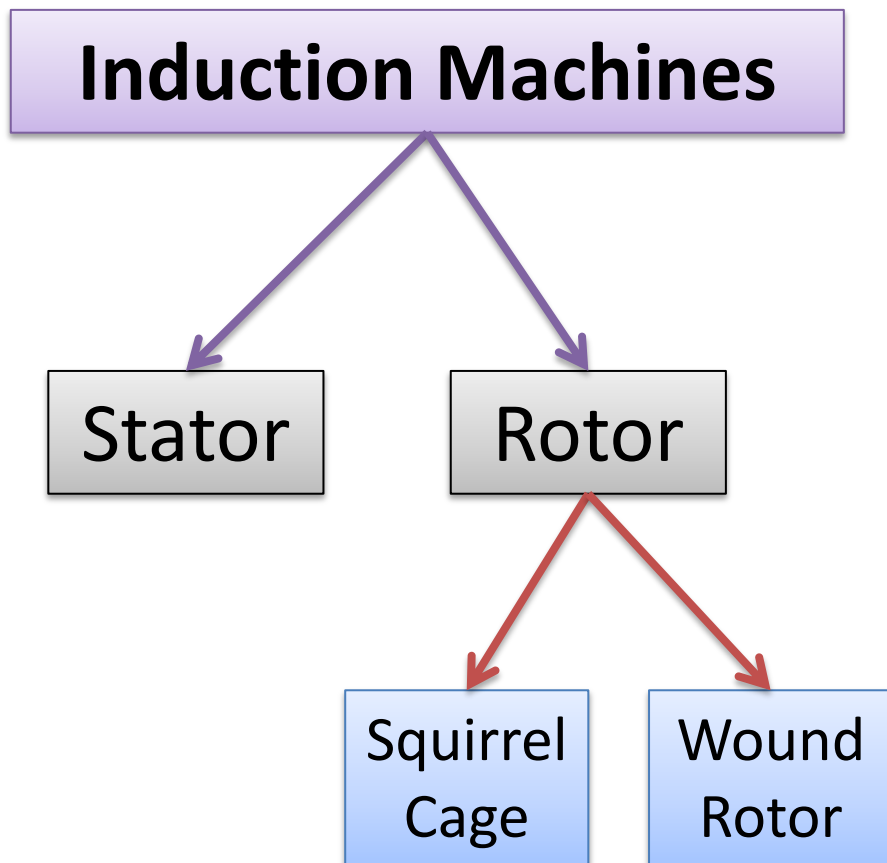

Structure of Induction Machines

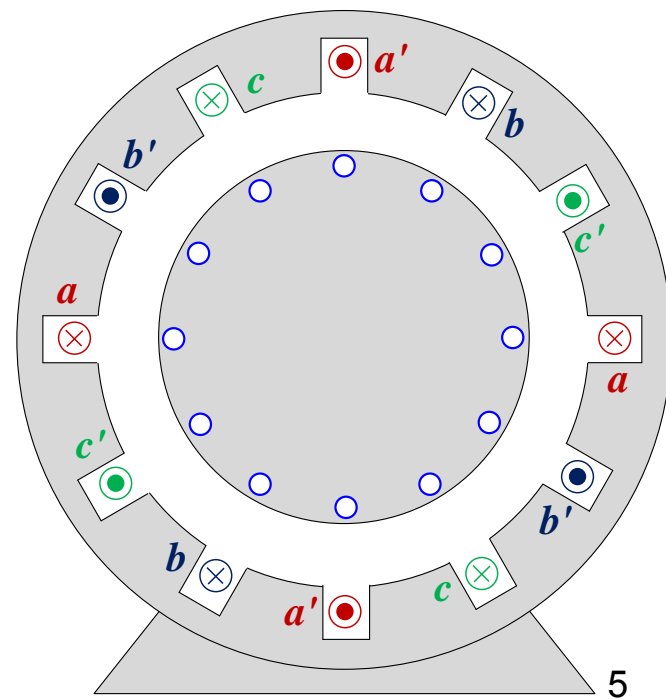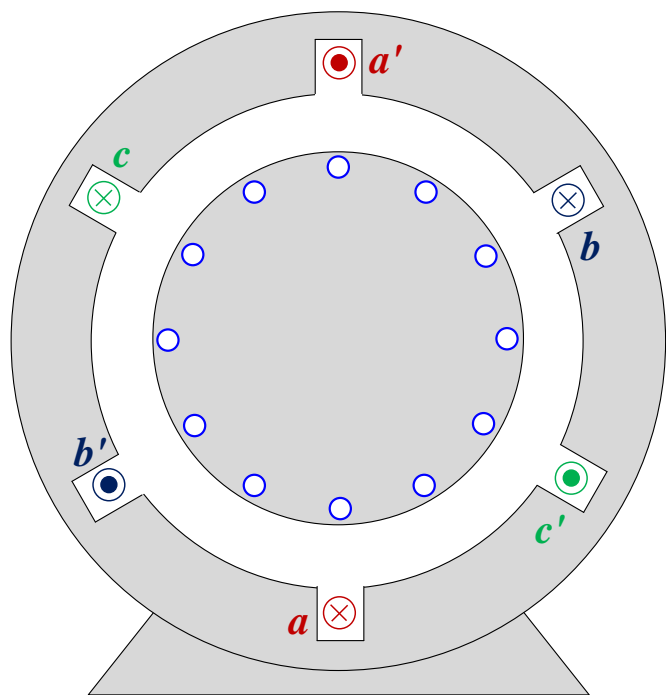
1. Stator

- The stator core is made from the **laminated** steel.
- The windings are located in **slots**.
- Three-phase windings are connected in **star** or **delta** configuration.






Structure of Induction Machines


1. Stator

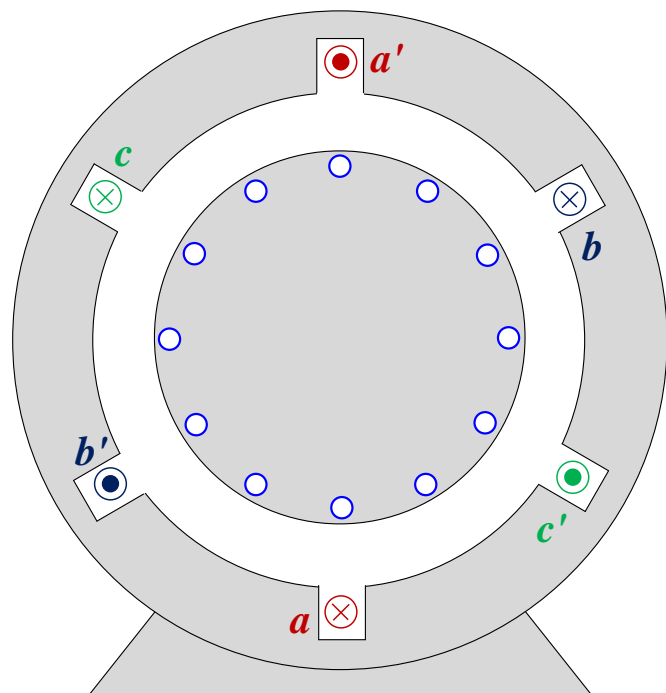

Star

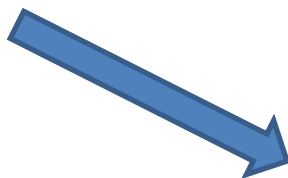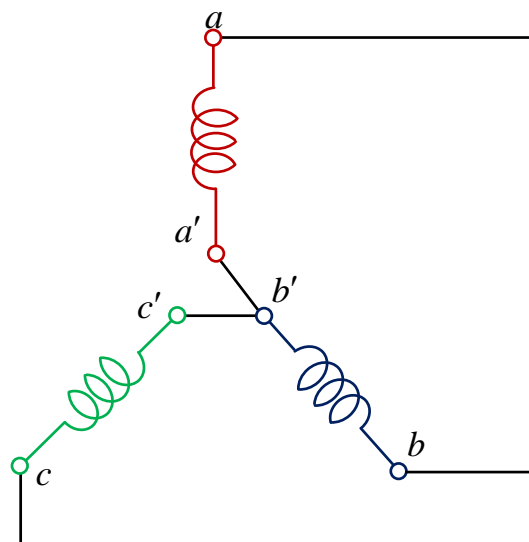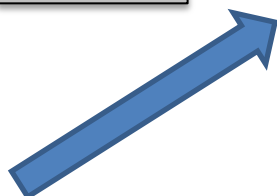

Delta

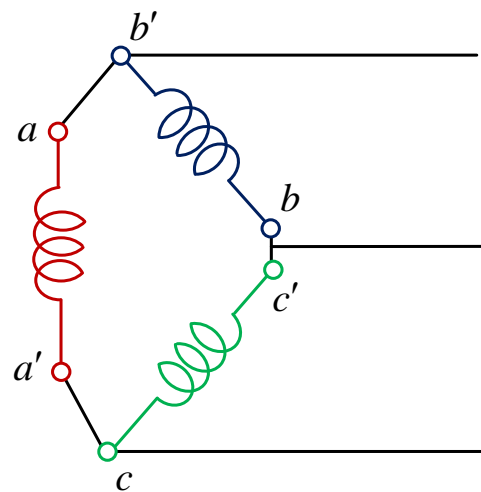


Structure of Induction Machines

2. Rotor

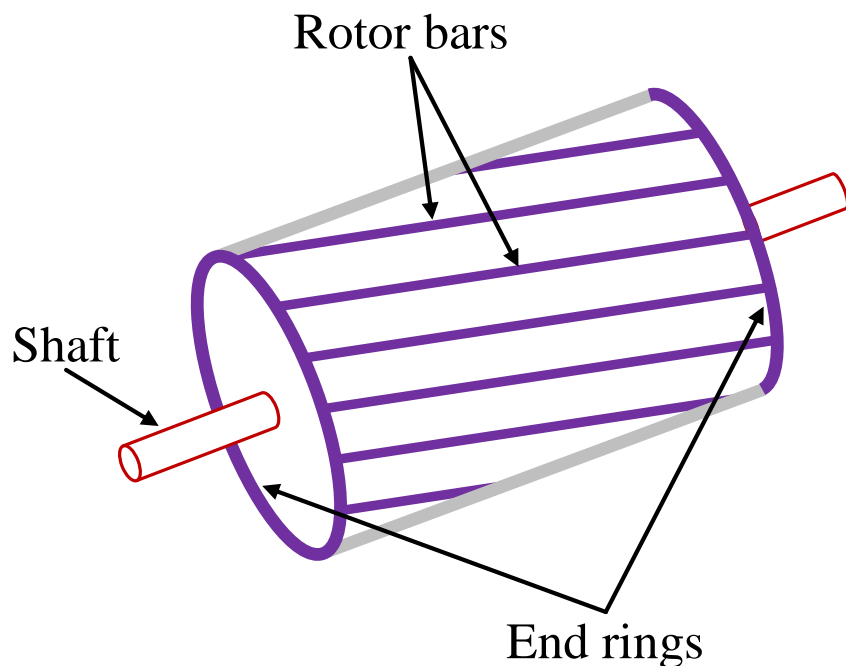A. Squirrel Cage

- Aluminium or copper bars are located in rotor slots.
- The bars are short-circuited from both sides using end rings.




Structure of Induction Machines

2. Rotor

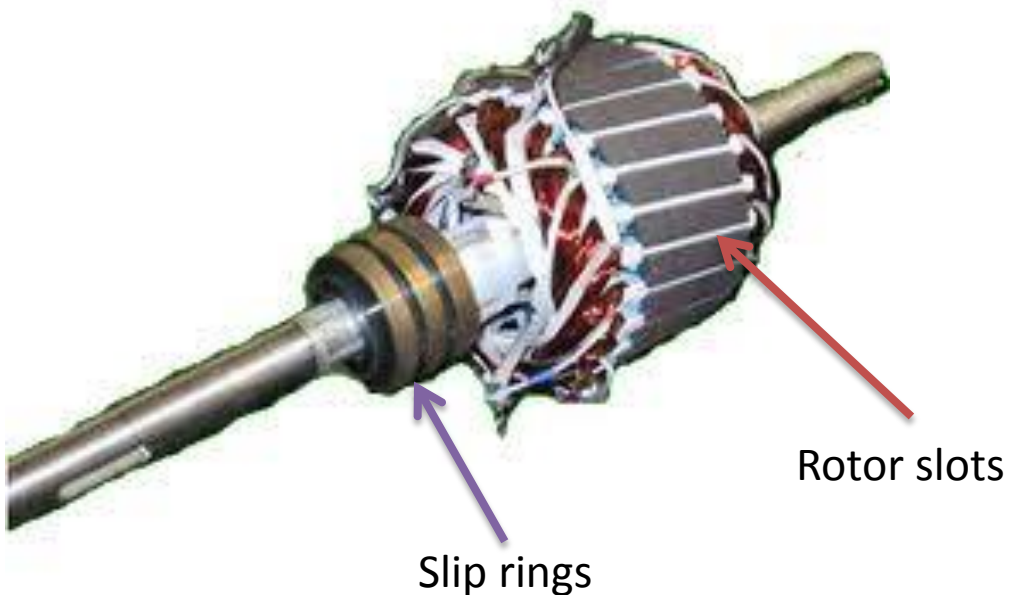B. Wound Rotor

- Aluminium or copper windings are located in rotor slots.
- There are three slip-rings and brushes used for energy transfer.




Basic Notions of Induction Machines

- Synchronous speed.** Assume the frequency of the applied voltage to the stator winding is f and the machine has p poles; the synchronous speed is defined as:

$$N_s = \frac{120f}{p} \quad \text{rpm}$$

$$n_s = \frac{2f}{p} \quad \text{rps}$$
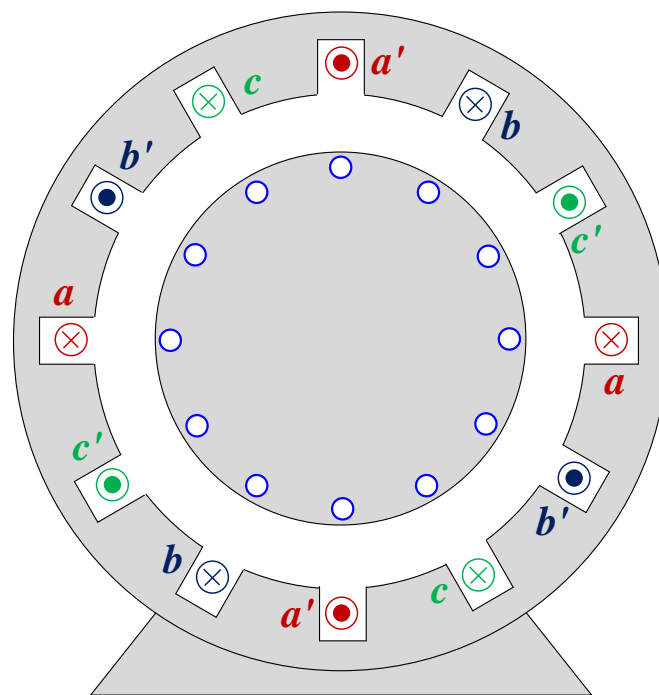
$$\omega_s = \frac{4\pi f}{p} \quad \text{rad/s}$$



Synchronous speed is a **mechanical** quantity.

Basic Notions of Induction Machines

2. **Rotor speed** is the speed of the rotor.

In motoring mode

$$N_r < N_s \quad \text{rpm}$$

$$n_r < n_s \quad \text{rps}$$


$$\omega_r < \omega_s \quad \text{rad/s}$$

In generating mode

$$N_r > N_s \quad \text{rpm}$$

$$n_r > n_s \quad \text{rps}$$
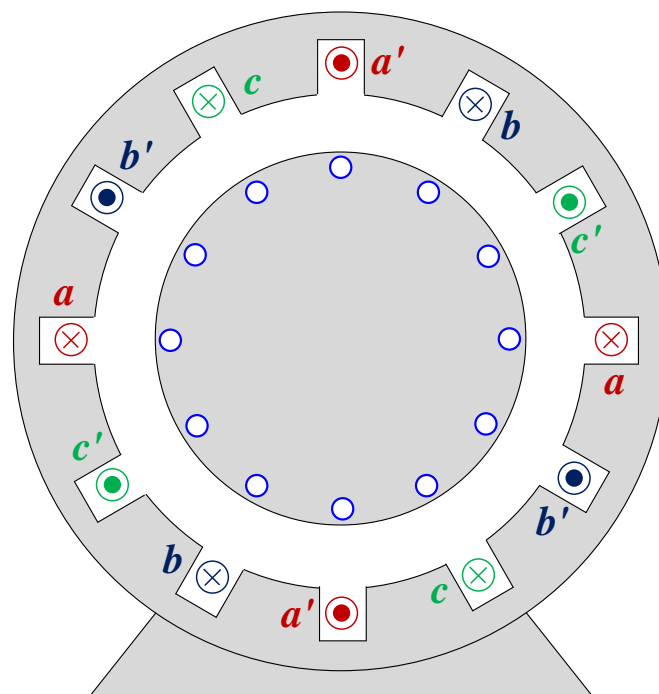
$$\omega_r > \omega_s \quad \text{rad/s}$$



Rotor speed is a **mechanical** quantity.

Basic Notions of Induction Machines




3. **Slip speed** is the difference between the synchronous speed and the rotor speed:

$$N_{slip} = N_s - N_r \quad \text{rpm}$$

$$n_{slip} = n_s - n_r \quad \text{rps}$$
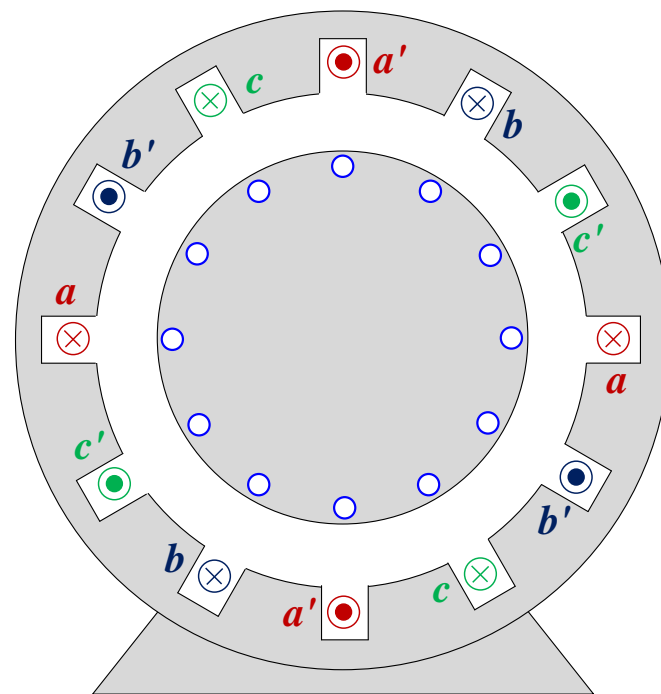
$$\omega_{slip} = \omega_s - \omega_r \quad \text{rad/s}$$




Slip speed is a **mechanical** quantity.

Basic Notions of Induction Machines

4. **Slip** is the slip speed divided by the synchronous speed:

$$\begin{aligned}
 S &= \frac{N_s - N_r}{N_s} \\
 &= \frac{n_s - n_r}{n_s} \\
 &= \frac{\omega_s - \omega_r}{\omega_s}
 \end{aligned}$$

$$N_r = (1 - S)N_s \quad \text{rpm}$$

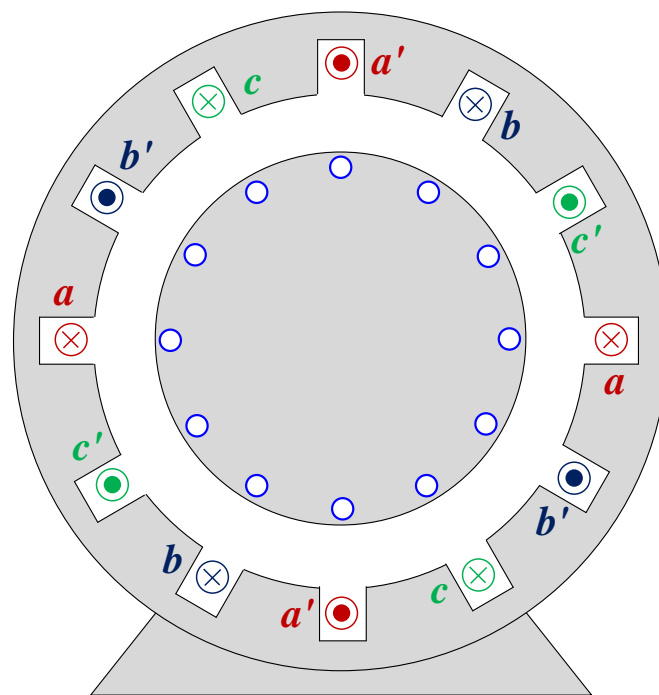

Slip is a **dimensionless** quantity.


How Does an Induction Motor Work?



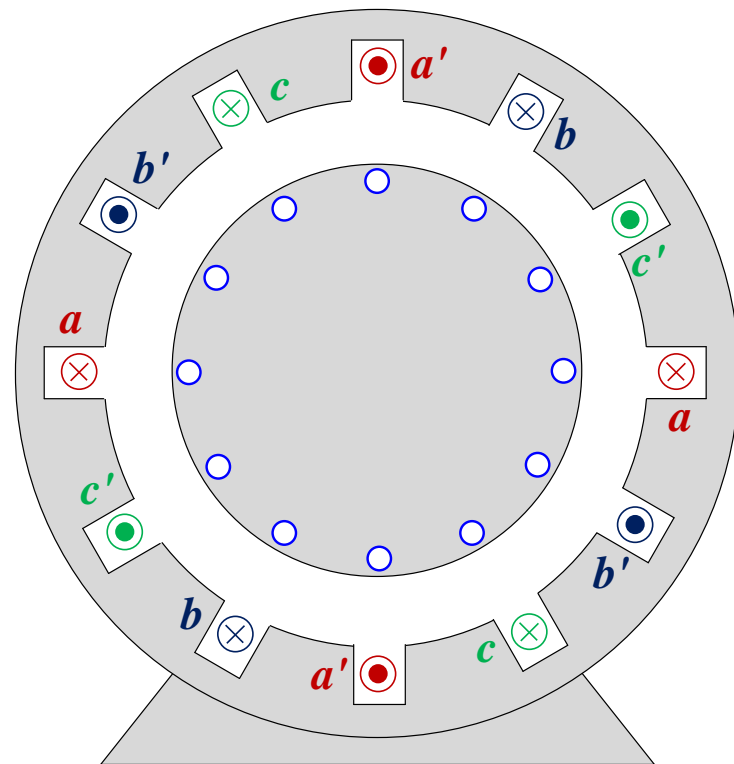1. Connecting the 3-phase stator windings to a 3-phase AC source flows the **current in the stator windings**.
2. The stator current causes a **rotating magnetic field** with synchronous speed.
3. The rotating magnetic field, **induces a voltage** in the rotor bars.
4. Since the rotor bars are short-circuited by end-rings, a **current flows in the rotor bars**.
5. The rotor bar current produces **another rotating magnetic field** which rotates with synchronous speed in the same direction as the stator magnetic field.
6. Electromagnetic **torque** is developed due to the interaction between two magnetic fields.
$$T_{em} = k B_r \times B_s$$
7. The developed torque can **rotate** the rotor.


What is Meant by Asynchronous?

- The induced voltage in rotor bars is due to the stator rotating magnetic field.
- Therefore if the rotor rotates with synchronous speed, no voltage is induced in the rotor bars and no torque can be developed.
- Hence, to develop torque, the rotor speed should be different from the synchronous speed.
- It is because induction motors are often called asynchronous motors.



What is Meant by Asynchronous?

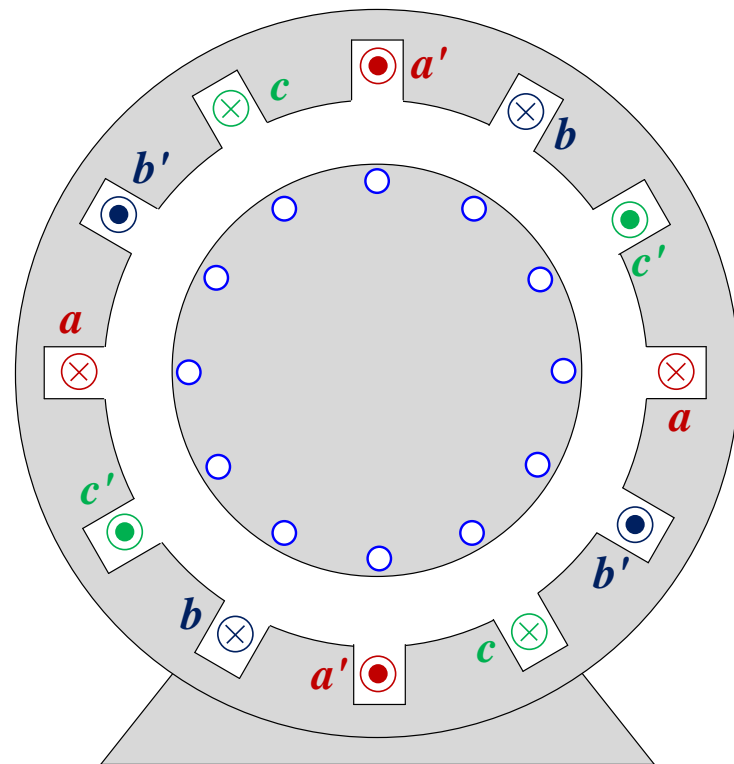
- The induced voltage in rotor bars is due to the stator rotating magnetic field.
- Therefore if the rotor rotates with synchronous speed, no voltage is induced in the rotor bars and no torque can be developed.
- Hence, to develop torque, the rotor speed should be different from the synchronous speed.
- It is because induction motors are often called asynchronous motors.



Different Operating Mode of Induction Machines

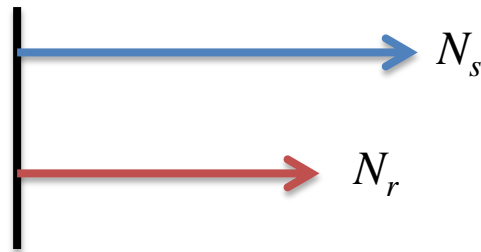
1. Motoring Mode

- The stator windings are connected to a 3-phase ac source.
- The mechanical energy is delivered on the motor shaft.



$$0 \leq N_r \leq N_s$$


$$1 \geq S \geq 0$$

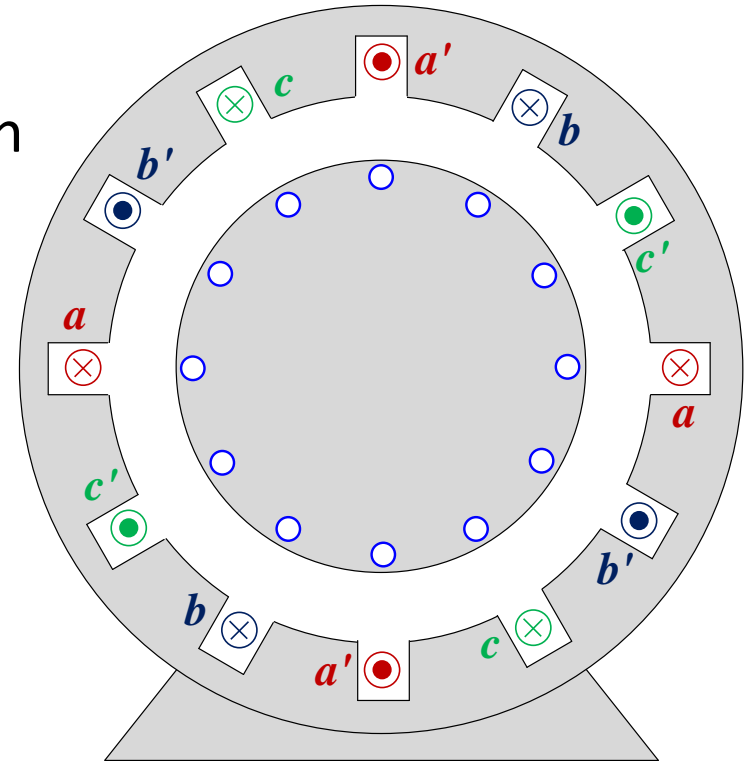

Different Operating Mode of Induction Machines

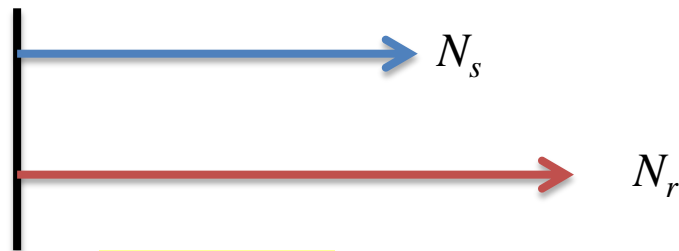
2. Generating Mode

- The stator windings are connected to a 3-phase ac source.
- The machine is in motoring mode.
- If by using a mechanical mover the rotor speed is increased to above synchronous speed the machine will be a generator.



$$N_r > N_s$$

$$S < 0$$

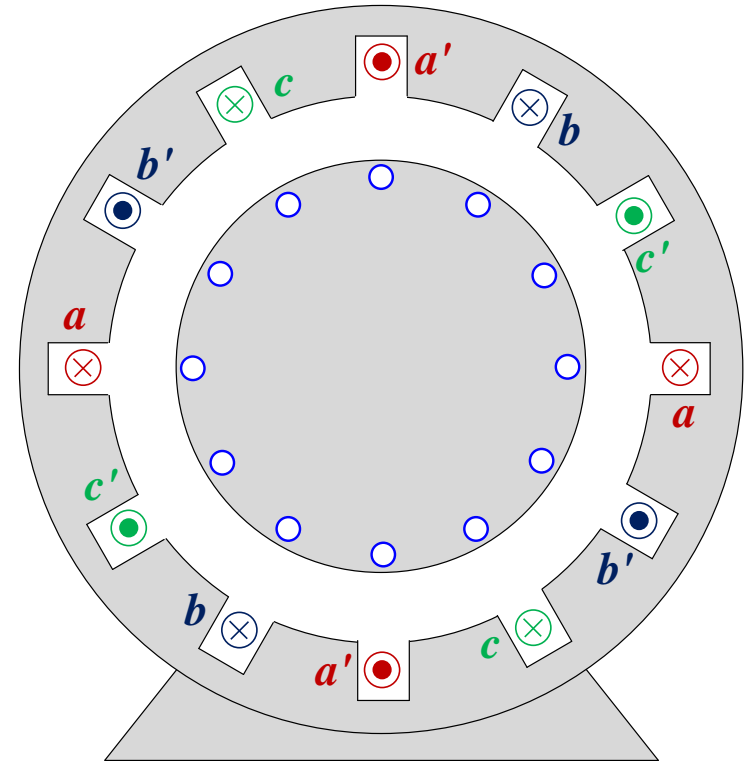


Different Operating Mode of Induction Machines



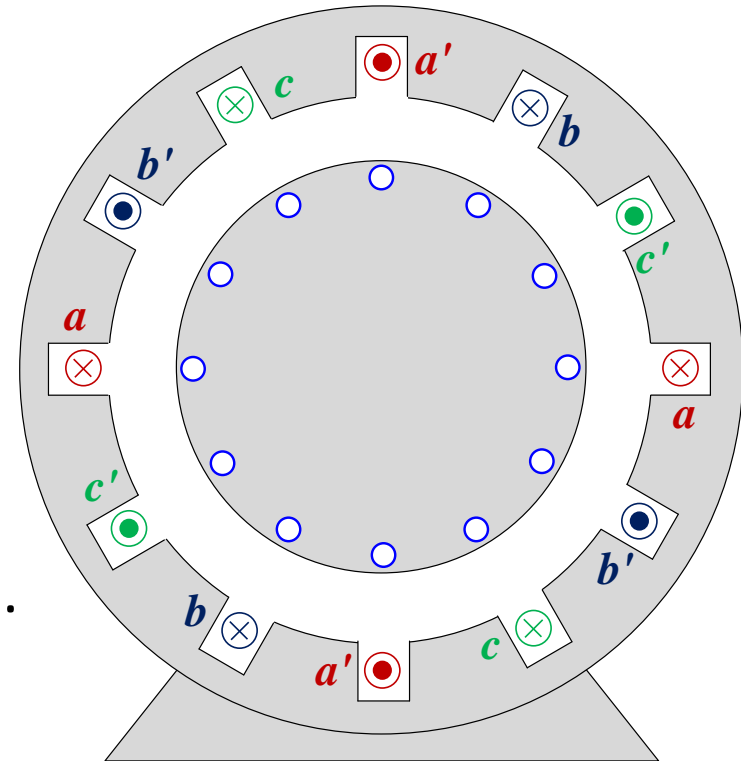
3. Plugging or Braking Mode

- If during the motoring mode the sequence of the applied voltage is changed,
- then the rotating magnetic field will change the direction,
- due to rotor inertia the magnetic field speed is in opposite of the rotor speed.
- The rotor will change the direction of rotation if it is not disconnected from the source.



$$N_r < 0$$

$$S > 1$$

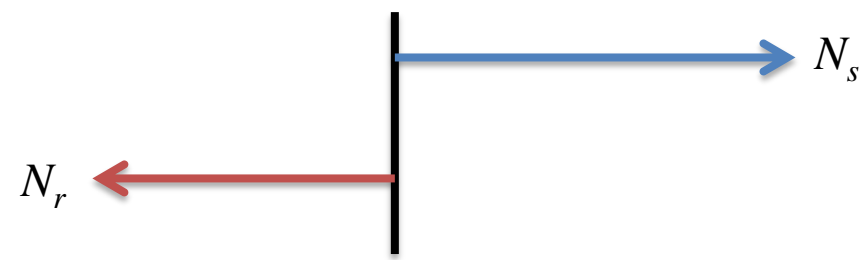

Motoring Mode



Assume the stator of a p -pole induction motor is connected to an ac source with frequency of f_1 ,

$$S = \frac{N_s - N_r}{N_s}$$

$$N_{slip} = N_s - N_r = SN_s$$

The rotor voltage/current frequency is

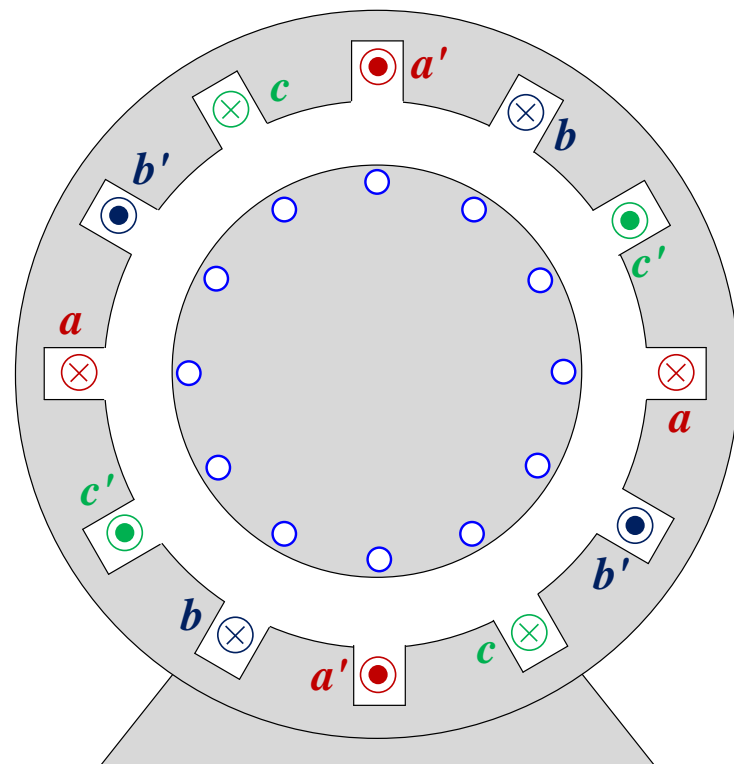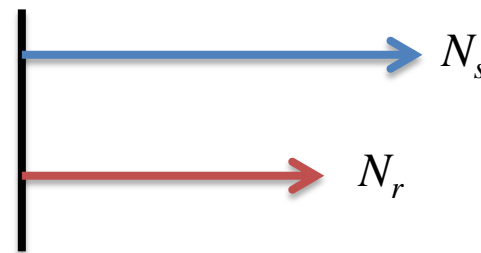
$$f_2 = \frac{p(N_s - N_r)}{120} = \frac{pSN_s}{120} = Sf_1$$



Motoring Mode


The speed of the rotor magnetic field with respect to rotor is
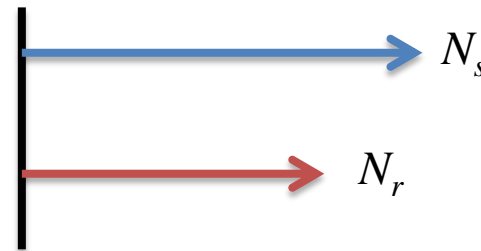
$$N_{frr} = \frac{120 f_2}{p} = \frac{120 S f_1}{p} = S N_s$$



The speed of the rotor magnetic field with respect to stator is

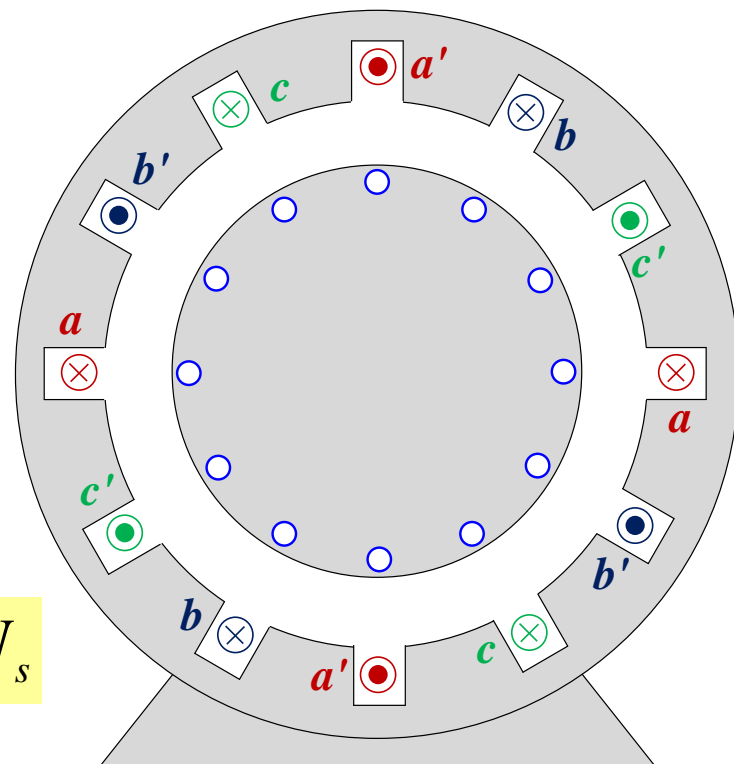
$$N_{frs} = N_r + N_{frr} = (1 - S) N_s + S N_s = N_s$$



Motoring Mode

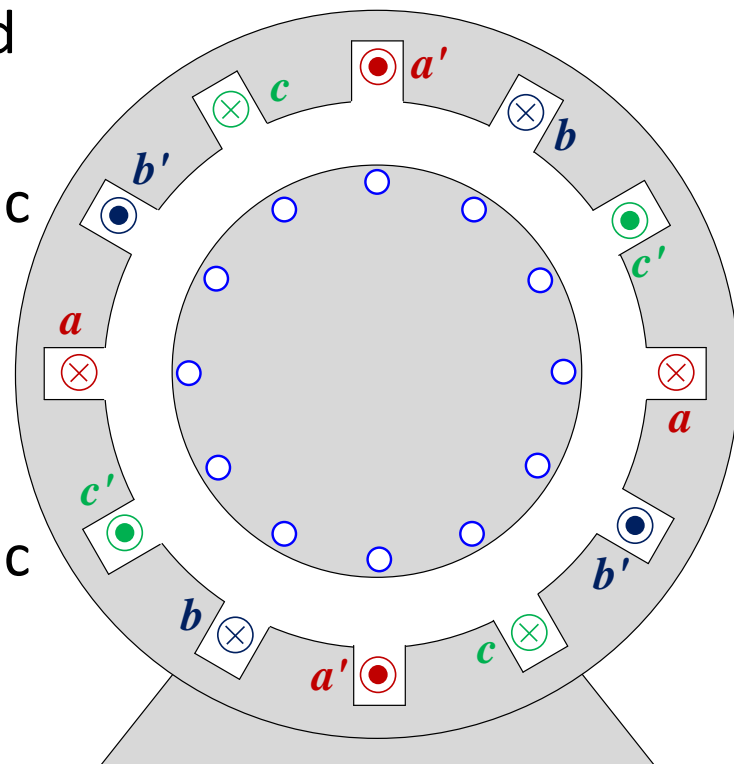Example: Consider a 3-phase induction motor with 460 V, 100 horsepower, 4-pole and 60 Hz which delivers the nominal power at the slip of 5%.

- Calculate the synchronous speed and the rotor speed
- Calculate the speed of rotor magnetic field
- Calculate the rotor frequency
- Calculate the slip speed
- Calculate the speed of rotor magnetic field with respect to (1) rotor; (2) stator; and stator magnetic field.



Motoring Mode

Solution:

$$a) \quad N_s = \frac{120 f_1}{p} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

$$f_1 = 60 \text{ Hz}$$

$$p_1 = 4$$


$$S = 0.05$$

$$N_r = (1 - S)N_s = 1710 \text{ rpm}$$

$$b) \quad N_{frs} = N_s = 1800 \text{ rpm}$$

$$c) \quad f_2 = s f_1 = 3 \text{ Hz}$$
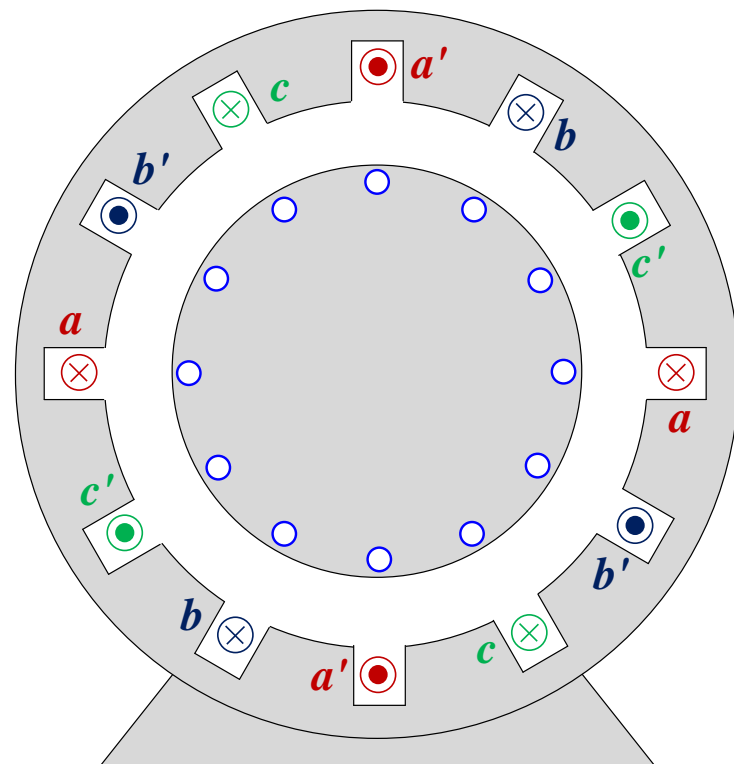
$$d) \quad N_{slip} = S N_s = 90 \text{ rpm}$$



Motoring Mode

Solution:

e) $N_{frr} = SN_s = 90 \text{ rpm}$


$N_{frs} = N_s = 1800 \text{ rpm}$

$N_{frfs} = 0$

$f_1 = 60 \text{ Hz}$



$p_1 = 4$

$S = 0.05$

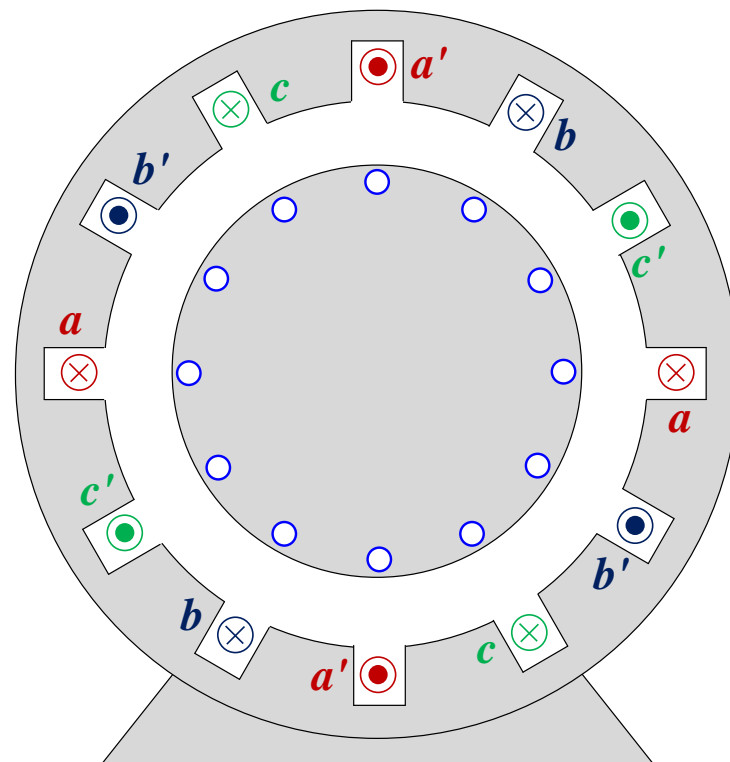


Equivalent Circuits of Induction Motors

Stator Equivalent Circuit

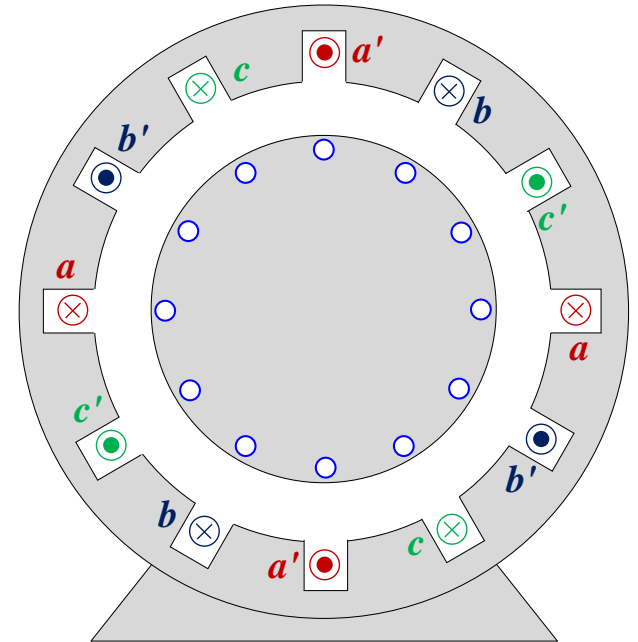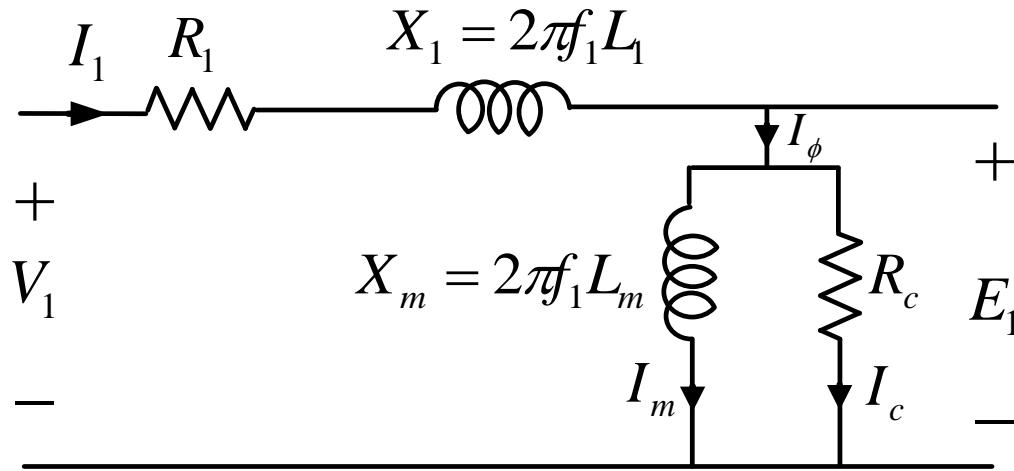


Rotor Equivalent Circuit

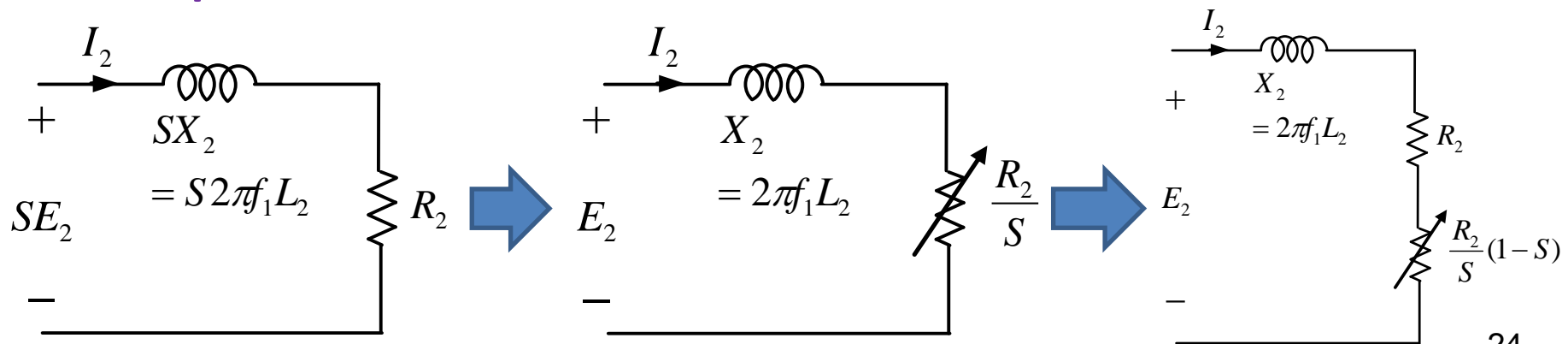

Equivalent Circuits of Induction Motors

Total Equivalent Circuit

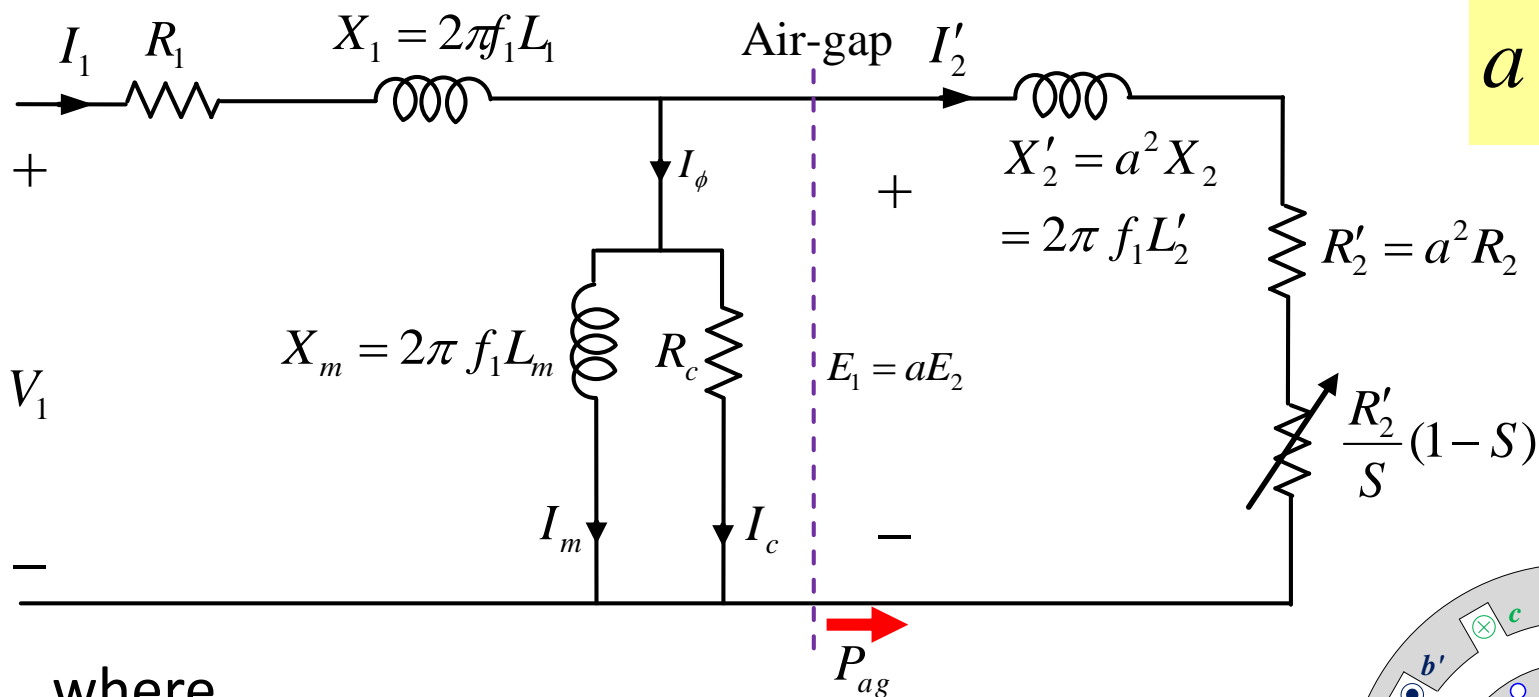


$$a = \frac{N_1 k_{w1}}{N_2 k_{w2}}$$

where

f_1 is the stator applied source frequency.

V_1 is the stator phase voltage.

R_1 is the per-phase stator resistance.

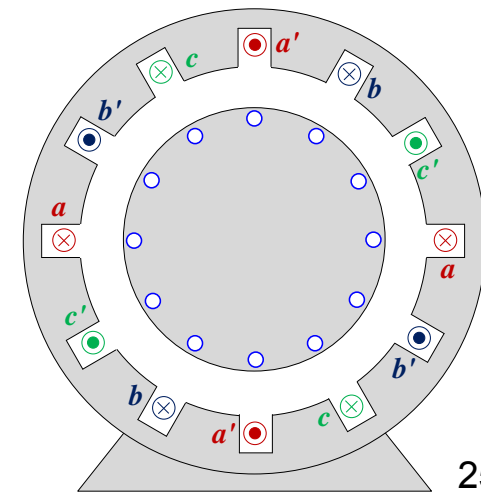

Equivalent Circuits of Induction Motors

Total Equivalent Circuit

L_1 is the per-phase stator leakage inductance.

X_1 is the per-phase stator leakage reactance.

E_1 is the phase induced voltage in stator.

L_m is the per-phase magnetizing inductance.

X_m is the per-phase magnetizing reactance.


R_c is the per-phase equivalent resistance to model core losses.

I_1 is the phase stator current.

I_ϕ is the phase excitation (no-load) current.

I_m is the phase magnetizing current.

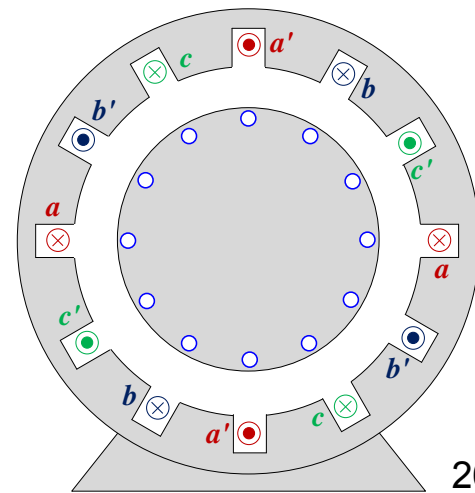I_c is the phase equivalent current to model core losses.




Equivalent Circuits of Induction Motors



Total Equivalent Circuit

- a is stator per rotor turn ratio.
- E_2 is the phase induced voltage in rotor.
- R_2 is the per-phase rotor resistance.
- R'_2 is the per-phase rotor resistance referred to stator.
- L_2 is the per-phase rotor leakage inductance.
- L'_2 is the per-phase rotor leakage inductance referred to stator.
- X_2 is the per-phase rotor leakage reactance under frequency of f_1 .
- X'_2 is the per-phase rotor leakage reactance referred to stator under frequency of f_1 .

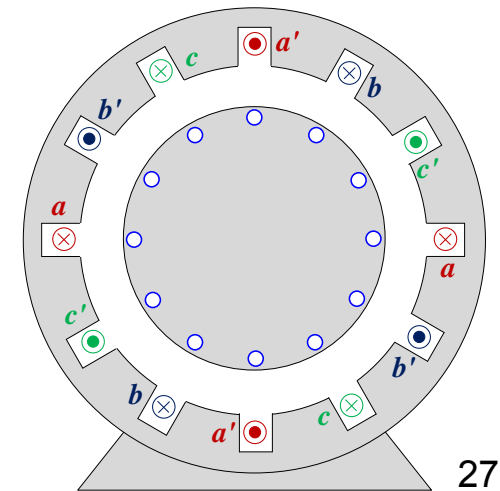



Equivalent Circuits of Induction Motors

Total Equivalent Circuit

I_2 is the phase rotor current.

I'_2 is the phase rotor current referred to stator.



P_{ag} is the per-phase air-gap power.

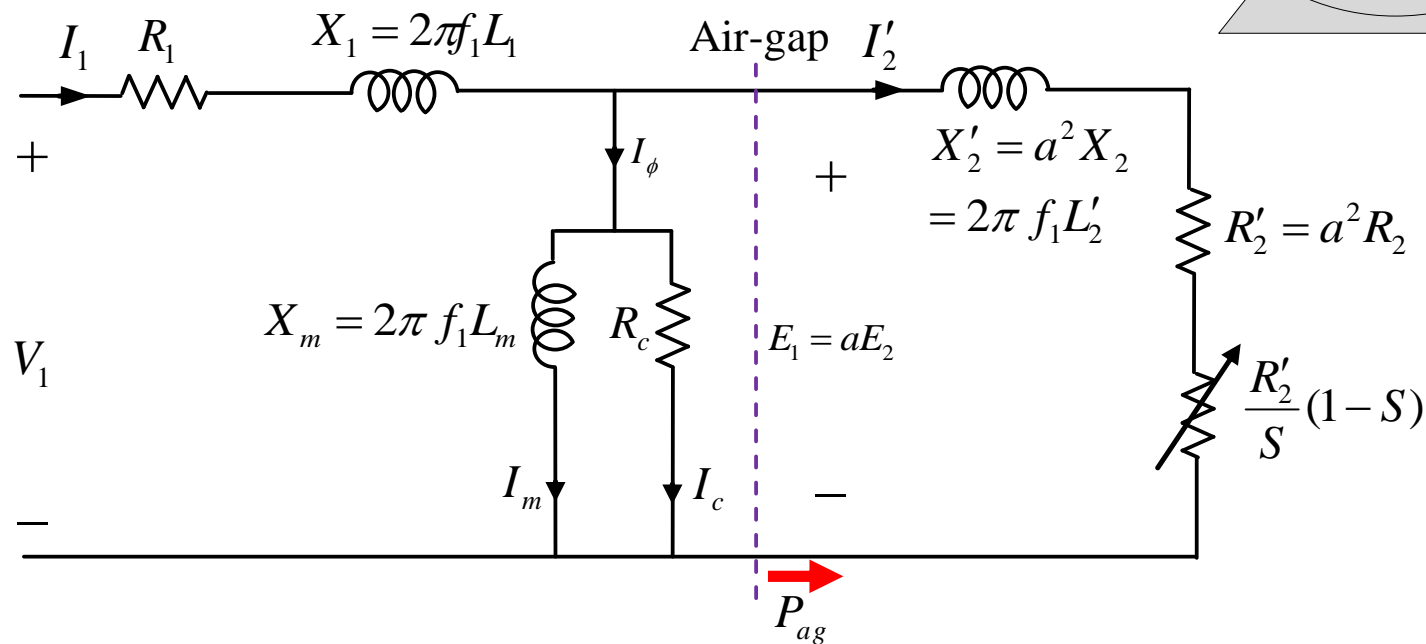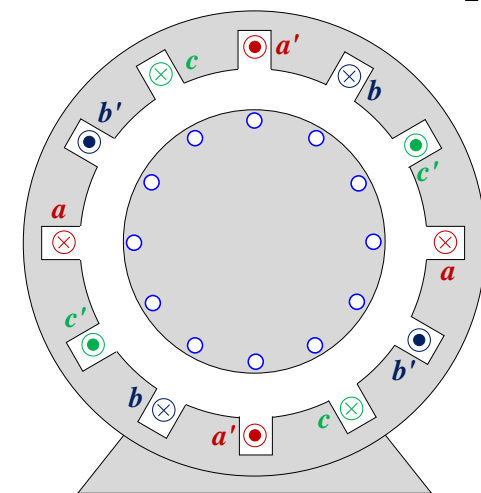

Equivalent Circuits of Induction Motors

A few points

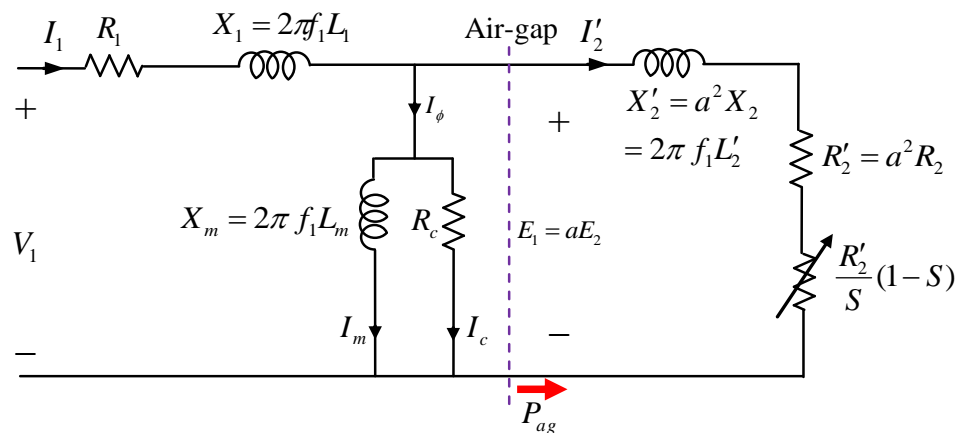
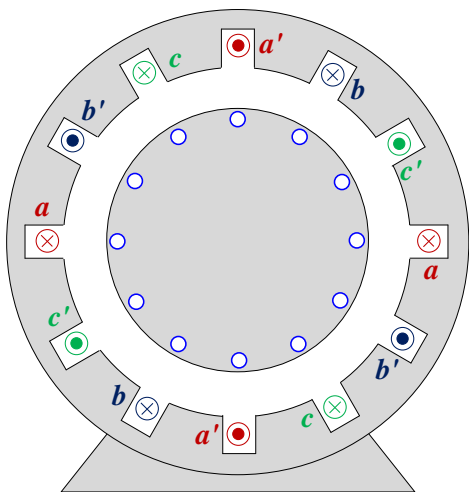
- The mentioned equivalent circuit is valid for single-phase of a 3-phase induction machine.
- In this equivalent circuit all quantities are per-phase.
- All quantities referred to stator side.
- The frequency of the equivalent circuit is f_1 .
- This equivalent circuit is similar to that of a transformer.





Air-Gap Power

Air-gap power = rotor copper losses + developed mechanical power

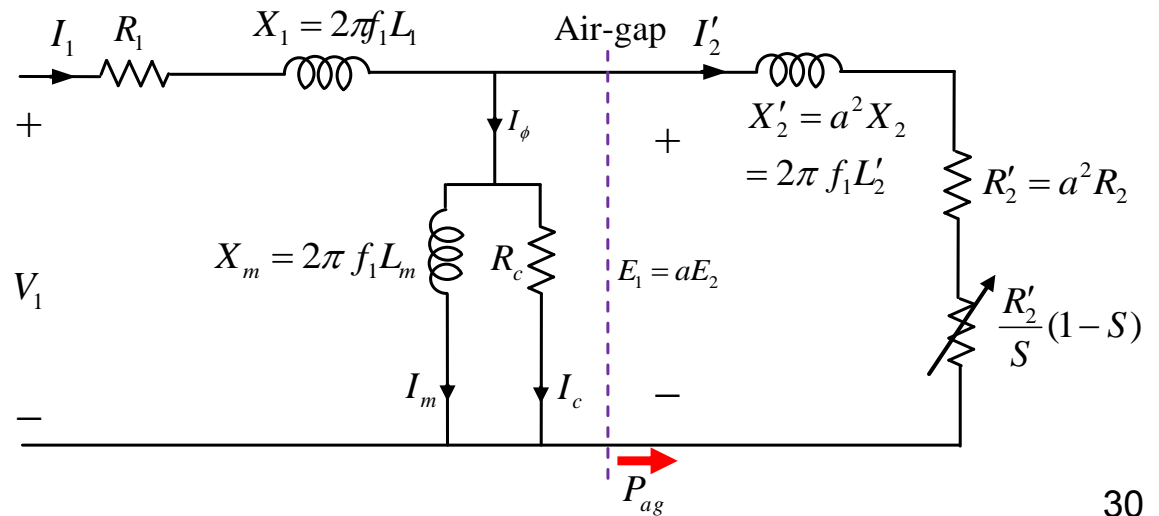
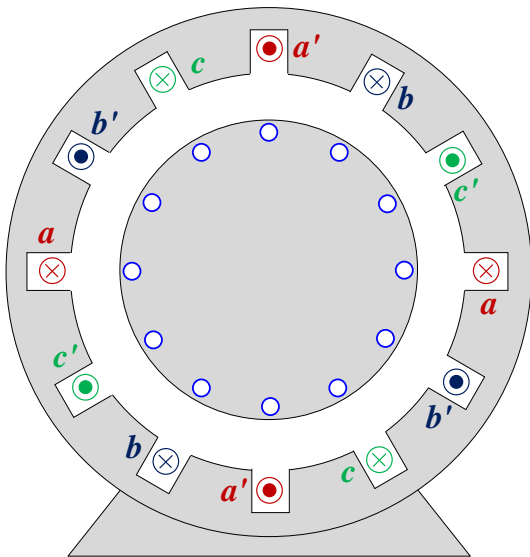
$$P_{ag} = R_2 I_2^2 + \frac{R_2}{S} (1-S) I_2^2$$



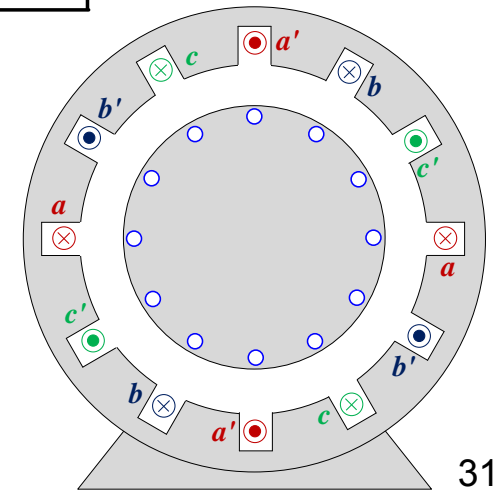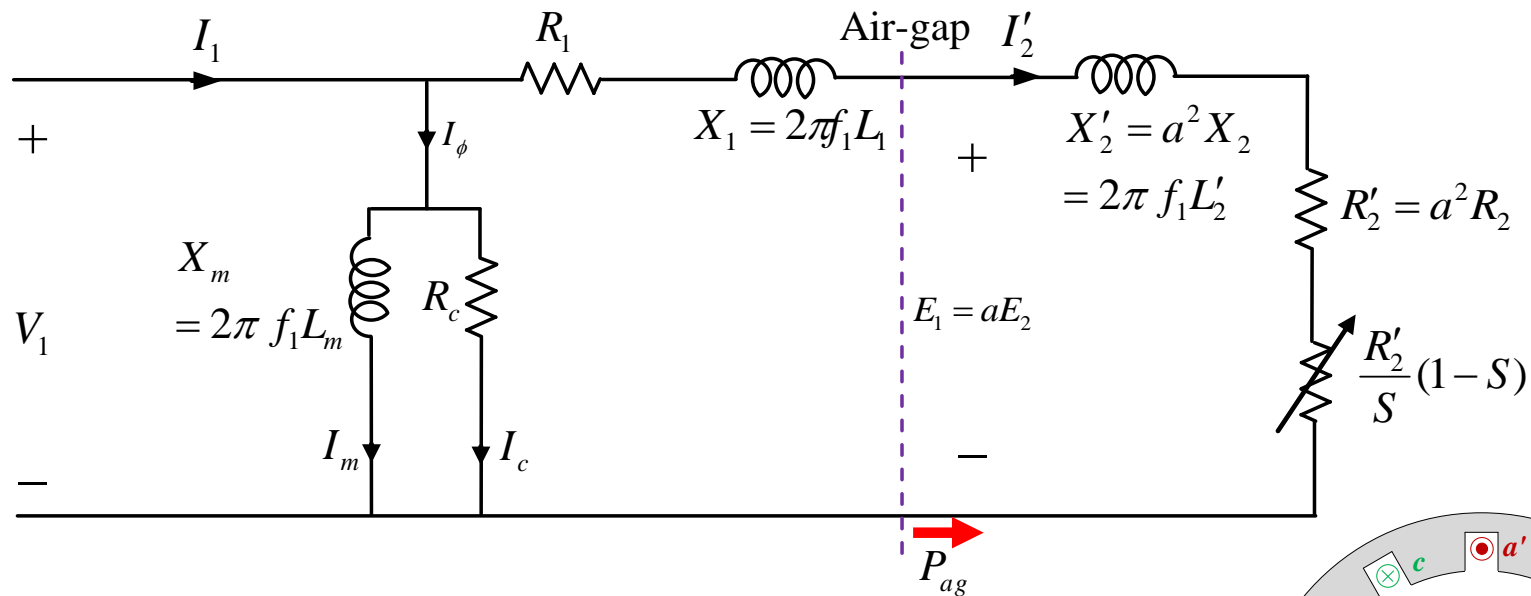Approximated Equivalent Circuits of Induction Motors



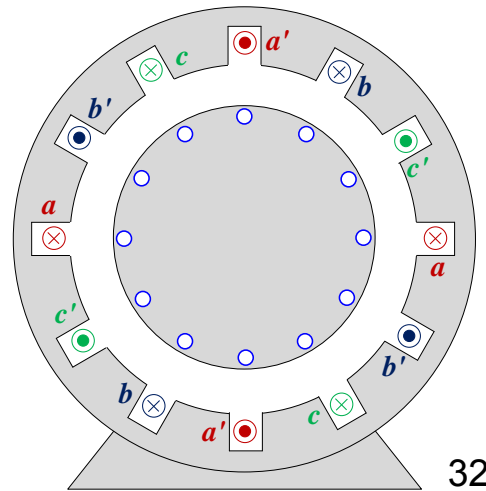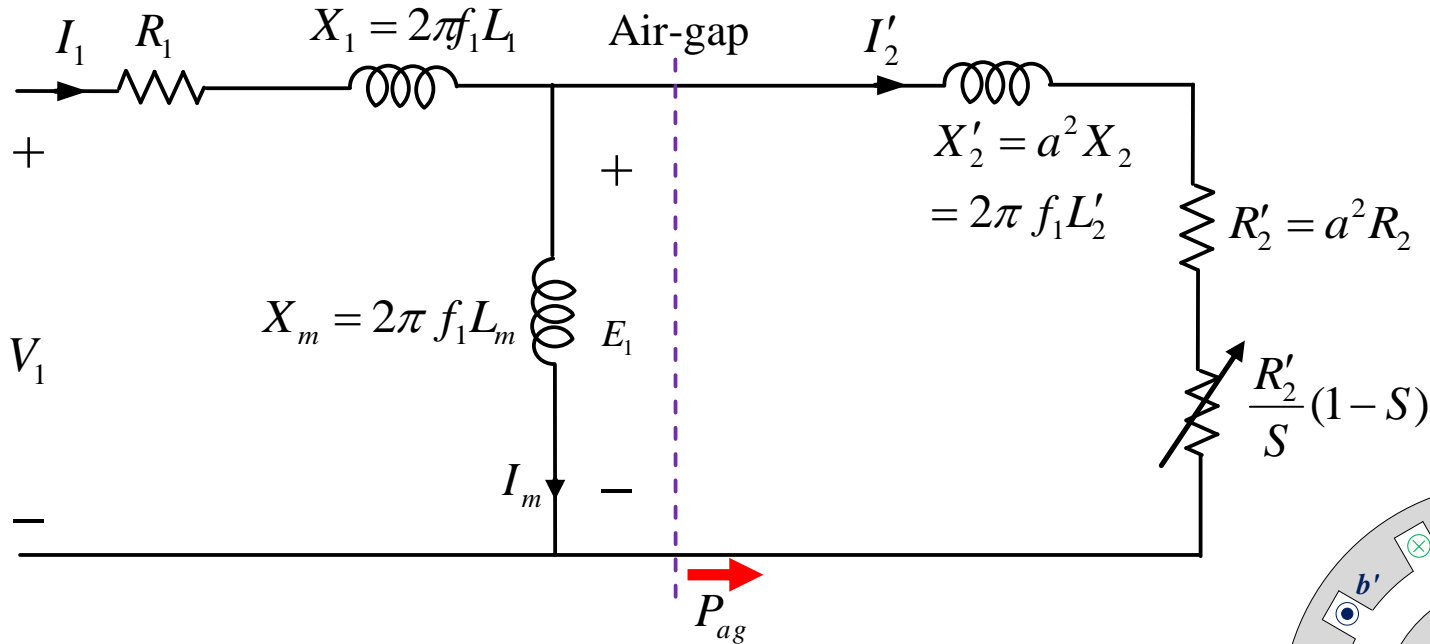
IEEE Equivalent Circuits of Induction Motors




R_c has been removed from the circuit and core losses assumed to be a constant value.

Thevenin's Equivalent Circuits of Induction Motors

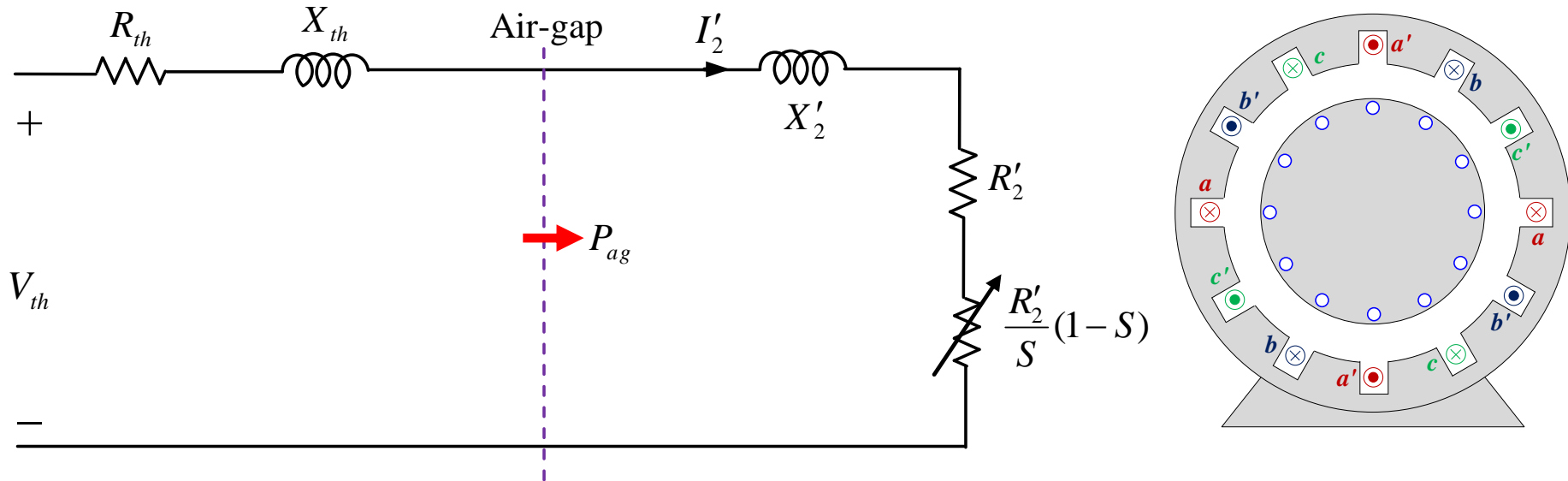It is obtained from the IEEE equivalent circuit.



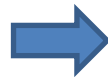
$$V_{th} = \frac{X_m}{\sqrt{R_1^2 + (X_1 + X_m)^2}} V_1$$



$$V_{th} \approx \frac{X_m}{X_1 + X_m} V_1$$
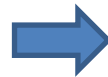
$$Z_{th} = \frac{jX_m(R_1 + jX_1)}{R_1 + j(X_1 + X_m)} = R_{th} + jX_{th}$$




$$R_{th} \approx \left(\frac{X_m}{X_1 + X_m} \right)^2 R_1$$

$$X_{th} \approx X_1$$



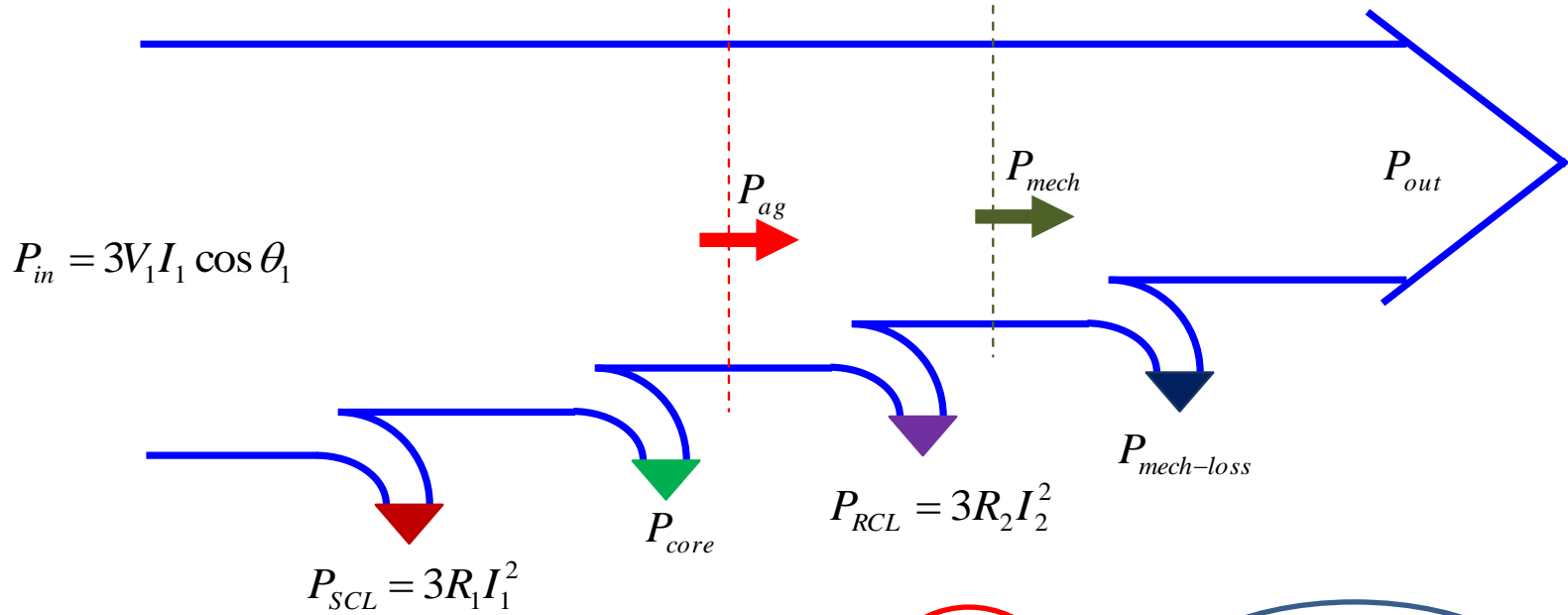Power and Torque in 3-phase Induction Motors



Air-gap power

$$P_{ag} = 3 \frac{R_2}{S} I_2^2 = 3R_2 I_2^2 + 3 \frac{R_2}{S} (1-S) I_2^2$$

Rotor copper losses

$$P_{RCL} = S P_{ag}$$

Mechanical power

$$P_{mech} = (1-S) P_{ag}$$



Power and Torque in 3-phase Induction Motors

Input power = Stator copper losses + Core losses + Air-gap power

Air-gap power = Rotor copper losses + Developed mechanical power


Developed mechanical power = Mechanical losses + Output power

$$P_{mech} = (1 - S)P_{ag}$$

$$P_{mech} = T_{mech} \omega_r$$

$$\omega_r = (1 - S)\omega_s$$

$$P_{ag} = T_{mech} \omega_s$$

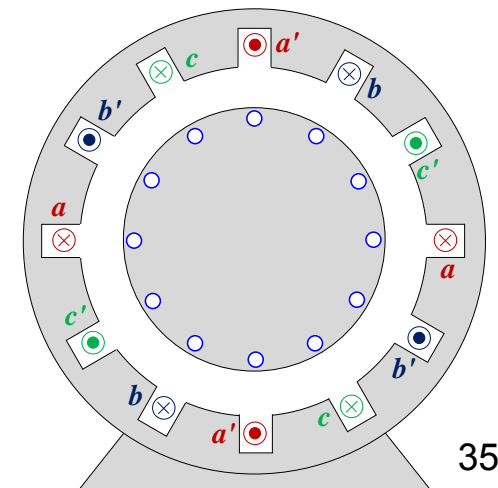

35

Power and Torque in 3-phase Induction Motors

Developed mechanical power

$$P_{ag} = T_{mech} \omega_s$$



&

$$P_{ag} = 3 \frac{R_2}{S} I_2^2$$



$$T_{mech} = \frac{3}{\omega_s} \frac{R_2}{S} I_2^2 = \frac{3}{\omega_s} \frac{R'_2}{S} I_2'^2$$

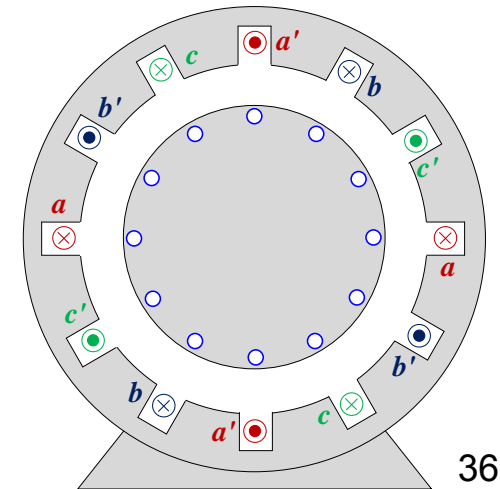
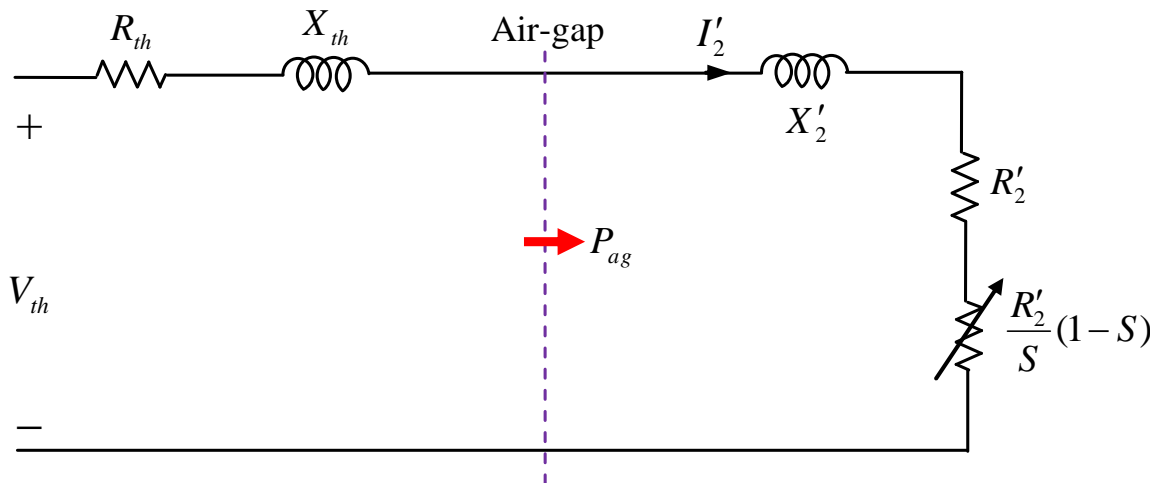
$$T_{mech} = \frac{3}{\omega_s} \frac{R'_2}{S} \frac{V_{th}^2}{\left(R_{th} + \frac{R'_2}{S}\right)^2 + \left(X_{th} + X'_2\right)^2}$$



Power and Torque in 3-phase Induction Motors

Developed mechanical power
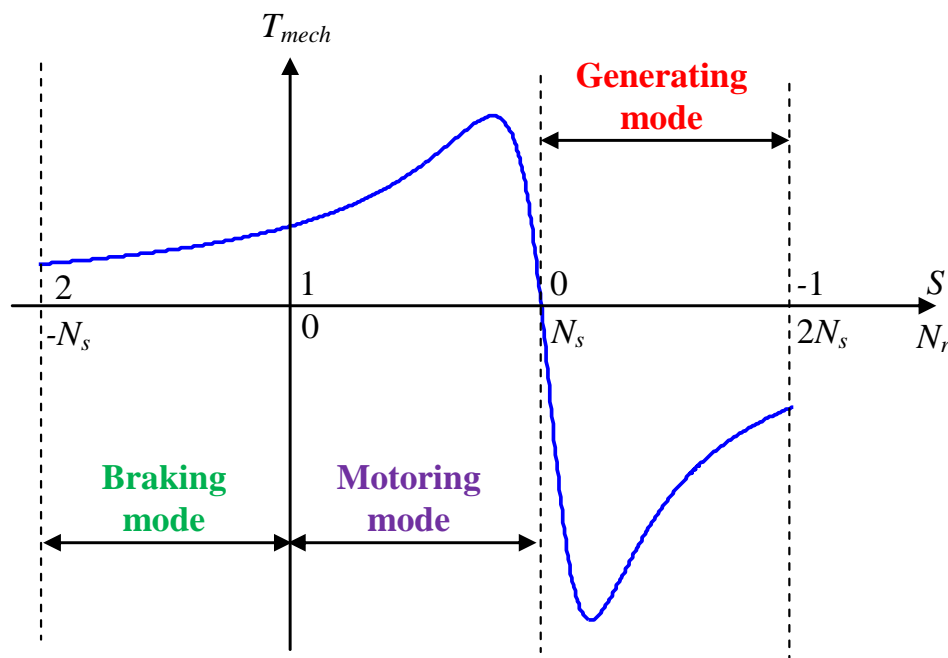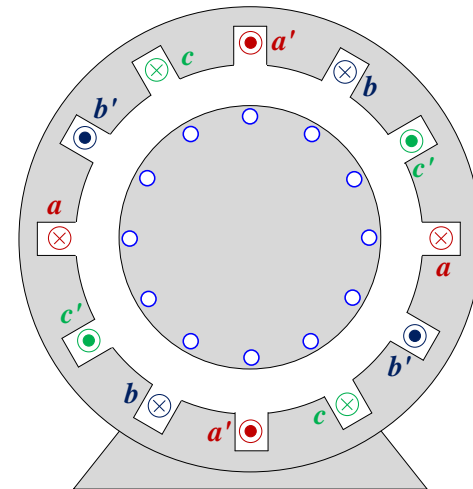
$$T_{mech} = \frac{3 R'_2}{\omega_s S} \frac{V_{th}^2}{\left(R_{th} + \frac{R'_2}{S}\right)^2 + \left(X_{th} + X'_2\right)^2}$$




Power and Torque in 3-phase Induction Motors



Developed mechanical power

$$T_{mech} = \frac{3 R'_2}{\omega_s S} \frac{V_{th}^2}{\left(R_{th} + \frac{R'_2}{S}\right)^2 + (X_{th} + X'_2)^2}$$

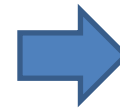If $R_{th} + \frac{R'_2}{S} \gg X_{th} + X'_2$ & $\frac{R'_2}{S} \gg R_{th}$



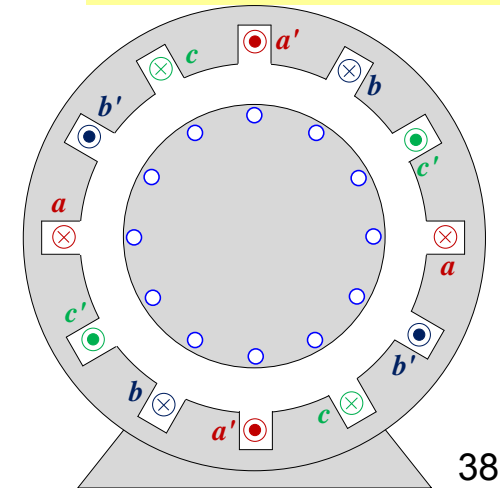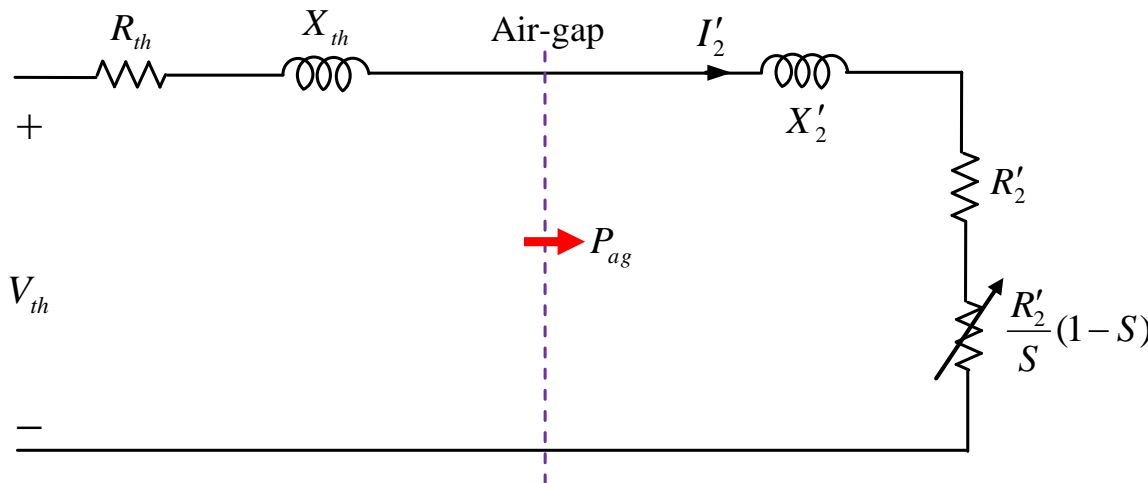
$$T_{mech} = \frac{3}{\omega_s} \frac{V_{th}^2}{R'_2} S$$



Power and Torque in 3-phase Induction Motors

Output or External Power



$$P_{out} = T_{out} \omega_r$$

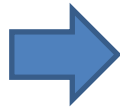

$$T_{out} = \frac{P_{out}}{\omega_r}$$


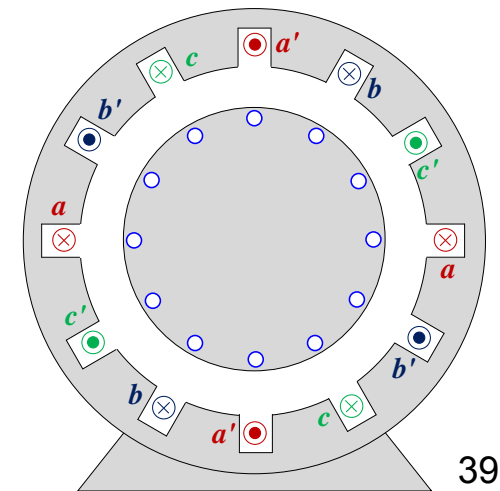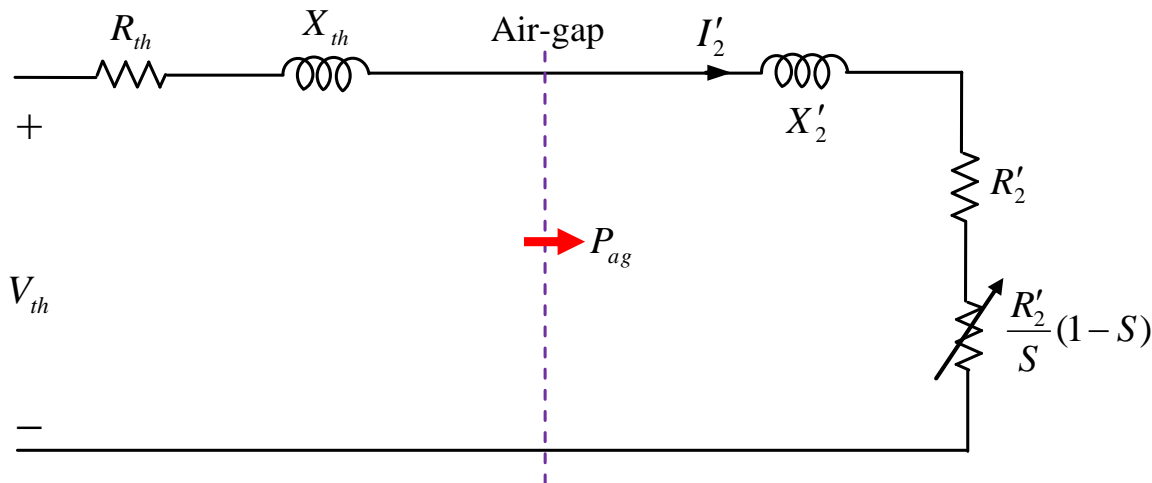
$$T_{out} = \frac{P_{mech} - P_{mech-loss}}{\omega_r}$$



Power and Torque in 3-phase Induction Motors

Maximum Torque

$$\frac{dT_{mech}}{dS} = 0$$



$$\frac{R'_2}{S_{T_{max}}} = \sqrt{R_{th}^2 + (X_{th} + X'_2)^2}$$




$$S_{T_{max}} = \frac{R'_2}{\sqrt{R_{th}^2 + (X_{th} + X'_2)^2}}$$



$$S_{T_{max}} \approx \frac{R'_2}{X_{th} + X'_2}$$

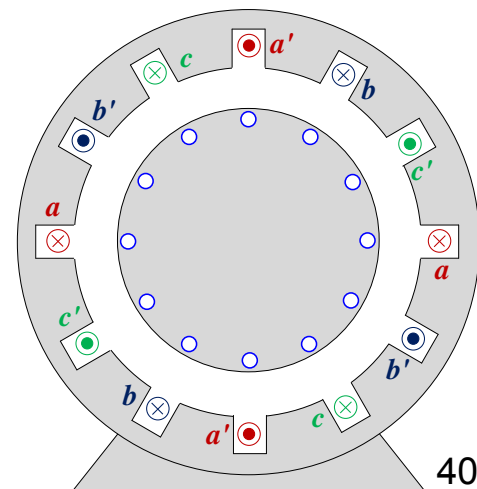The **slip of the maximum torque** depends on the **rotor resistance**.



Power and Torque in 3-phase Induction Motors

Maximum Torque

$$S_{T_{\max}} = \frac{R'_2}{\sqrt{R_{th}^2 + (X_{th} + X'_2)^2}}$$




$$S_{T_{\max}} \approx \frac{R'_2}{X_{th} + X'}$$

$$T_{\max} = \frac{3}{2\omega_s} \frac{V_{th}^2}{R_{th} + \sqrt{R_{th}^2 + (X_{th} + X'_2)^2}}$$



$$T_{\max} = \frac{3}{2\omega_s} \frac{V_{th}^2}{X_{th} + X'_2}$$

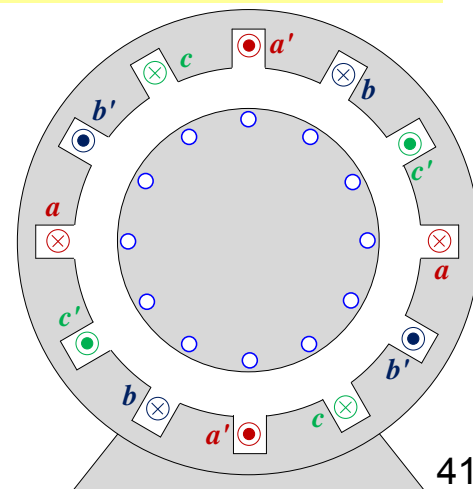The **maximum torque** is **independent** of the **rotor resistance**.



Power and Torque in 3-phase Induction Motors

Starting Torque

Starting torque is the torque when the rotor speed is zero or $S=1$.

$$T_{start} = \frac{3}{\omega_s} R'_2 \frac{V_{th}^2}{(R_{th} + R'_2)^2 + (X_{th} + X'_2)^2}$$

